

Using the ideal parameters

## Negative Logic AND Gate


Negative Logic

$$V(0) = 5V$$

$$V(1) = 0V$$

AND Gate

A	B	$V_o$
$V(0)$	$V(0)$	$V(0)$
$V(0)$	$V(1)$	$V(0)$
$V(1)$	$V(0)$	$V(0)$
$V(1)$	$V(1)$	$V(1)$


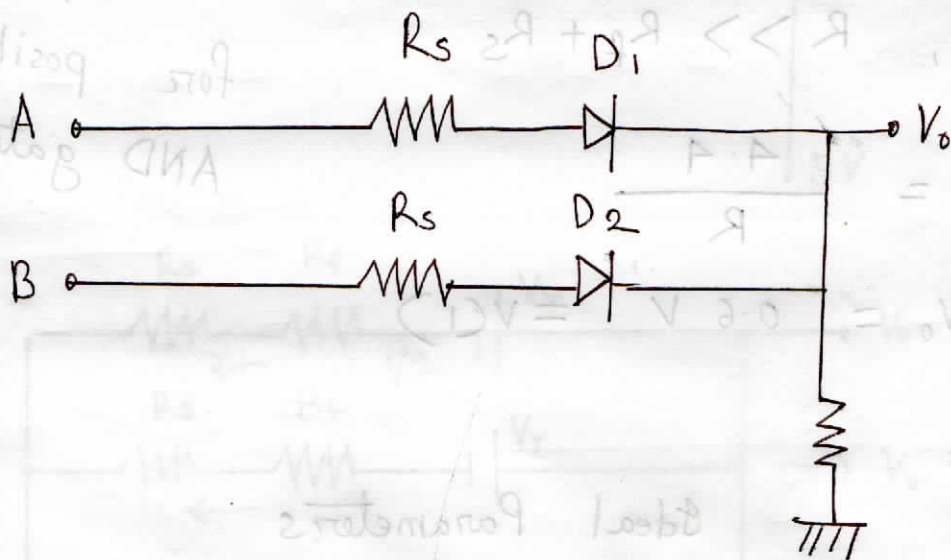


Case 1:

$$A = V(0) = 5V$$

$$B = V(0) = 5V$$

Both diodes are in forward bias

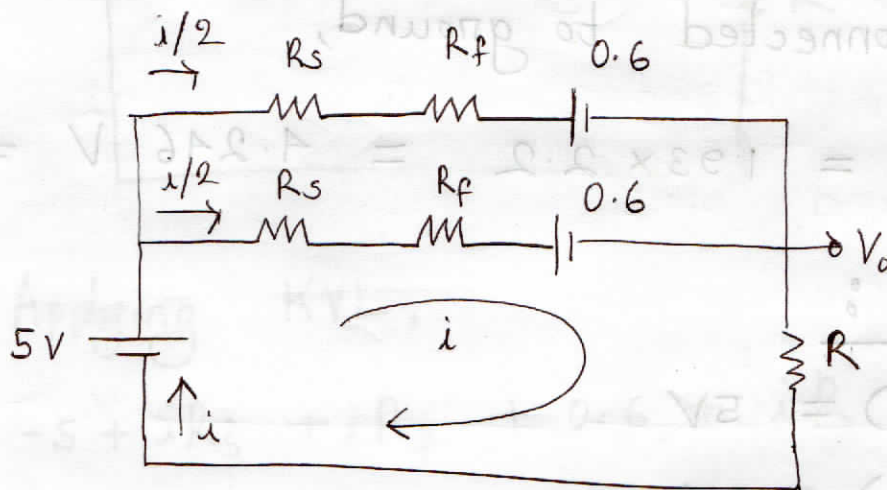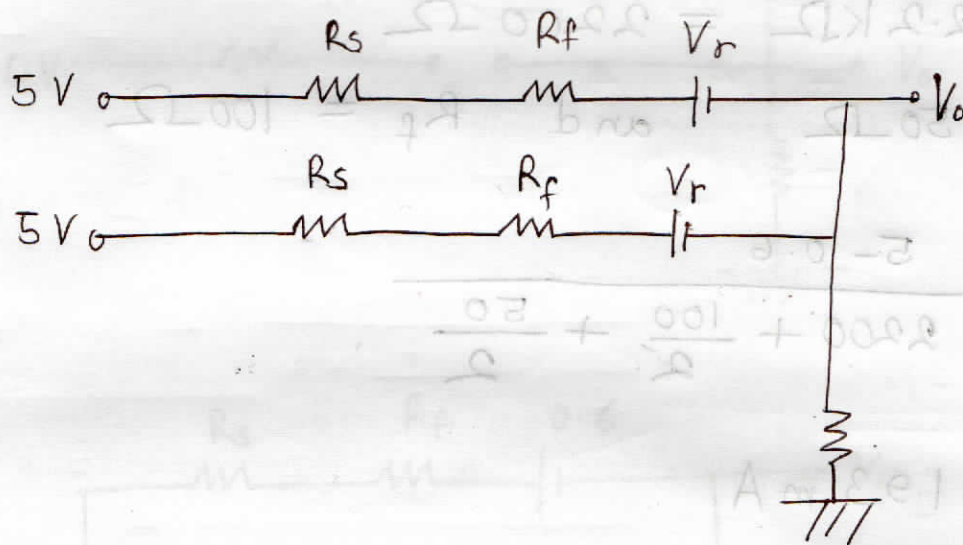

Applying KVL,

$$-5 + iR + V_r + \frac{i}{2} R_f + \frac{i}{2} R_s = 0$$

$$i = \frac{5 - V_r}{R + \frac{R_f}{2} + \frac{R_s}{2}}$$

Putting the ideal parameters, i.e.

$$R = 2.2 \text{ k}\Omega = 2200 \Omega$$

$$R_s = 50 \Omega \quad \text{and} \quad R_f = 100 \Omega$$

$$i = \frac{5 - 0.6}{2200 + \frac{100}{2} + \frac{50}{2}}$$

$$= 1.93 \text{ mA}$$

Since connected to ground,



$$V_o = iR = 1.93 \times 2.2 = 4.246 \text{ V} = V(o)$$

Case 2 :

$$A = V(o) = 5 \text{ V}$$

$$B = V(i) = 0 \text{ V}$$

 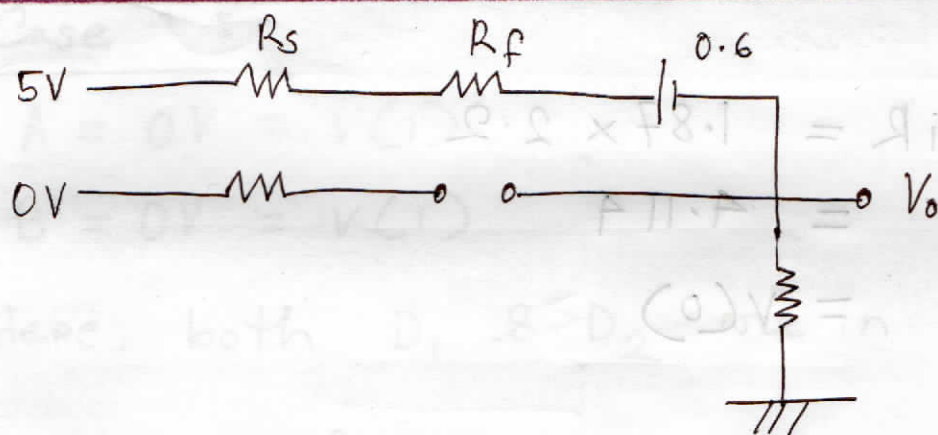Here,  $D_1$  is in forward bias and  $D_2$  in reverse bias.



Applying KVL,

$$-5 + iR_s + iR_f + 0.6 + iR = 0$$

$$\Rightarrow i(R_s + R_f + R) = 5 - 0.6$$

$$\Rightarrow i = \frac{5 - 0.6}{R_s + R_f + R}$$

$$= \frac{5 - 0.6}{100 + 50 + 2200}$$

$$\therefore i = 1.87 \text{ mA}$$



So,


$$\begin{aligned} V_o &= iR = 1.87 \times 2.2 \\ &= 4.114 \\ &= V(0) \end{aligned}$$

Case 3 :

$$A = V(1) = 0V$$

$$B = V(0) = 5V$$

$D_1$  is in Reverse bias &  $D_2$  is in Forward bias

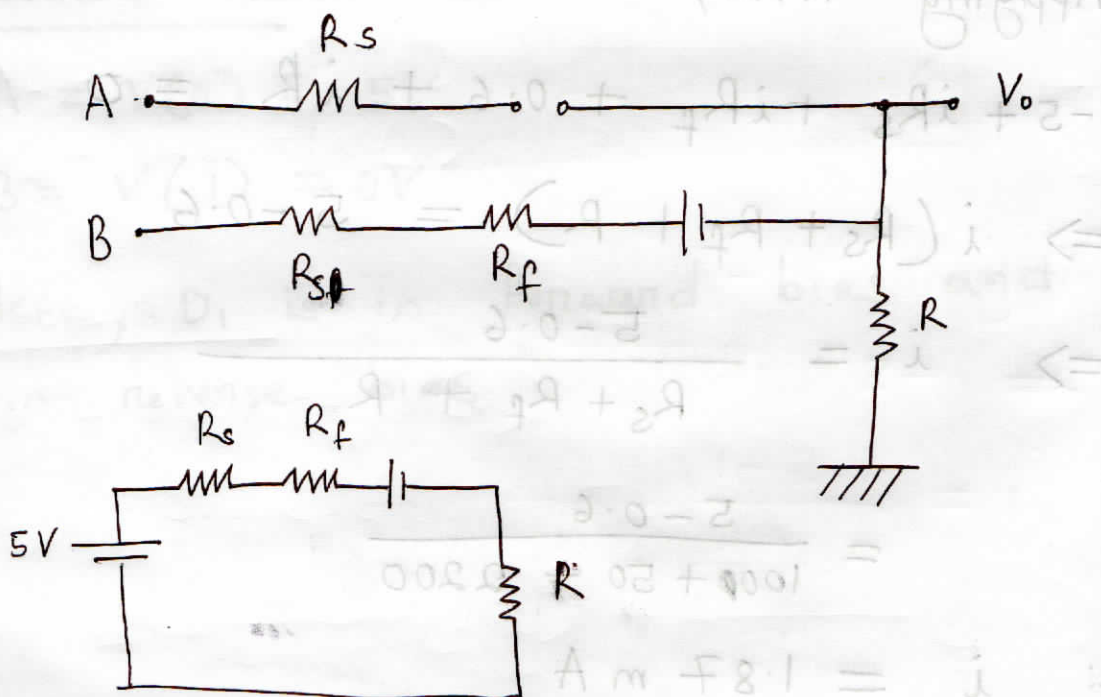


Case 1 :

$$A = 0V = V(1)$$


$$B = 0V = V(1)$$

 Here, both  $D_1$  &  $D_2$  are in reverse bias.



$$\therefore V_O = 0V = V(1)$$

## Transistorized NOT Gate

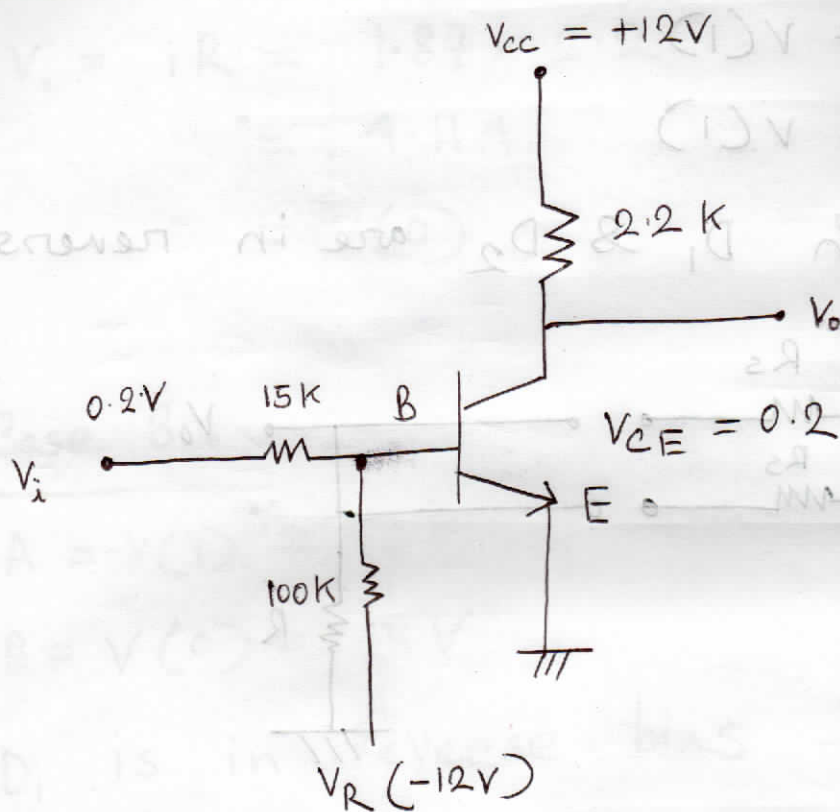

$V_i = \text{input}$   
 $V_o = \text{output}$

Positive Logic, so

$$V_L = 0.2V = V(0)$$

$$V_H = 12V = V(1)$$

Case 1 :

$$V_i = 0.2V = V(0)$$

Using Superposition Theorem,

$$V_B = \frac{15}{15+100}(-12) + \frac{100}{15+100}(0.2)$$

$$\therefore V_B = -1.391 \text{ V}$$

$$\text{As, } V_{BE} = -1.391 \text{ V} < 0.5 \text{ V}$$


which is the cut in voltage. So, the transistor will be in cut-off state.

$$\therefore V_o = 12 \text{ V} = V(1)$$

Thus, when  $V_i = V(0)$ ,  $V_o = V(1)$ .

Case 2 :

$$V_i = 12 \text{ V} = V(1)$$

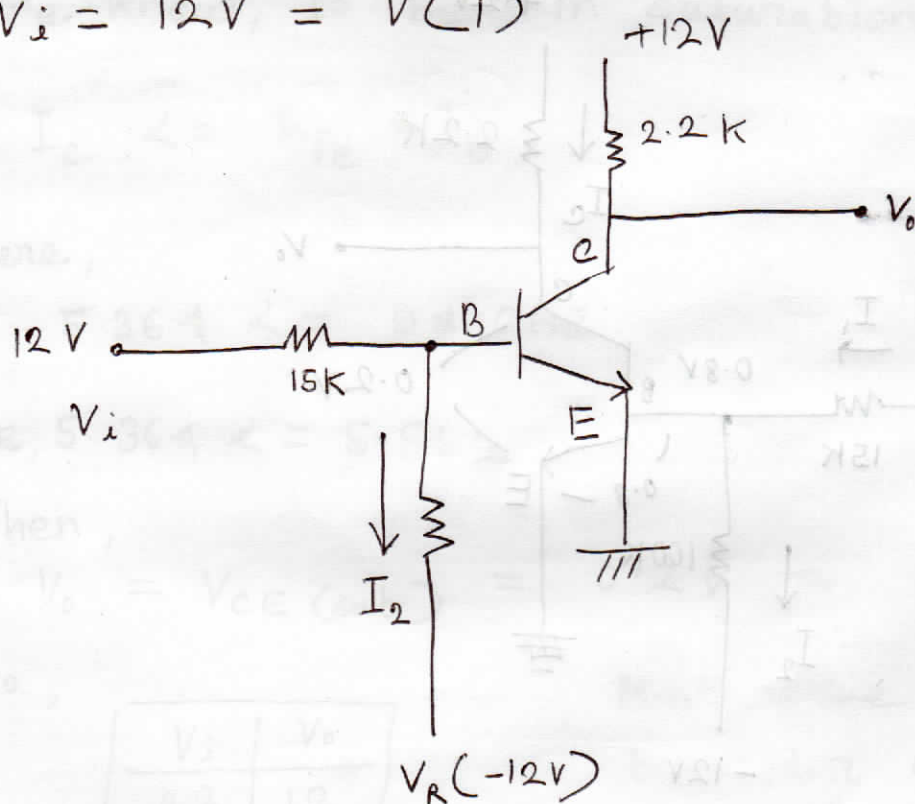



Let us assume that ~~the~~ the transistor is in saturation mode,


So,

$$V_{CE}(\text{sat}) = 0.2 \text{ V}, \quad V_{BE}(\text{sat}) = 0.8 \text{ V}$$

$$I_C \leq h_{fe} * I_B$$

$$\Rightarrow h_{fe} \geq \frac{I_C}{I_B}$$
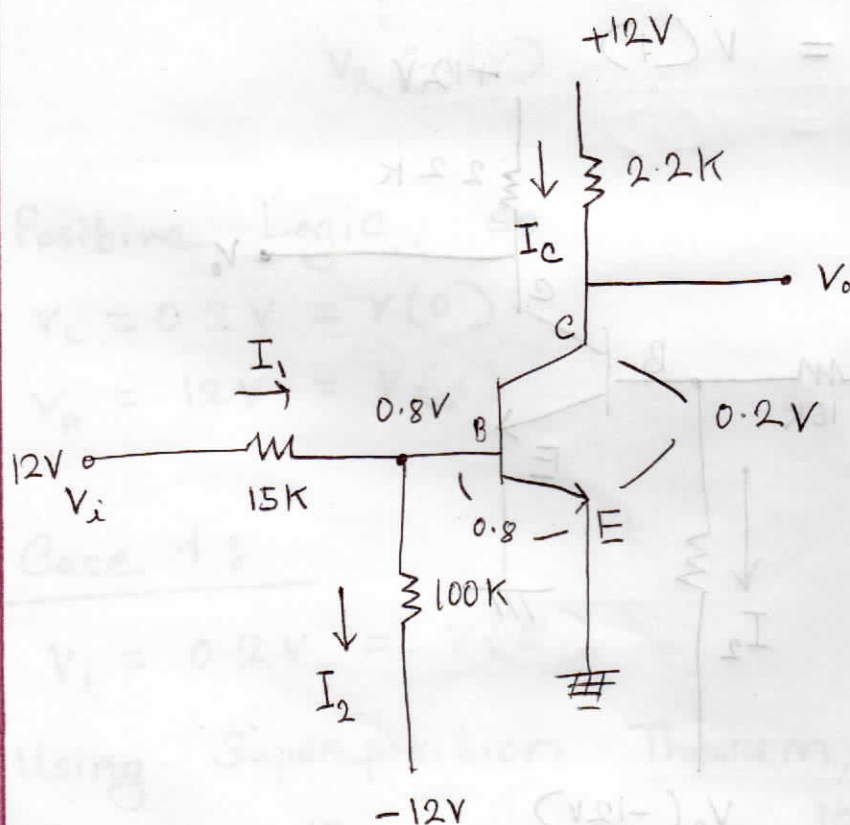
$$\therefore h_{fe}(\text{min}) = \frac{I_C}{I_B}$$



$$I_1 = \frac{12 - 0.8}{15K} = 0.746 \text{ mA}$$

$$I_2 = \frac{0.8 - (-12)}{100K} = 0.128 \text{ mA}$$

$$\therefore I_B = I_1 - I_2 = 0.618 \text{ mA}$$

$$I_C = \frac{12 - 0.2}{2.2} = 5.364 \text{ mA}$$

$$\therefore h_{fe}(\text{min}) = \frac{I_C}{I_B} = \frac{5.364}{0.618} = 8.66 \approx 9$$

we know, to be in saturation mode,

$$I_C \leq h_{fe} * I_B$$

here,

$$5.364 \leq 9 * 0.618$$

$$\text{ie, } 5.364 \leq 5.562$$

Then,


$$V_o = V_{CE}(\text{sat}) = 0.2 \text{ V} = V(0)$$

So,

$V_i$	$V_o$
0.2	12
12	0.2

Minm value for which transistor will be in saturation,  $h_{fe}(\text{min}) = 9$

# DTL Positive Logic NAND gate :

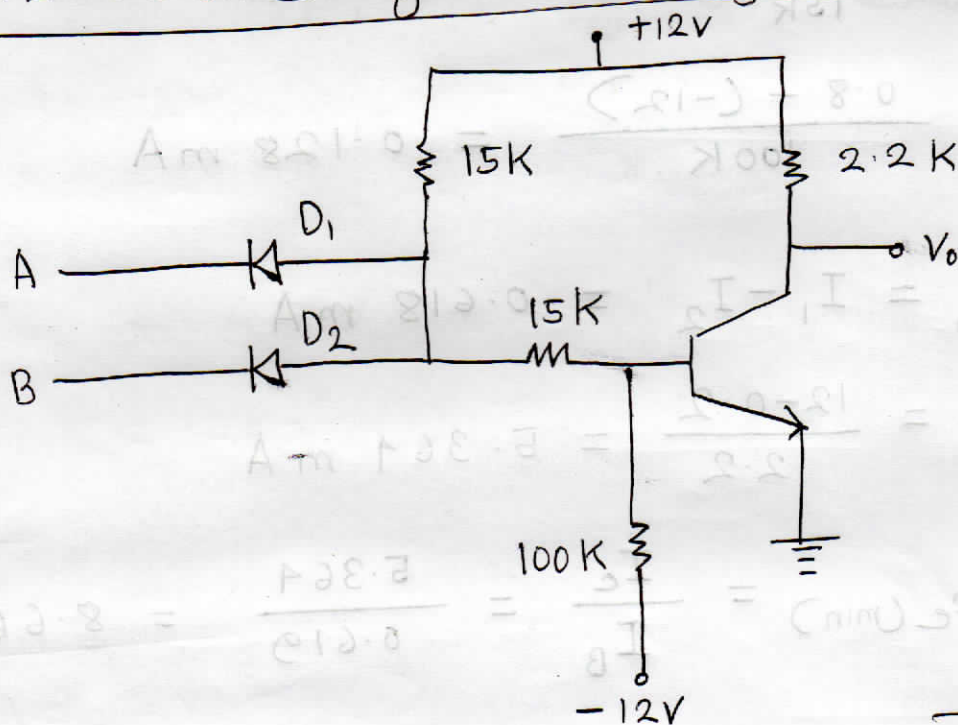

NAND

0	0	→ 1
0	1	→ 1
1	0	→ 1
1	1	→ 0

Case 1 :


$$A = 0.2V = V(0)$$

$$B = 12V = V(1)$$

So,  $D_1$  is in Forward Bias

$D_2$  is in Reverse Bias

V	V
0	0
0	0

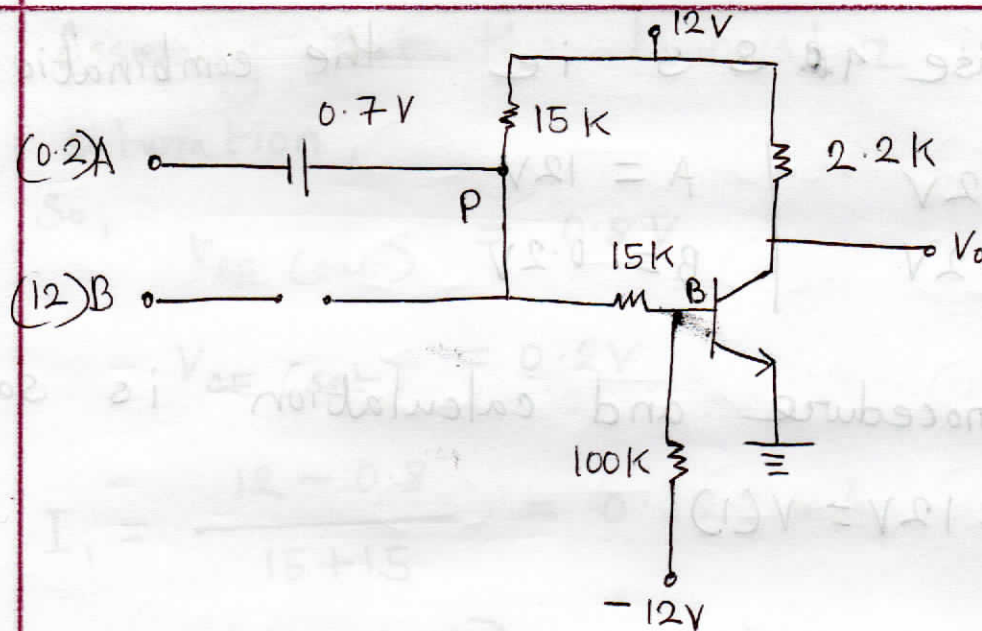

Here, Voltage at point P,  $V_P = 0.2 + 0.7$   
 $V_P = 0.9V$

Now, using Superposition,

$$V_B = \frac{100}{15+100} (0.9) + \frac{15}{15+100} (-12)$$

$$= -0.782V < 0.5V$$

which is the cut in voltage of transistor  
 So, transistor is in cut off mode.

$$\therefore V_o = 12V = V(1)$$



For case 1 & 3 i.e the combination,

$$A = 0.2V$$

$$B = 0.2V$$

$$A = 12V$$

$$B = 0.2V$$

DIY

The procedure and calculation is same.


$$\therefore V_0 = 12V = V(1)$$

Case 4 :

$$A = 12V = V(1)$$

$$B = 12V = V(1)$$

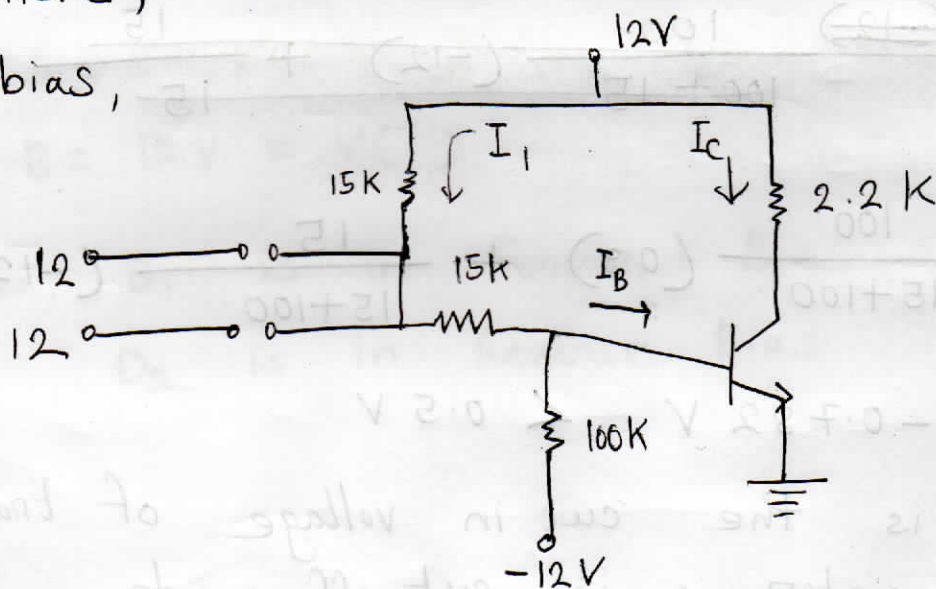Here, both  $D_1$  &  $D_2$  are in reverse bias,



Assuming that the transistor is in saturation,

$$\text{So, } V_{BE}(\text{sat}) = 0.8 \text{ V}$$

$$V_{CE}(\text{sat}) = 0.2 \text{ V}$$

$$I_1 = \frac{12 - 0.8}{15 + 15} = 0.373 \text{ mA}$$

$$I_2 = \frac{0.8 - (-12)}{100} = 0.128 \text{ mA}$$

$$I_B = I_1 - I_2 = 0.245 \text{ mA}$$

$$I_C = \frac{12 - 0.2}{2.2} = 5.3636 \text{ mA} \approx 5.364 \text{ mA}$$

$$h_{fe}(\text{min}) = \frac{I_C}{I_B} = \frac{5.364}{0.245} = 21.89 \approx 22$$

here,

$$I_C \leq h_{fe} * I_B$$

So, transistor will be in saturation mode.

$$\therefore V_o = 0.2 \text{ V} = V(0)$$

Min<sup>m</sup> value at which transistor will be in saturation is ~~22~~  $h_{fe}(\text{min}) = 22$

Thus,

$$V(0) \quad V(0) \rightarrow V(1)$$

$$V(0) \quad V(1) \rightarrow V(1)$$

$$V(1) \quad V(0) \rightarrow V(1)$$

$$V(1) \quad V(1) \rightarrow V(0)$$

The truth table is for NAND gate.  
So, proved.

Ques :

Prove that the previous ckt works like a -ve logic NOR gate.

Find the minimum value & mode of operation.