

Memory and Programmable Logic

Memory Device:

Device to which binary information is transferred for storage, and from which information is available for processing as needed.

Memory Unit:

is a collection of cells capable of storing a large quantity of binary information.

In digital systems, there are two types of memories:

1. RAM
2. ROM

Memory and Programmable Logic

1. *Random-Access Memory* (RAM)

RAM is the place in a computer where the operating system, application programs, and data in current use are kept so that they can be quickly reached by the computer's processor.

2. *Read-Only Memory* (ROM):

ROM is a type of memory that is as fast as RAM, but has two important differences: It can not be changed, and it retains its contents even when the computer is shut off. It is generally used to start your computer up and load the operating system.

Random-Access Memory

Memory unit:

Stores binary information in groups of bits called *words*.

Memory word:

group of 1's and 0's and may represent a number, character(s), instruction, or other binary-coded information.

Most computer memories use words that are multiples of 8 bits (*byte*).

32-bit word \rightarrow 4 bytes

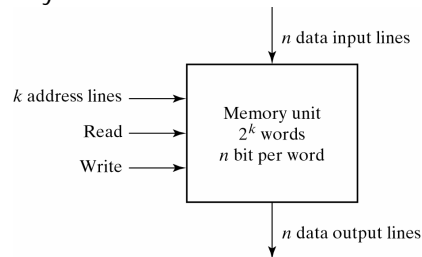


Fig. 7-2 Block Diagram of a Memory Unit

Random-Access Memory

Each word in memory is assigned an address 0 up to $2^k - 1$ ($k = \#$ of address lines).

Memory address		Memory content
Binary	decimal	memory content
000000000	0	1010101110001001
000000001	1	0000110101000110
000000010	2	\vdots
	\vdots	\vdots
111111101	1021	1001110100010100
111111110	1022	0000110100011110
111111111	1023	1101111000100101

Fig. 7-3 Content of a 1024×16 Memory

How many bytes is this memory module? 2KB

RAM: Write and Read Operations

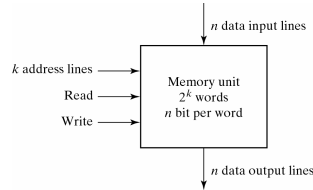


Fig. 7-2 Block Diagram of a Memory Unit

To transfer a new word to be stored into memory:

1. Apply the binary address of the word to address lines.
2. Apply the data bits that must be stored in memory to the data input lines.
3. Activate the *write* input.

To transfer a stored word out of memory:

1. Apply the binary address of the word to address lines.
2. Activate the *read* input.

Memory Types


Integrated circuit RAM units are available in two possible operating modes: *static* and *dynamic*.

Static RAM (SRAM) consists of internal latches that store the binary information. The stored information remains valid as long as power is applied to the unit.

Dynamic RAM (DRAM) stores the binary information in the form of electric charges on capacitors provided by the MOS transistors. The charge on the capacitors tends to decay with time and the capacitors must be periodically recharged by *refreshing* of the dynamic memory every few milliseconds.

- DRAM offers reduced power consumption, large integration of units on chip.
 - SRAM is faster; has shorter read and write cycles, SRAM is used in cache.
- Disadvantages: high power consumption, low density, expensive.

Memory Hierarchy

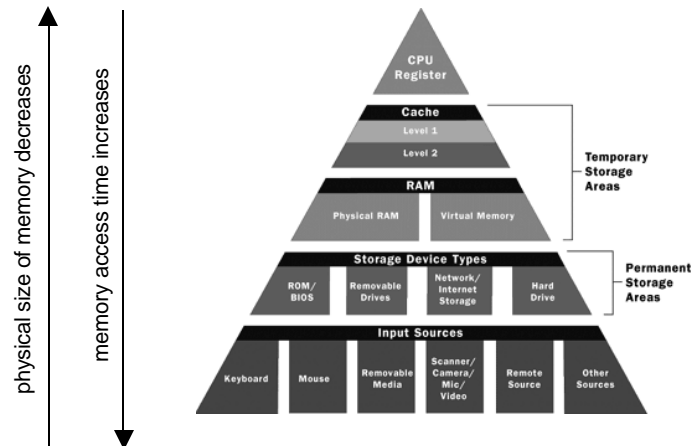

Volatile vs. Non-Volatile Memory

- RAM (static and dynamic) is said to be volatile, since information is lost when power is turned off.
 - Non-volatile memory retains its information even when power is turned off.
1. Magnetic disks: stored data is represented by the direction of magnetization.
 2. CD: compact disc is a piece of polycarbonate (a type of plastic) on which a spiral track has been impressed. This spiral track is a series of indentations ("pits") separated by flat areas ("land").
 3. ROM: The internal storage elements are set to their values once and after that are only read.

RAM Memory Cell

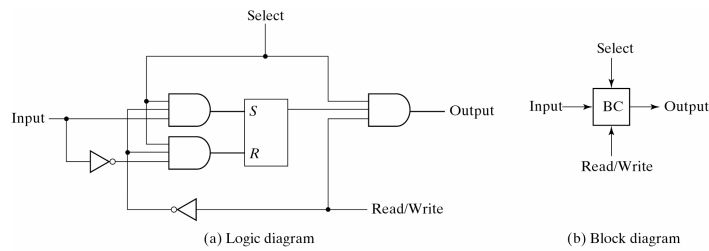


Fig. 7-5 Memory Cell

The storage part of the cell is modeled by an *SR* latch with associated gates.

A 1 in the read/write input provides the read operation by forming a path from the latch to the output.

A 0 in the read/write input provides the write operation by forming a path from the input to latch.

4 x 4 RAM

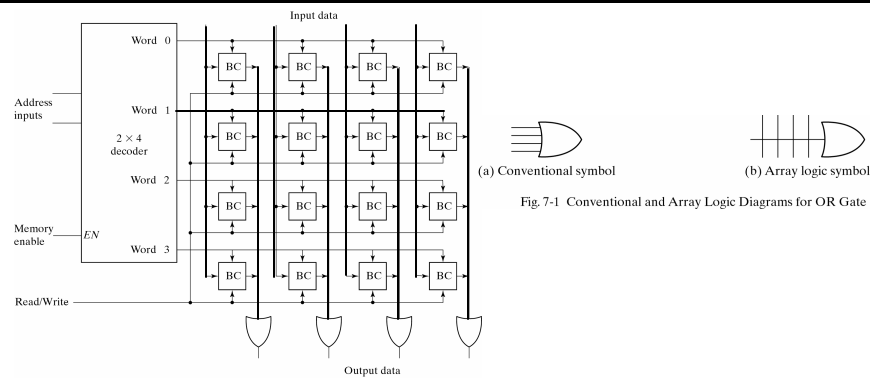


Fig. 7-6 Diagram of a 4×4 RAM

WRITE operation: the data available in the input lines are transferred into the four binary cells of the selected word. The memory cells that are not selected are disabled.

READ Operation: the four bits of the selected word go through OR gates to the output terminals.

Commercial RAM

Commercial RAM → thousands of words, with each word 1 - 64 bits.
A memory with 2^k words of n bits/word requires k address lines that go into a $k \times 2^k$ decoder.

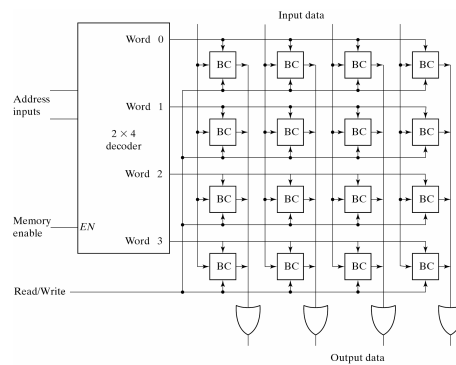


Fig. 7-6 Diagram of a 4×4 RAM

Two Dimensional Decoding

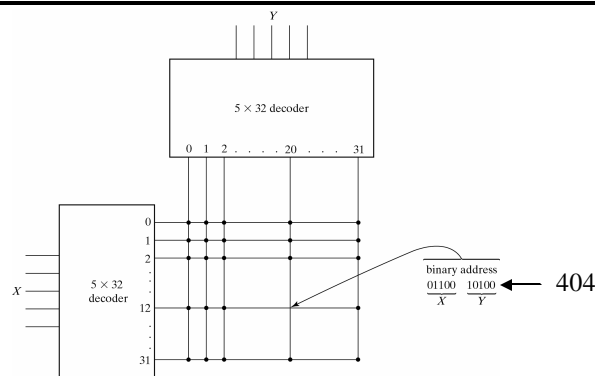


Fig. 7-7 Two-Dimensional Decoding Structure for a 1K-Word Memory


The idea of two-dimensional decoding is to arrange the memory cells in an array that is as close as possible to square. Use two $k/2$ -input decoders instead of one k -input decoder. One decoder performs the row selection and the other the column selection in a two dimensional matrix configuration.
How many words can be selected?

Constructing 256K X 8 RAM (similar to 7-8)

1. How many 64K x 8 RAM chips are needed to provide a memory capacity of 256KB?
2. How many lines of the address must be used to access 256K bytes? How many of these lines are connected to the address inputs of all chips?
3. How many lines must be decoded for the chip select inputs of all chips?

64K X 8 RAM chip


Capacity: 64K words of 8 bits each

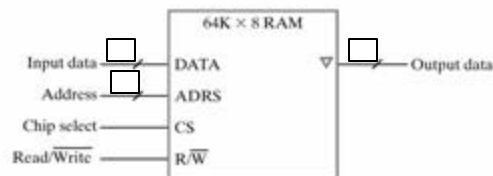

How many chips are needed to construct 256K x 8?
What is the size of the decoder?

256K X 8 RAM

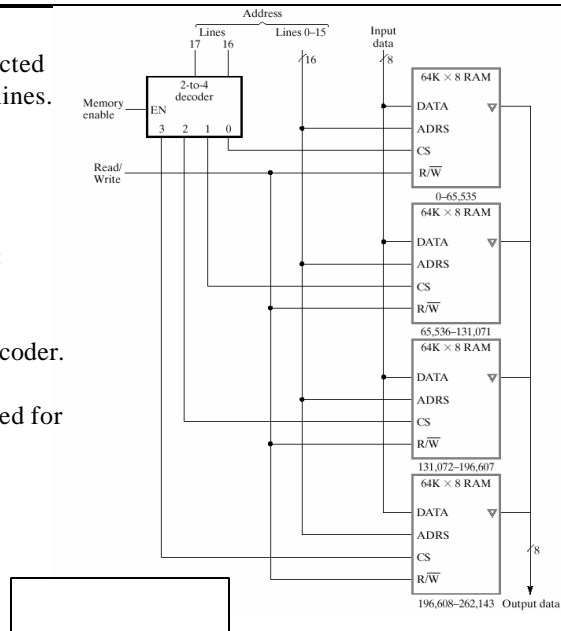- Three-state outputs are connected together to form 8 data output lines.
- Just one chip select (CS) will be active at any time.
- RAM requires 18-bit address:
16 LSB address are applied to the inputs of each RAM.
2 MSB are applied to 2-to-4 decoder.
- Address bits 16 and 17 are used for chip selection.



32 X 8 ROM chip

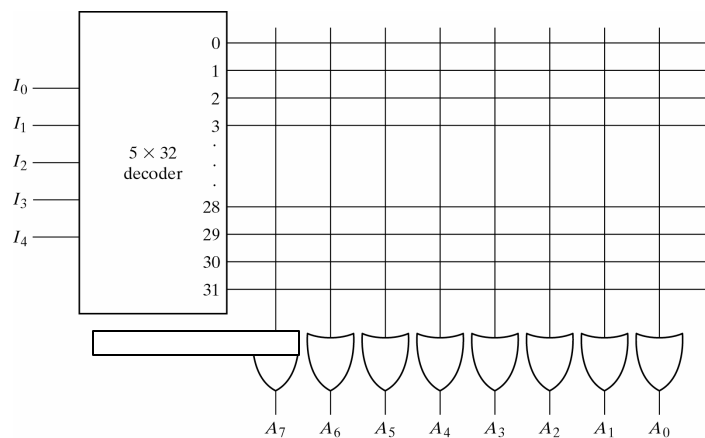


Fig. 7-10 Internal Logic of a 32×8 ROM