
 
 


CSE2209: Digital Electronics and Pulse Techniques



Course Conducted By:

Nowshin Nawar Arony
Lecturer, Dept of CSE, AUST

NPN Transistor

 


  NPN Transistor Reverse Active Mode ($h_{fe} < 1$)




$$I_C = h_{fe} * I_B \quad \text{or} \quad I_B = \frac{I_C}{h_{fe}}$$

 Collector becomes emitter and emitter becomes collector




BE	BC	Transistor State
$(V_{BE} < 0.7V) \text{ R}$	$(V_{BC} < 0.7V) \text{ R}$	Cut off $I_C = I_B = I_E = 0$
$(V_{BE} > 0.7V) \text{ F}$	$(V_{BC} < 0.7V) \text{ R}$	Active $I_C = h_{fe} * I_B$
$(V_{BE} < 0.7V) \text{ R}$	$(V_{BC} > 0.7V) \text{ F}$	Inverse active $I_C = h_{fe} * I_B$
$(V_{BE} > 0.7V) \text{ F}$	$(V_{BC} > 0.7V) \text{ F}$	Saturation $I_C \leq h_{fe} * I_B$ $V_{CE}(\text{sat}) = 0.2V$ $V_{BE}(\text{sat}) = 0.8V$

TTL NAND Gate

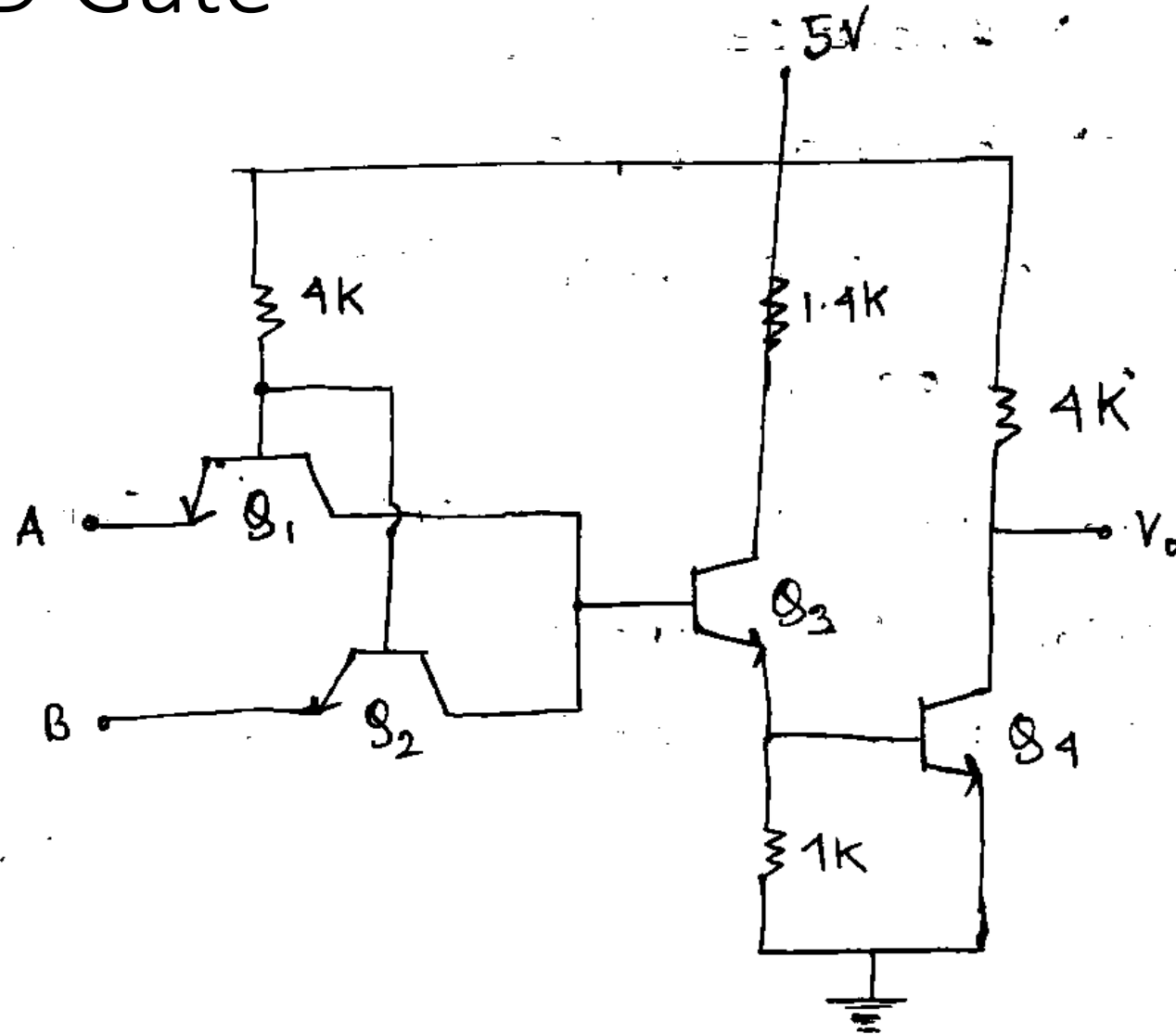


TTL NAND Equivalent Circuit

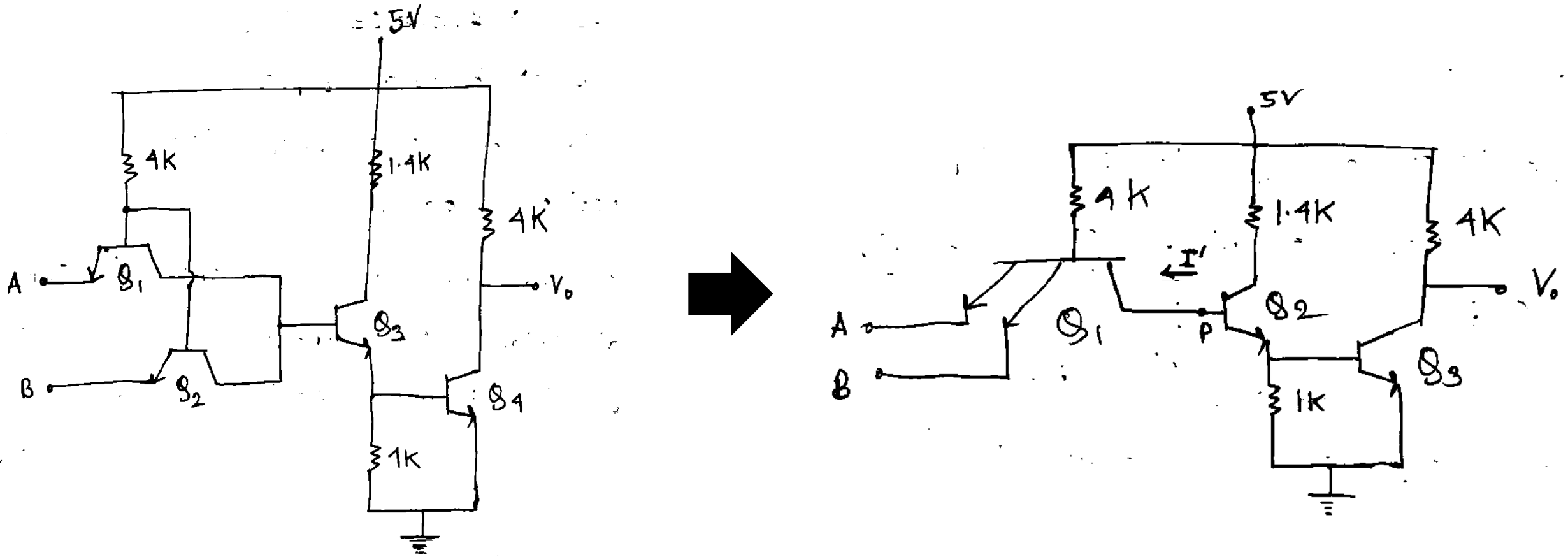


Clamping Diodes

PG - 147

 


Input Clamping Diodes

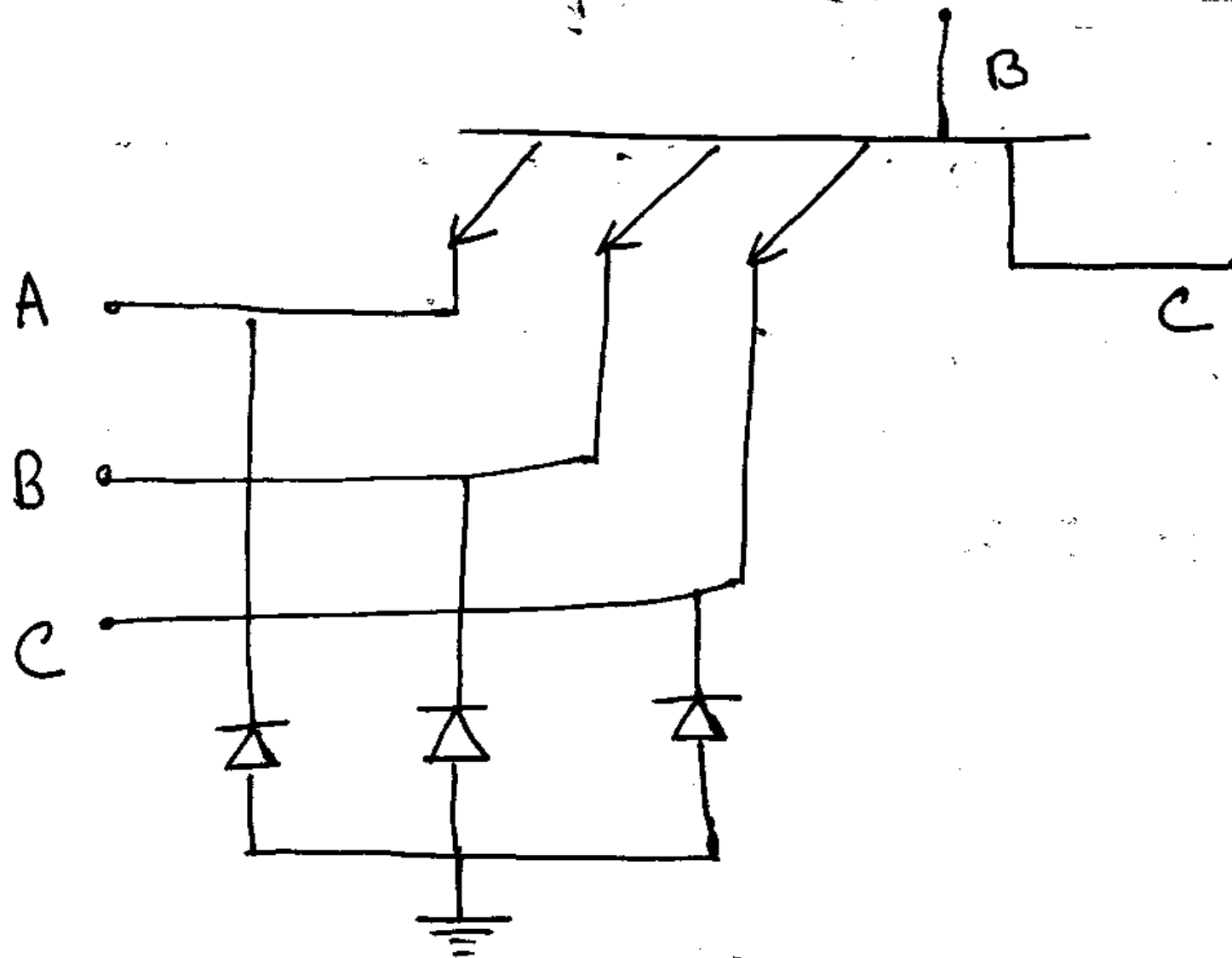
These diodes (shown in the shaded block in Fig. 5-21) are often included from each input to ground, with the anode grounded. These diodes are effectively out of the circuit for positive input signals, but they limit negative voltage excursions at the input to a safe value. These negative signals may arise from ringing caused by lead inductance resonating with shunt capacitance.



Passive Pull Up Circuit

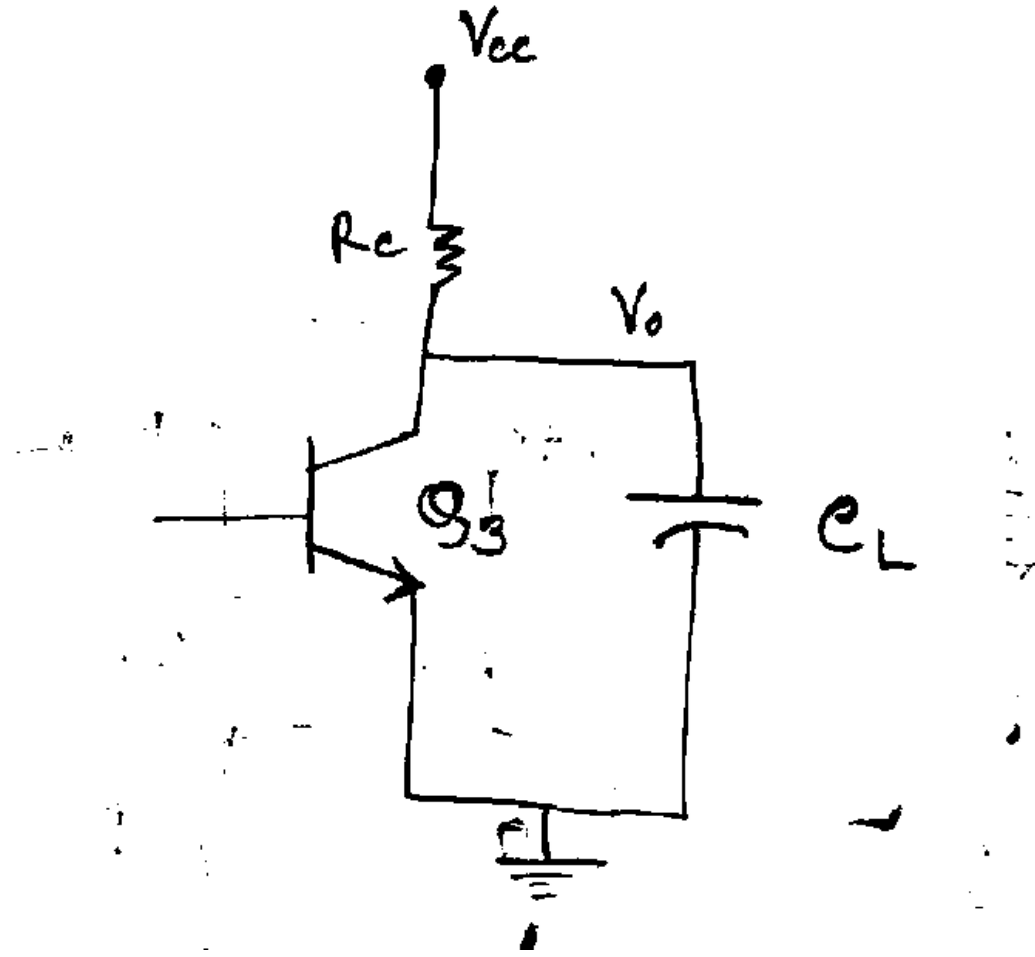


Wired End (Totem Pole)

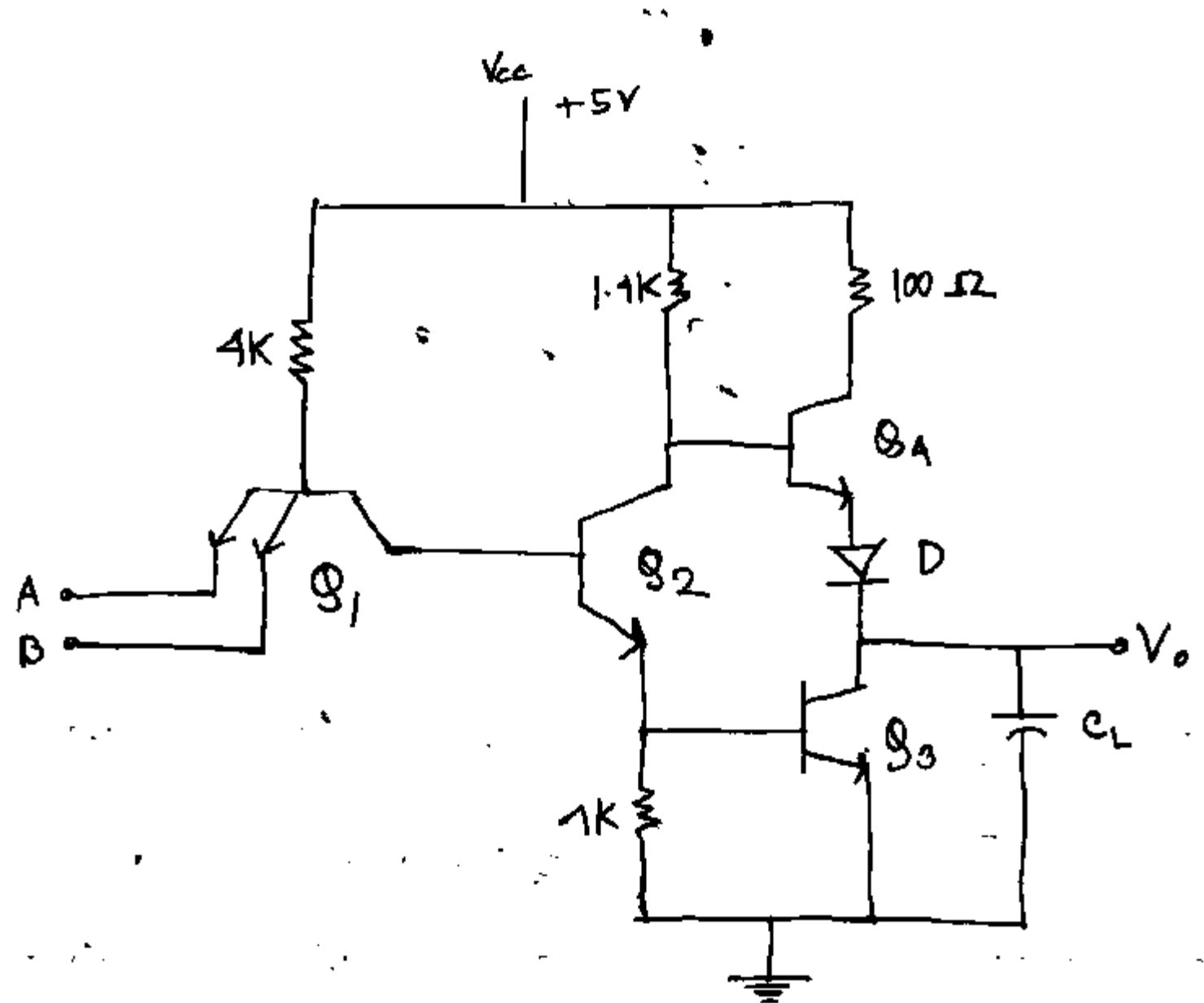


Resistor-Transistor Logic (RTL) NOR Gate (Positive Logic)

Pg. 152-153
(5.13)

 

Direct-coupled Transistor Logic (DCTL) NOR Gate (Positive Logic)

Pg. 152-155
(5.13)

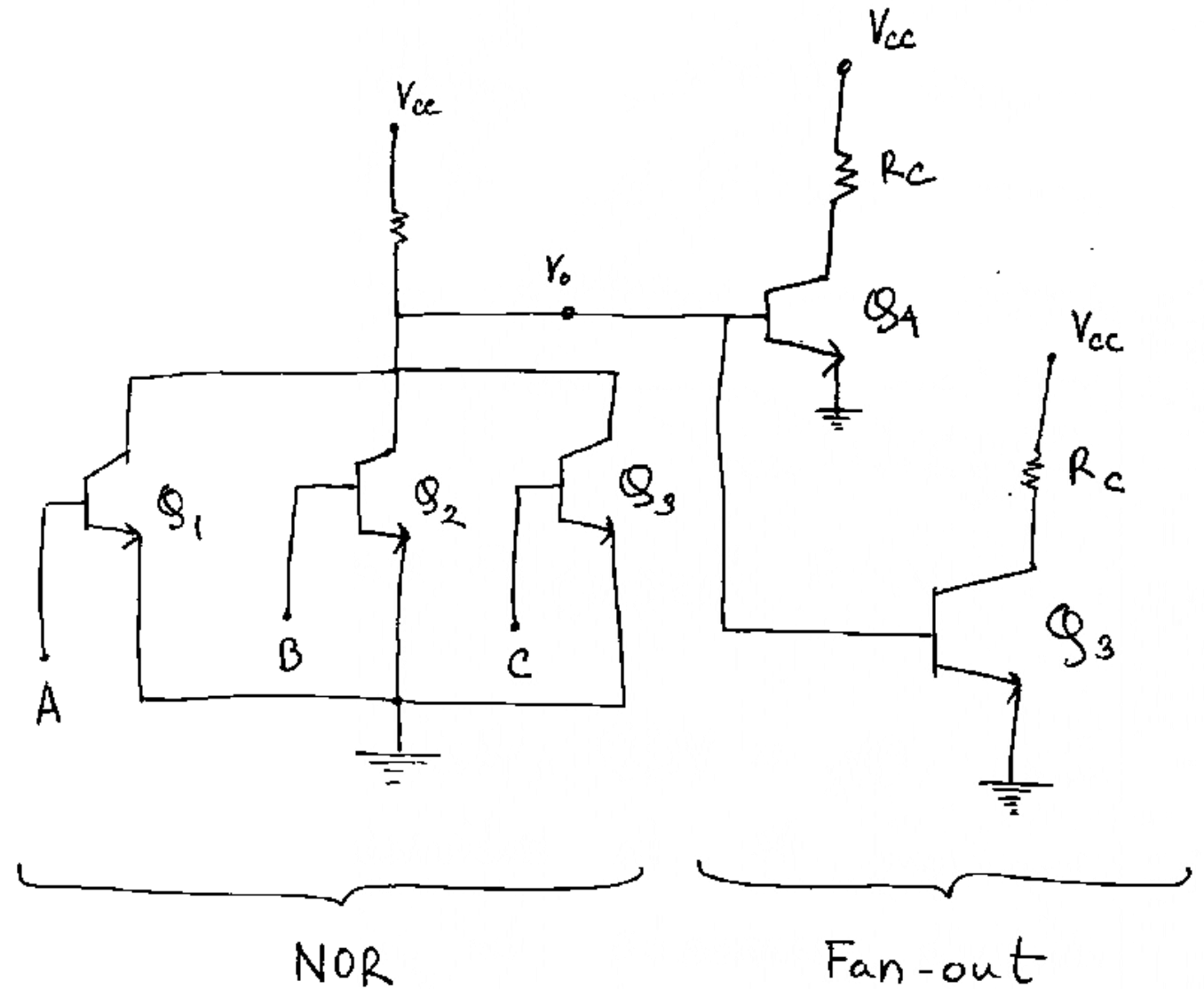

DCTL

- Direct coupled transistor logic means inputs are directly coupled to the base of the transistor.
- DCTL circuits have fast switching speed.

Self Study:

- Advantages and Disadvantages of DCTL. (Pg. 154-155)