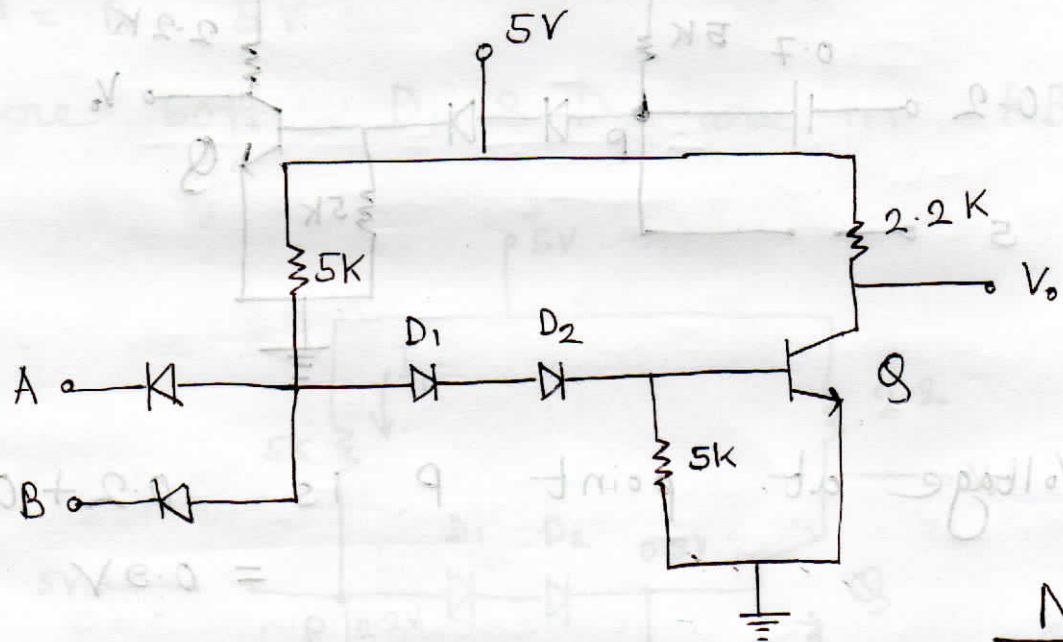


Integrated ckt DTL NAND gate : (positive logic)



NAND

Case 1 :

$$A = B = 0.2V = V(0)$$

For case 2 & 3,

$$A = 0.2V = V(0), B = 5V = V(1)$$

$$\text{or, } A = 5V = V(1), B = 0.2V = V(0)$$


Let us do it for,

$$A = 0.2V \text{ and } B = 5V$$

So here diode across A input will be forward bias and B input will be reverse bias.

| A | B | V _o |
|-----|-----|----------------|
| 0.2 | 0.2 | 0.2 |
| 0.2 | 5 | 5 |
| 5 | 0.2 | 5 |
| 5 | 5 | 0.2 |

So,

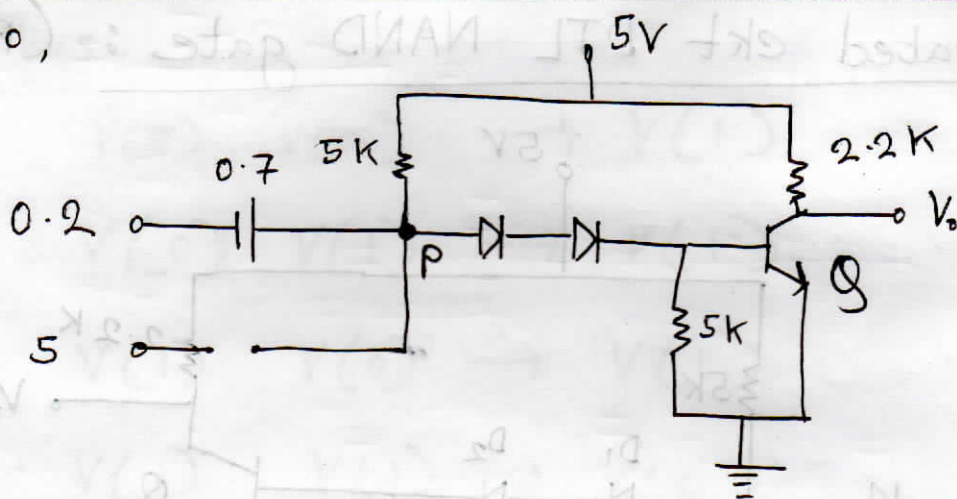

Voltage at point P is $0.2 + 0.7 = 0.9V$

Minimum amount of voltage required at P to turn ON D_1 and D_2 is $0.6 + 0.6 = 1.2V$


And, along with that to turn on Q we need $0.5V$. So at P we need total $(0.6 + 0.6 + 0.5) = 1.7V$.

As, $V_{P(\text{actual})} = 0.9V$ is not sufficient enough to turn on D_1 , D_2 and transistor Q. So, $V_0 = 5V = V(1)$

Case 2 :

$$A = B = 5V$$

Here both D_1 & D_2 are in RB.

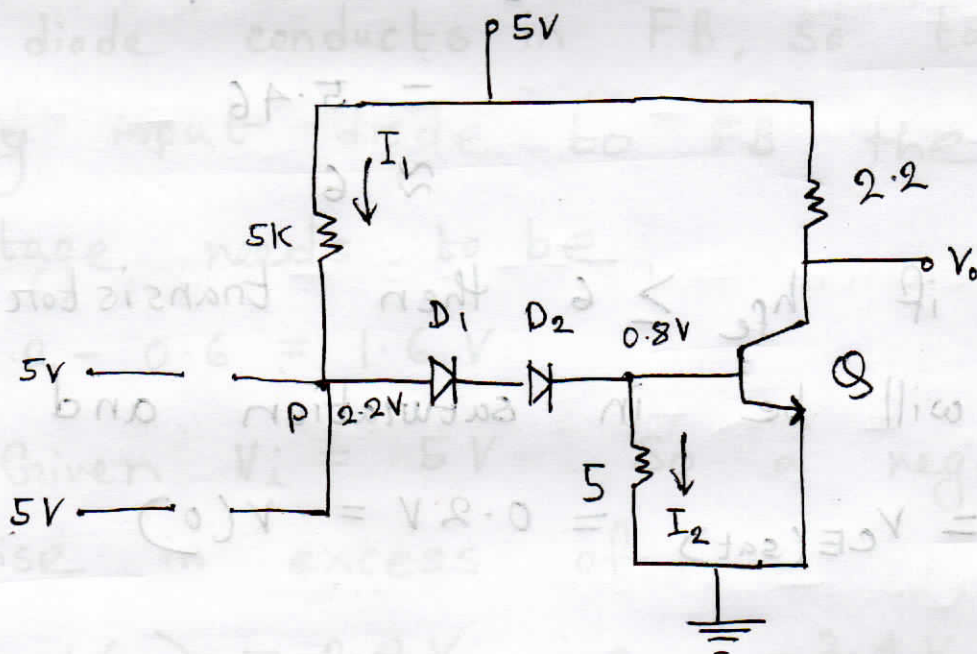

Assuming that transistor Q is in saturation, Voltage at p,

$$V_p = 0.8 + 0.7 + 0.7 = 2.2V$$

$$I_1 = \frac{5 - 2.2}{5} = 0.56 \text{ mA}$$

$$I_2 = \frac{0.8}{5} = 0.16 \text{ mA}$$

$$\therefore I_B = I_1 - I_2 = 0.56 - 0.16 = 0.4 \text{ mA}$$

$$I_c = \frac{5 - 0.2}{2.2} = 2.182 \text{ mA}$$

$$\therefore h_{fe}(\text{min}) = \frac{I_c}{I_B} = \frac{2.182}{0.4}$$

$$= 5.46$$

$$\approx 6$$

So, if $h_{fe} \geq 6$ then transistor Q will be in saturation and

$$V_o = V_{CE}(\text{sat}) = 0.2 \text{ V} = V(0)$$

Noise Margin :

For the circuit of DTL NAND gate. Find $NM(0)$ & $NM(1)$.

$NM(0)$:

For $V_i = 5 \text{ V}$, output $V_o = 0.2 \text{ V}$

$V(0) = 0.2 \text{ V}$

Then,

$$V_p = 0.2 + 0.7 - 0.8 + 0.7 + 0.7 = 2.2 \text{ V}$$

All input diodes are in reverse bias.

A diode conducts in FB, so to take any input diode to FB the input voltage needs to be,


$$2.2 - 0.6 = 1.6 \text{ V}$$

\therefore Given $V_i = 5 \text{ V}$. So a negative noise in excess of

$$(5 - 1.6) = 3.4 \text{ V i.e. } -3.4 \text{ V}$$

must be present at input before

 ckt malfunctions. $\therefore NM(0) = -3.4 \text{ V}$



NM(1) :

As $\exists V_i = 0.2$ then $V_o = 5V = V(1)$

$$V_P(\text{actual}) = \cancel{0.9V} 0.2 + 0.7 = 0.9V$$


$$V_P(\text{required}) = 0.5 + 0.6 + 0.6 = 1.7V$$

$$\text{Difference} = 1.7 - 0.9 = 0.8V$$

$$\therefore V_i = 0.2 + 0.8 = 1V$$

$$NM(1) = +0.8V$$

Fan-out

 

$$I_o = \frac{5 - 0.9}{5} = 0.82 \text{ mA}$$

We know, from case 2,

$$I_B = 0.4 \text{ mA} \text{ and } I_C = 2.18 \text{ mA}$$

Let us consider, $h_{fe} = 30$

Then,

$$h_{fe} * I_B = 30 \times 0.4 = 12 \text{ mA}$$

So,

$$N * I + I_C < h_{fe} * I_B$$

$$\text{or, } N < \frac{h_{fe} * I_B - I_C}{I}$$

$$\text{or, } N < \frac{12 - 2.182}{0.82}$$

$$\therefore N < 11.97$$

$$\text{So, } N_{(\text{max})} = 11$$

Power Dissipation :

$$P_{avg} = \frac{P(0) + P(1)}{2}$$

$P(0)$ = Power dissipation when $V_o = V(0)$

$P(1)$ = Power dissipation when $V_o = V(1)$

$$P(0) = V \cdot I(0) \quad \text{and} \quad P(1) = V \cdot I(1)$$

When the ckt is in saturation mode,

$$I(0) = I_1 + I_c = 0.56 + 2.182 = 2.742 \text{ mA}$$

When in ~~sat~~ cut off,


$$I(1) = \frac{5 - 0.9}{5} = 0.82 \text{ mA}$$

The highest voltage in a ckt is fixed & here $V = 5V$

$$\begin{aligned} P_{avg} &= \frac{5(2.742 + 0.82)}{2} \\ &= 8.905 \text{ mW} \end{aligned}$$

D17

DTL NAND Gate

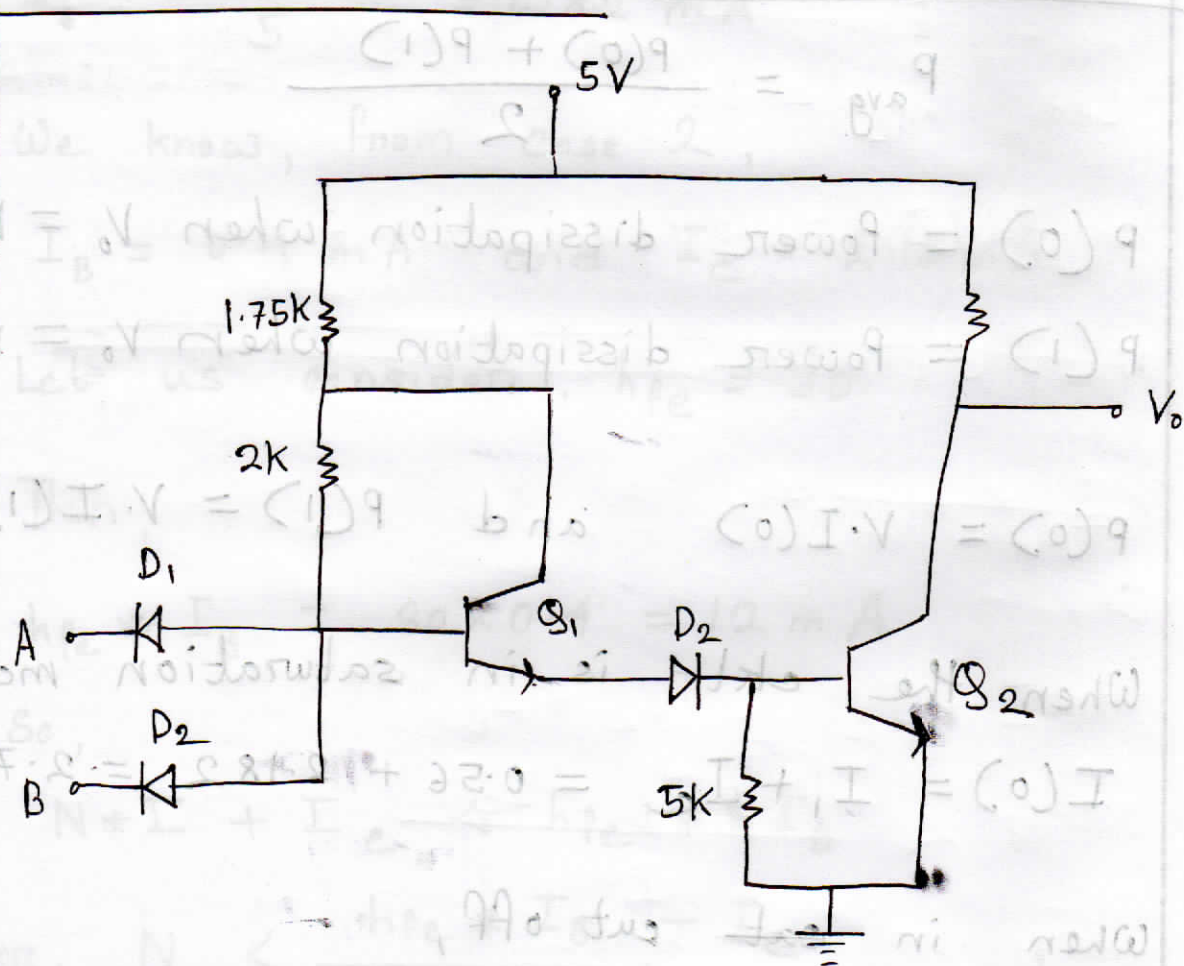

* Operations :

— case 1

— case 2

* Fan-in

* $NM(0) / NM(1)$

* Fan-out

* Power Dissipation