

Digital System Design

Lecture – 6

Memory Device (ROM and PLA)

Memory Device

- Device to which binary information is transferred for storage
- And from which information is available for processing as needed

Memory Unit

- A collection of cells capable of storing a large quantity of binary information

Types of Memories

In digital systems, there are two types of memories:

1. RAM
2. ROM

ROM (Read Only Memory)

- Non-volatile
- Retains its contents even when the computer is shut off
- Generally used to start the computer up and load the operating system
- **A memory device in which a fixed set of binary information is stored**
- **The binary information must first be specified by the user**
- **Then embedded in the unit to form the required interconnection pattern**

ROM (Contd.)

- Includes both the decoder and the OR gates within a single IC package
- Particular function implementation is done by “**programming**”
- Very often used to implement complex combinational circuit in one IC package
- Thus eliminates all interconnecting wires
- Once a pattern is established, it remains fixed even when the power goes off
- **ROM has special internal links that can be fused or broken**

ROM Structure (Contd.)

- Consists of **n input lines** and **m output lines**
- **2^n distinct addresses** possible with **n inputs**
- Each bit combination of the input variables called as **address**
- Each bit combination coming out of the output lines known as **word**
- Number of **bits per word** = number of output lines **m**
- So, **a word equals m bits**
- An output word can be selected by a unique address
- A ROM is defined by number of words (**2^n**) and the number of bits (**m**) per word.
- **$2^n \times m$**


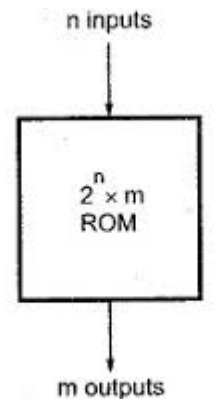


Fig. 3.82 Block diagram of ROM

An Example of a ROM

- Consider a 32×8 ROM i.e, **256-bit ROM**
- The unit consists of 32 words of 8 bits each
- Here $32=2^5$, means 5 input lines
- Input 00000 means word number 0 will be selected
- Input 11111 means word number 31 will be selected
- **Design a 2048-bit ROM having word size 8 bits each?**
- **Design a 2048-bit ROM having word size 4 bits each?**

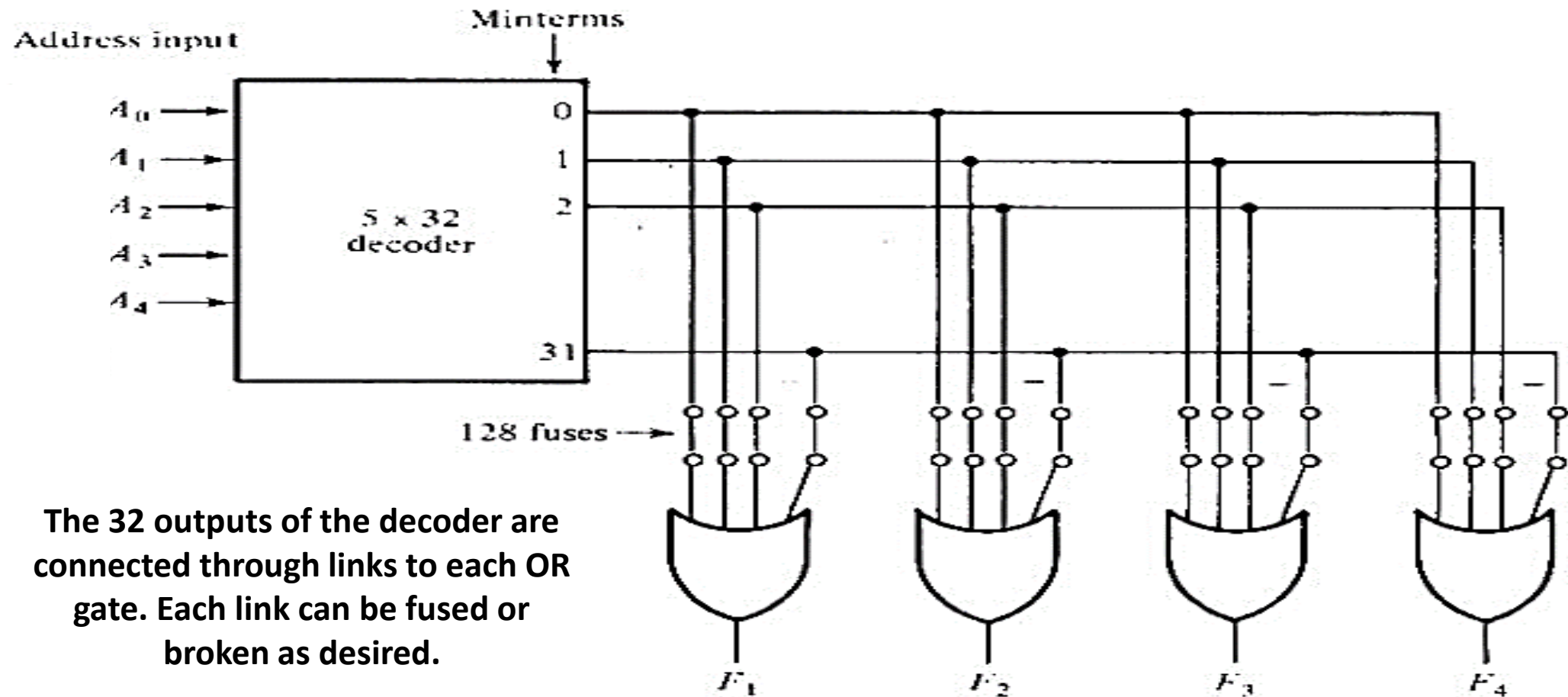Internal Logic Construction of a 32 X 4 ROM



Combinational Logic Implementation Using ROM

For an n -input, m -output combinational circuit, we need a $2^n \times m$ ROM

$$F_1(A_1, A_0) = \Sigma(1, 2, 3)$$

$$F_2(A_1, A_0) = \Sigma(0, 2)$$


When a combinational circuit is implemented using ROM, the functions must be expressed in sum of minterms or by a truth table.

The truth table gives all the information for programming a ROM.

A_1	A_0	F_1	F_2
0	0	0	1
0	1	1	0
1	0	1	1
1	1	1	0

(a) Truth table

ROM with AND-OR Gates

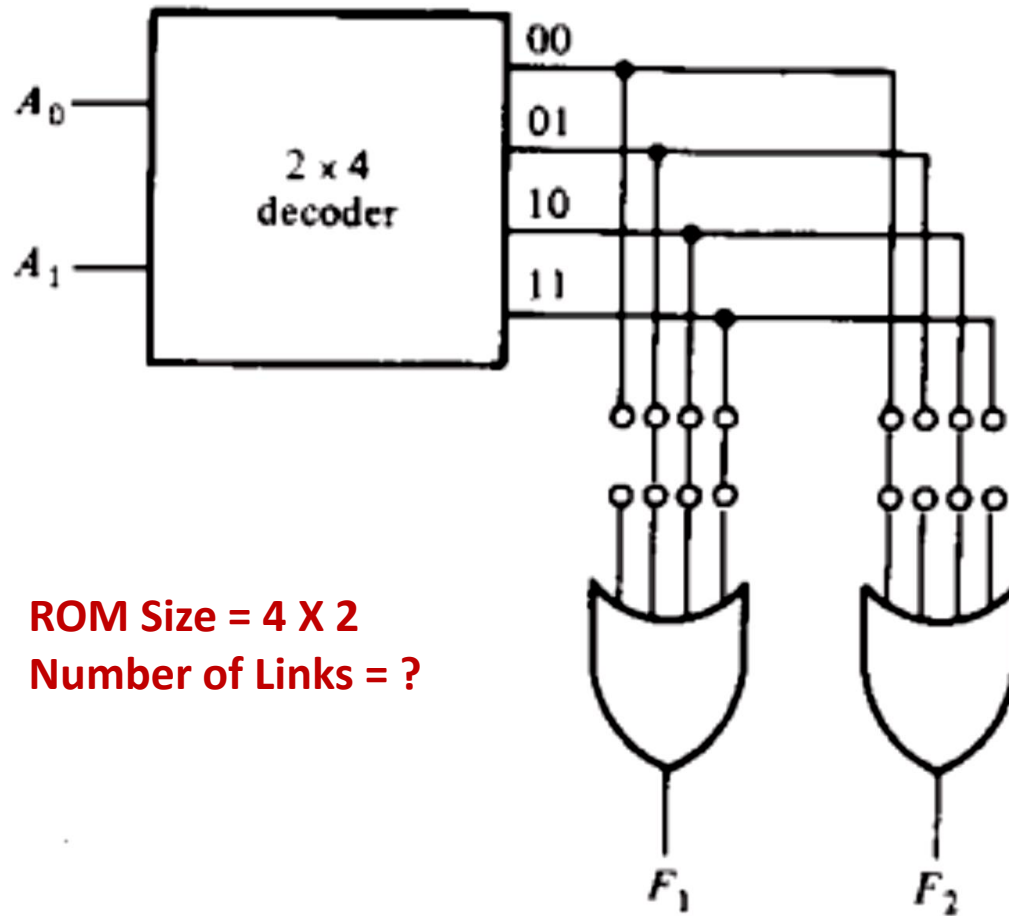


ROM Size = 4 X 2
Number of Links = ?

(b) ROM with AND-OR Gates

A_1	A_0	F_1	F_2
0	0	0	1
0	1	1	0
1	0	1	1
1	1	1	0

(a) Truth table

ROM with AND-OR-Invert Gates

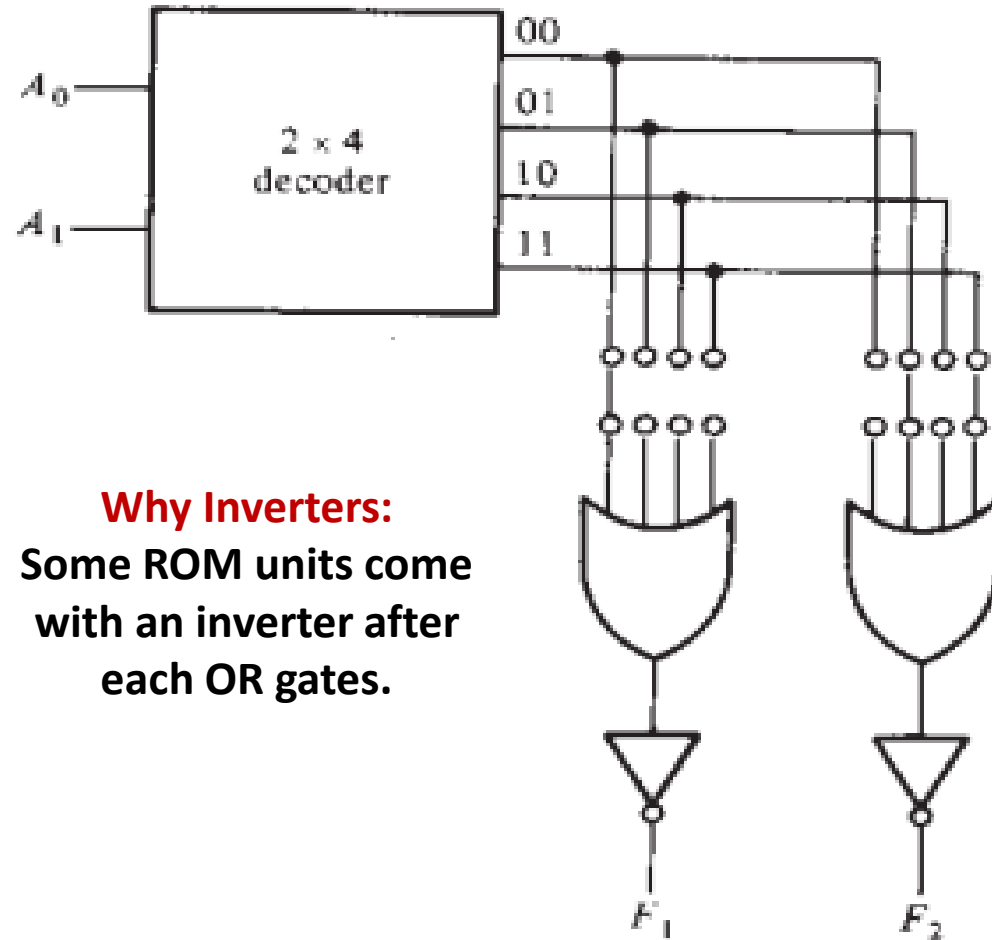

Why Inverters:
Some ROM units come with an inverter after each OR gates.

(c) ROM with AND-OR-Invert Gates

A_1	A_0	F_1	F_2
0	0	0	1
0	1	1	0
1	0	1	1
1	1	1	0

(a) Truth table


Example

Design a combinational circuit using a ROM. The circuit accepts a 3 bit number and generates an output binary number equal to the square of the input number.

TABLE 5-5
Truth Table for Circuit of Example 5-3

Inputs			Outputs						Decimal
A_2	A_1	A_0	B_5	B_4	B_3	B_2	B_1	B_0	
0	0	0	0	0	0	0	0	0	0
0	0	1	0	0	0	0	0	1	1
0	1	0	0	0	0	1	0	0	4
0	1	1	0	0	1	0	0	1	9
1	0	0	0	1	0	0	0	0	16
1	0	1	0	1	1	0	0	1	25
1	1	0	1	0	0	1	0	0	36
1	1	1	1	1	0	0	0	1	49

Example (Contd.)

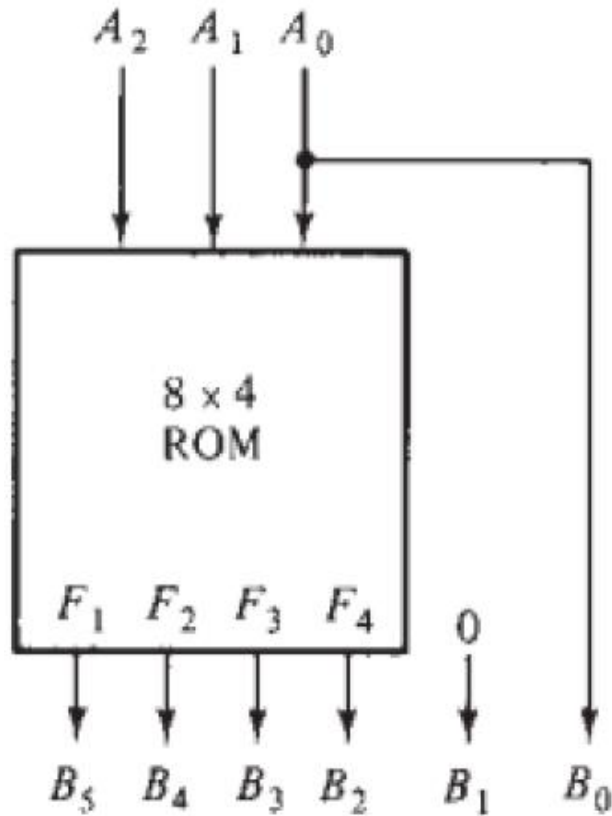

(a) Block diagram

A_2	A_1	A_0	F_1	F_2	F_3	F_4
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	0	0	0	1
0	1	1	0	0	1	0
1	0	0	0	1	0	0
1	0	1	0	1	1	0
1	1	0	1	0	0	1
1	1	1	1	1	0	0

(b) ROM truth table

**The three inputs specify
eight words of 4-bits
each.**

Types of ROMs

ROMs may be programmed in two ways:

- mask programming
- programmable read only memory (PROM)

Mask Programming:

- Done by the manufacturer during the last fabrication process of the unit.
- The manufacturer makes the mask for the paths to produce 1's or 0's according to the customers truth table.
- It is economical only if large quantities of the same ROM configuration are to be manufactured.

Types of ROMs (Contd.)

PROM (Programmable Read-Only Memory):

- Economical for small quantities of ROMs
- The links in PROM are broken as per application
- User can use his own laboratory to achieve the desired relationship between input address and stored words
- Special units called **PROM programmers** are available commercially to facilitate the procedure
- **PROM is a hardware procedure.**
- So, **hardware procedure for ROM or PROM is irreversible**
- Once programmed, permanent fixed pattern and cannot be altered
- Unit must be discarded if the bit pattern is to be changed

Types of ROMs (Contd.)

ERASABLE PROM (EPROM):

- Can be restructured to the initial value even though it has been changed previously
- When placed under a special ultraviolet light for a given period time, the short wave radiation discharges the internal gates that serve as constant
- After erasure, the ROM returns to its initial state and can be reprogrammed
- Some ROMs can be erased with electrical signal instead of ultraviolet light which are called **Electrically Alterable ROMs (EAROMs)**

Why it is called Read-Only Memory?

- **Memory** Designates a storage unit
- **Read** signifies the contents of a word specified by an address in a storage unit which is placed at the output terminals
- So, a **memory unit** with a fixed word pattern that can be **read out** upon application of a given address
- The bit pattern in the ROM is permanent and cannot be changed during **normal operation**


Usage of ROM

- To implement complex combinational circuits from truth tables
- Converting from one binary code to another (e.g., ASCII to EBCDIC and vice versa)
- For arithmetic functions such as multipliers
- For displaying characters in a cathode-ray tube
- For applications which require a large number of inputs and outputs
- In the design of control units of digital systems
- A control unit that utilizes a ROM to store binary control information is called a **microprogrammed control unit**

Programmable Logic Array (PLA)


- **Programmable Logic Array(PLA) is a fixed architecture logic device with programmable AND gates followed by programmable OR gates.**
- More economical to use when the **don't care conditions are excessive**
- Similar to ROM, but does not provide full decoding i.e., **does not generate all the minterms**
- The **decoder is replaced by a group of AND gates**, where each can be programmed to generate a product term of the input variables
- The **AND and OR gates** inside the PLA has **links** among them
- Functions are implemented in sum of products form by opening appropriate links and leaving the desired connections

Programmable Logic Array (Contd.)

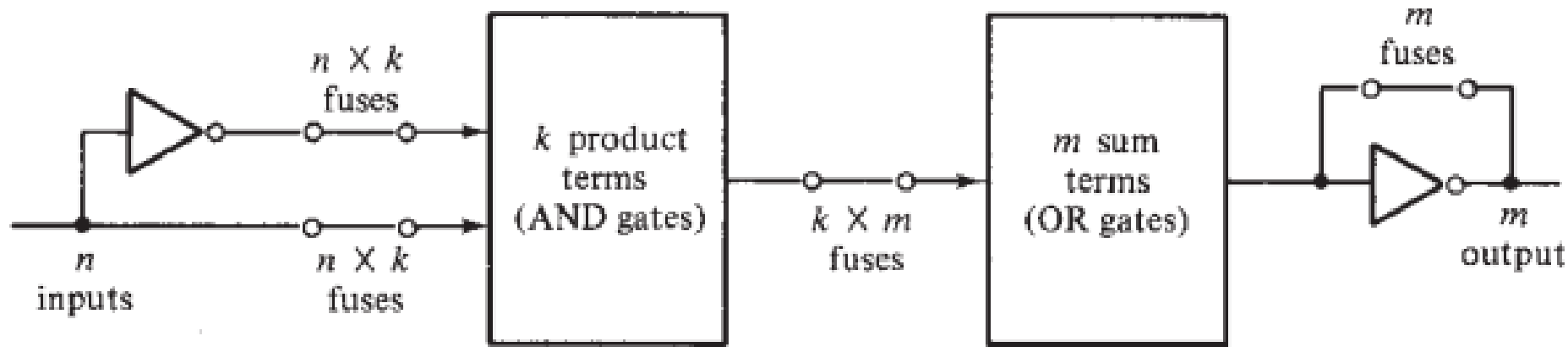

- n inputs, m outputs, k product terms, m sum terms
- Product terms constitute a group of k AND gates
- Sum terms constitute a group of m OR gates
- **The size of a PLA = $n \times m \times k$**
- A typical PLA contains 16 inputs, 48 product terms and 8 outputs
- **Number of programmed links = $2n \times k + k \times m + m$** , whereas that of a **ROM** is $2^n \times m$

An example of PLA

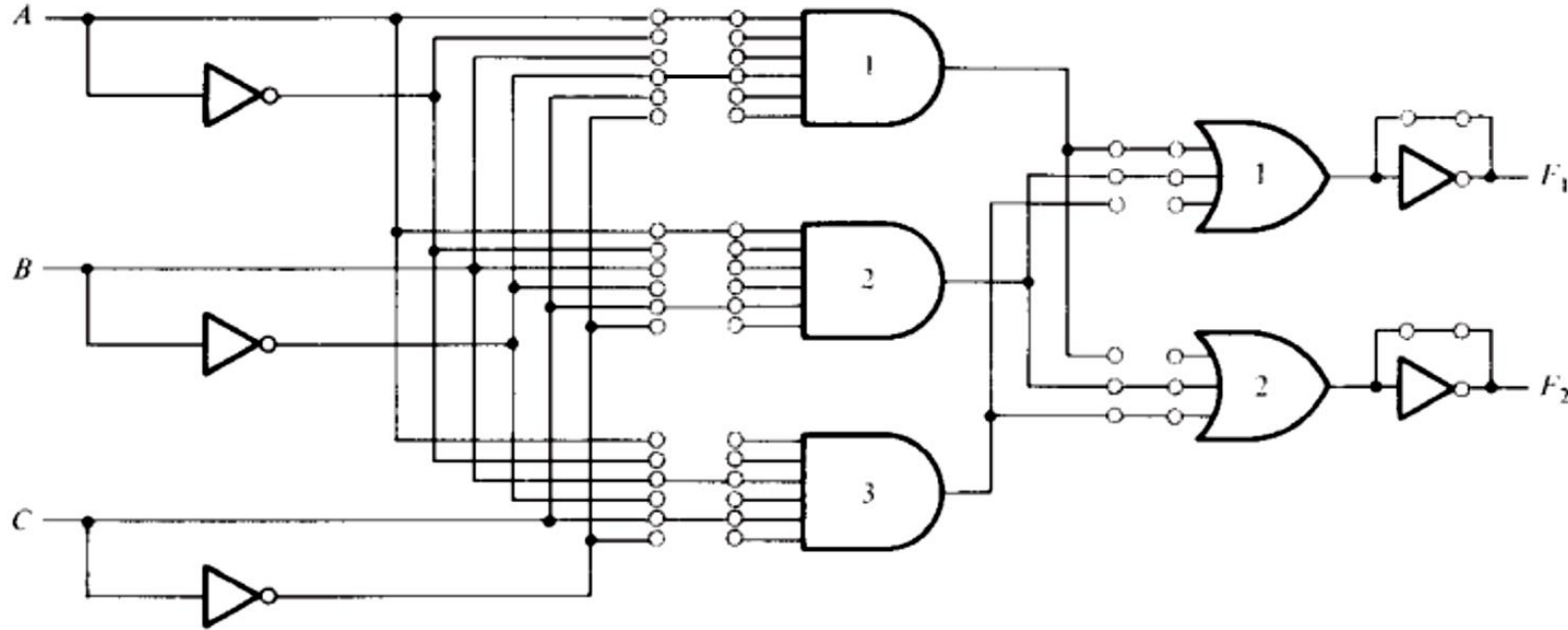

Inputs, $n = 3$
Product terms, $k = 3$
Outputs, $m = 2$
So, PLA size= ?


- As with ROM, PLA can be mask programmable and field programmable
- With a mask programmable PLA, customer must submit a PLA program table to the manufacturer
- Field programmable PLA is called FPLA and it is like as PROM

PLA Implementation Example


Consider the following combinational circuit as a truth table:

<i>A</i>	<i>B</i>	<i>C</i>	<i>F</i> ₁	<i>F</i> ₂
0	0	0	0	0
0	0	1	0	0
0	1	0	0	0
0	1	1	0	1
1	0	0	1	0
1	0	1	1	1
1	1	0	0	0
1	1	1	1	1

(a) Truth table

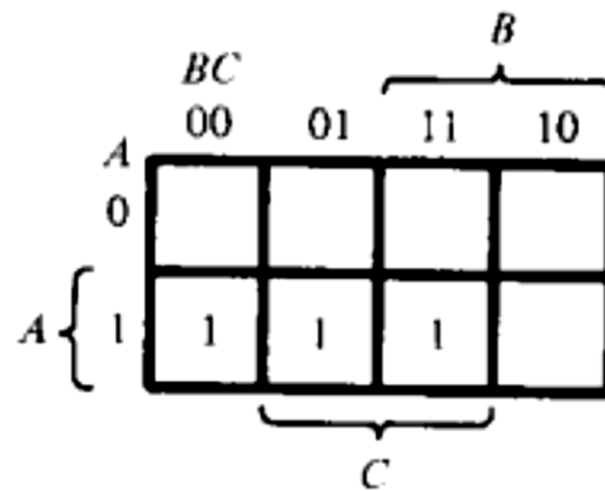

$$F_1 = AB' + AC$$

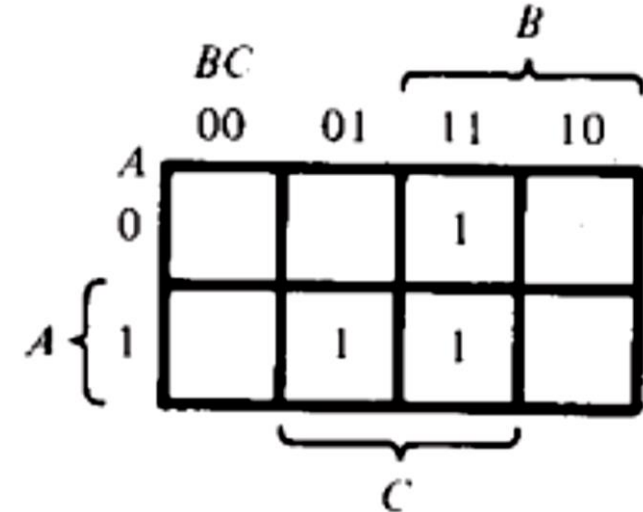

$$F_2 = AC + BC$$

(b) Map Simplification

PLA Implementation Example (Contd.)

$$F_1 = AB' + AC$$

$$F_2 = AC + BC$$


T: if output inverter is to be bypassed

C: For complement

	Product term	Inputs			Outputs	
		<i>A</i>	<i>B</i>	<i>C</i>	<i>F</i> ₁	<i>F</i> ₂
<i>AB'</i>	1	1	0	—	1	—
<i>AC</i>	2	1	—	1	1	1
<i>BC</i>	3	—	1	1	—	1
					<i>T</i>	<i>T</i>
					<i>T/C</i>	

(c) PLA program table

PLA Implementation Example (Contd.)

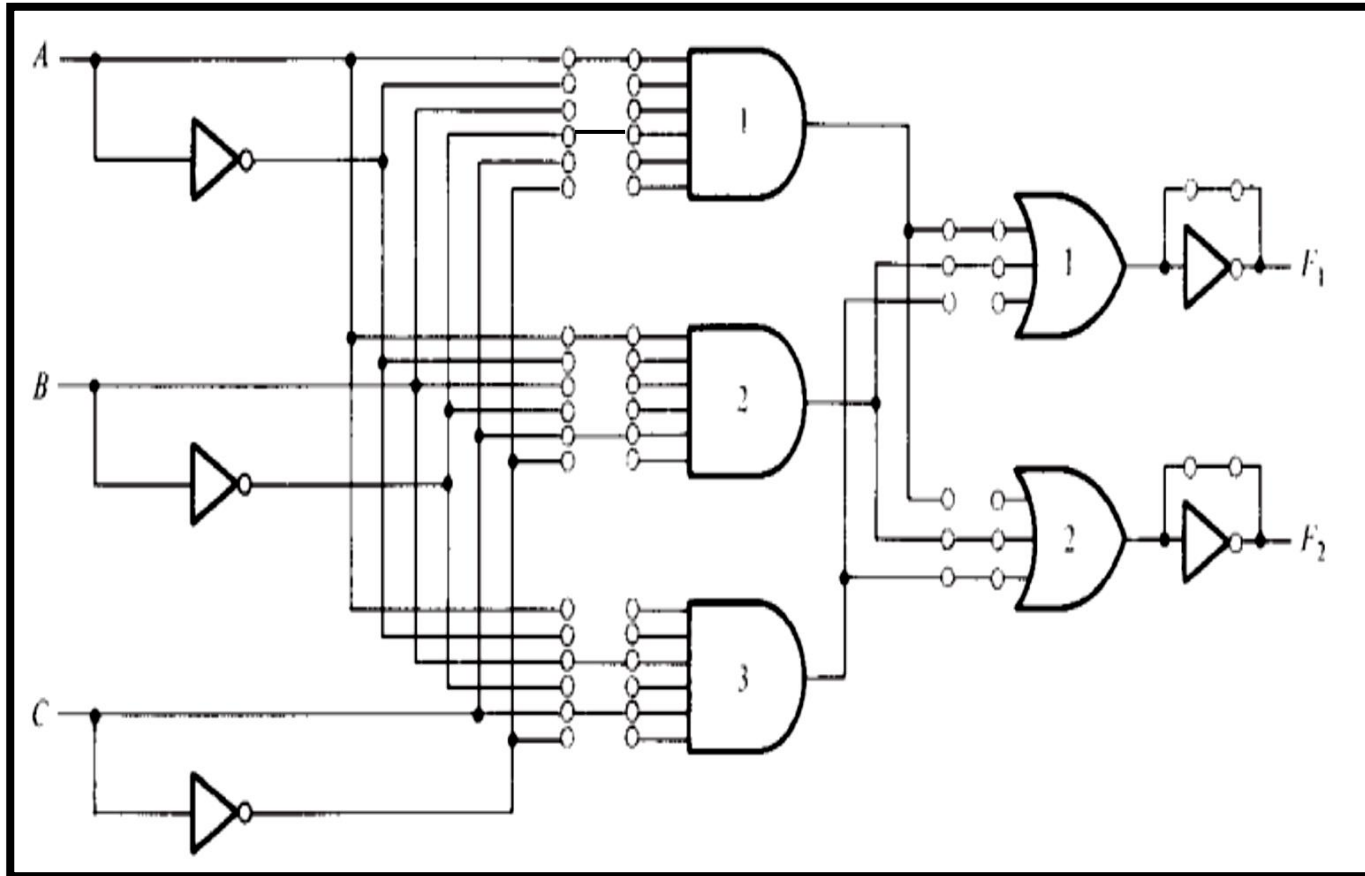

(d)PLA Diagram

Product term	Inputs			Outputs	
	A	B	C	F ₁	F ₂
AB'	1	0	—	1	—
AC	1	—	1	1	1
BC	—	1	1	—	1
				T	T
				T/C	

Designing a Digital System with PLA

- Reduce the number of distinct product terms
- The number of literals in a product is not important since we have all input variables
- Both the truth value and the complement value should be simplified
- See which can be expressed with fewer product terms
- And which one provides product terms that are common to other functions

PLA Implementation Example - 2

A combinational circuit is defined by the functions:

$$F_1(A, B, C) = \Sigma(3, 5, 6, 7)$$

$$F_2(A, B, C) = \Sigma(0, 2, 4, 7)$$

Implement the circuit with a PLA having three inputs, four product terms and two outputs.

PLA Implementation Example – 2 (Contd.)

$$F_1(A, B, C) = \Sigma(3, 5, 6, 7)$$

$$F_2(A, B, C) = \Sigma(0, 2, 4, 7)$$

$$F_1 = (B'C' + A'C' + A'B')'$$

$$F_2 = B'C' + A'C' + ABC$$

		<i>BC</i>		<i>B</i>	
		00	01	11	10
<i>A</i>	0			1	
<i>A</i>	1		1	1	1

$$F_1 = AC + AB + BC$$

		<i>BC</i>		<i>B</i>	
		00	01	11	10
<i>A</i>	0	1			1
<i>A</i>	1	1		1	

$$F_2 = B'C' + A'C' + ABC$$

		<i>BC</i>		<i>B</i>	
		00	01	11	10
<i>A</i>	0	0	0		0
<i>A</i>	1	0			

$$F_1' = B'C' + A'C' + A'B'$$

		<i>BC</i>		<i>B</i>	
		00	01	11	10
<i>A</i>	0		0	0	
<i>A</i>	1		0		0

$$F_2' = B'C + A'C + ABC'$$

PLA Implementation Example – 2 (Contd.)

$$F_1 = (B'C' + A'C' + A'B')'$$

$$F_2 = B'C' + A'C' + ABC$$

PLA program table

	Product term	Inputs			Outputs	
		A	B	C	F ₁	F ₂
<i>B'C'</i>	1	–	0	0	1	1
<i>A'C'</i>	2	0	–	0	1	1
<i>A'B'</i>	3	0	0	–	1	–
<i>ABC</i>	4	1	1	1	–	1
					<i>C</i>	<i>T</i>
					<i>T/C</i>	

*****Draw the PLA Circuit Diagram.**

Applications of PLA

- PLA is used to provide control over datapath.
- PLA is used as a counter.
- PLA is used as a decoders.
- PLA is used as a BUS interface in programmed I/O.
- It defines various states in an instruction set, and produces the next state (by conditional branching)