



Ahsanullah University of Science & Technology

Department of Computer Science & Engineering

LAB REPORT

Course No : EEE-2142

Course Title : Electronics Device & Circuits Lab

Experiment No : 05

Experiment Name : The output characteristics of CE (common emitter) configuration of BJT

Submitted By-

Name : S.M. Tasnimul Hasan

Id : 18.02.04.142

Department : CSE

Section : B (B2)

Group No : 06

Date of Performance : 31/08/2020

Date of Submission : 10/09/2020

Experiment No : 05

Name of the Experiment :

The output characteristics of CE (common emitter) configuration of BJT.

Objective :

Study of the output characteristics of CE (common emitter) configuration of BJT.

Equipments and Components :

Serial No.	Component Details	Specification	Quantity
1.	Transistor	C828	1 piece
2.	Resistor	470K Ω , 1K Ω	1 piece each
3.	POT	100 K Ω	1 unit
4.	Trainer Board		1 unit
5.	DC Power Supply		1 unit
6.	Digital Multimeter		1 unit
7.	Cables and wire		as required

Experimental setup :

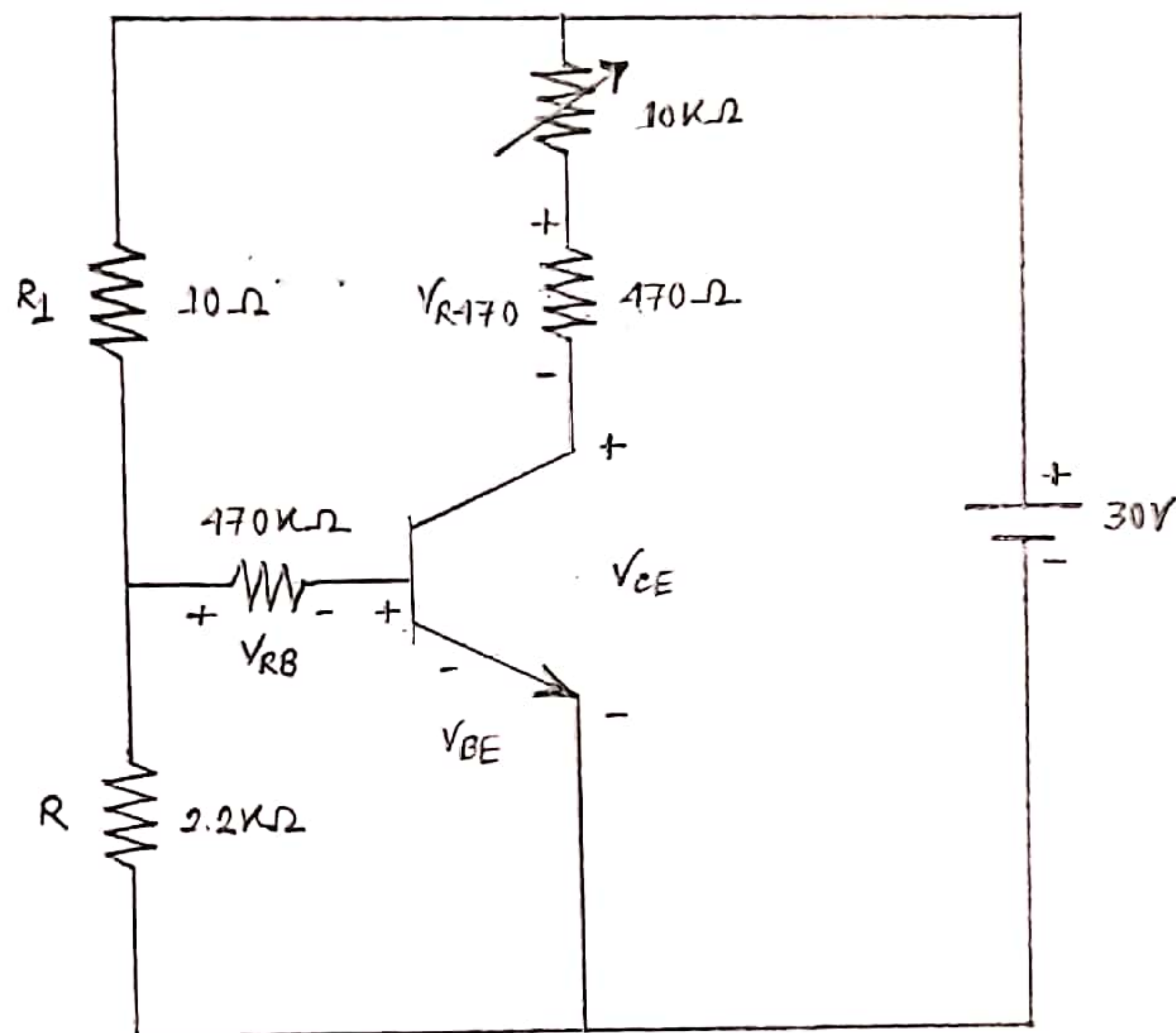


Figure : Experimental Circuit.

Data Table :

V_{RB} (V)	$I_B = V_{RB}/470K$ (μA)	V_{CE} (V)	V_{R470} (V)	$I_C = V_{R470}/470$ (mA)
4.63	9.85	0.05	0.19	0.40
		0.08	0.35	0.74
		0.09	0.51	1.09
		0.11	0.66	1.40
		0.12	0.88	1.87
		0.19	1.73	3.68
		3.05	1.97	4.19
		7.8	2.06	4.38
		12.66	2.13	4.53
		17.81	2.14	4.56

Calculation :


Here,

$$\begin{aligned} I_C &= \frac{V_{R470}}{R} \\ &= \frac{0.19}{470} \\ &= 0.4 \text{ mA} \end{aligned}$$

Similarly, we get the other values of I_C by
Varying the pot.

Report :

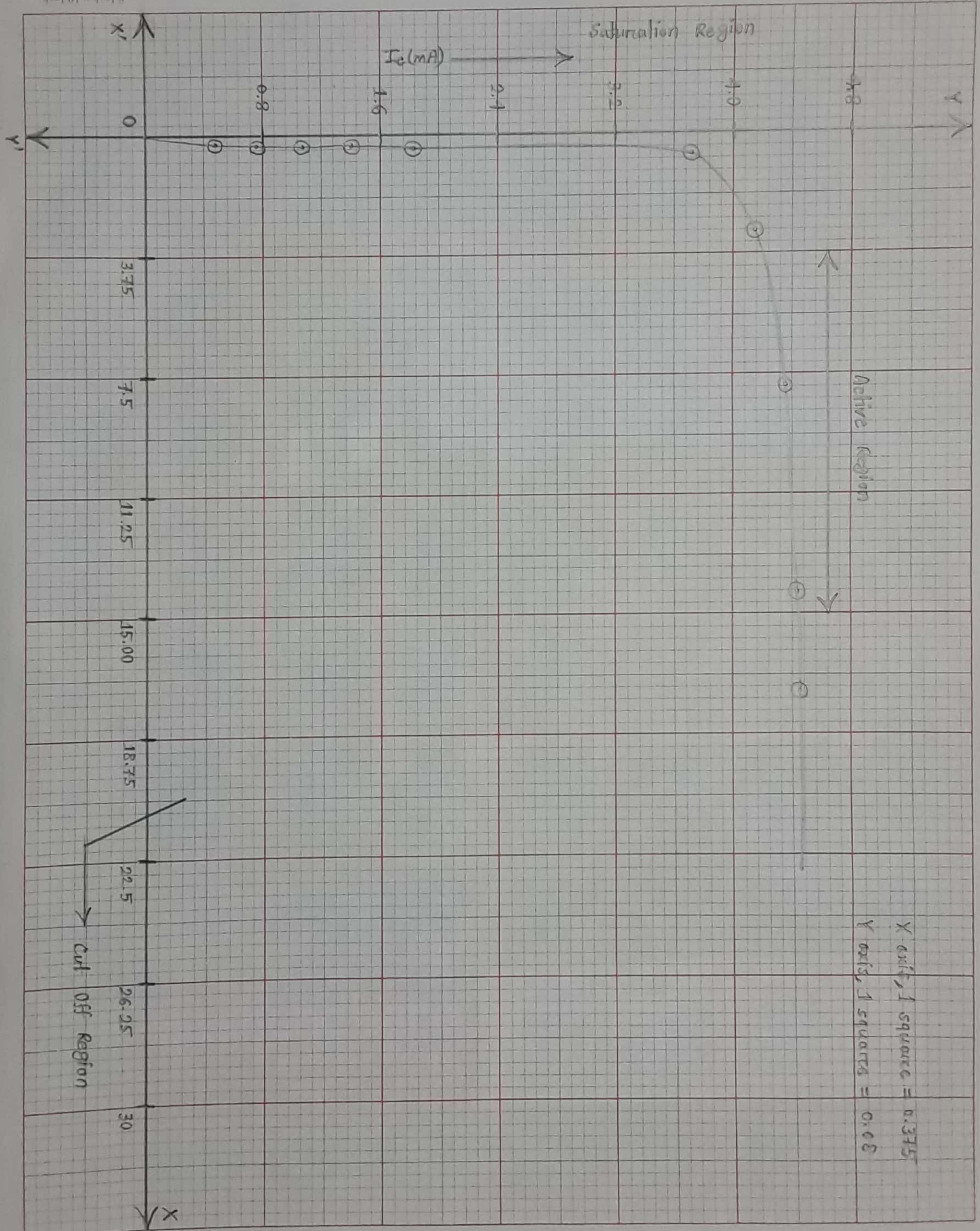- ① Plot the graph of I_c vs V_{CE} with necessary details. show the different regions of operation.



X axis, 1 square = 0.375
Y axis, 1 square = 0.08

Saturation Region

Active Region

Cut Off Region

② Plot a hypothetical output characteristics using PNP transistor.

Ans: A hypothetical output characteristics using PNP transistor is given below :

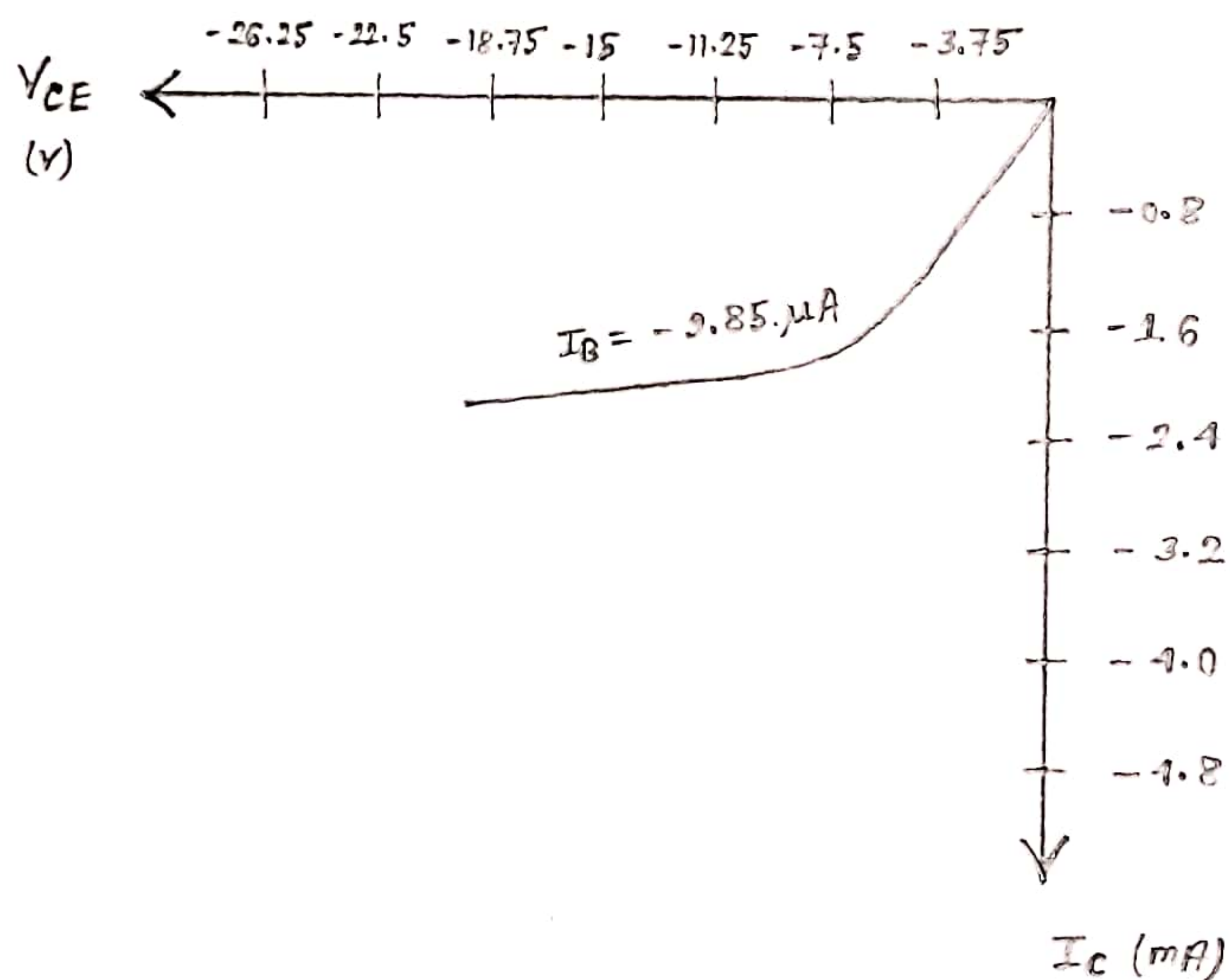


Figure : Hypothetical output characteristics using PNP transistor.

③ Find β for the three different condition.

Ans: From the experiment,

$$I_c = 4.56 \text{ mA}$$

$$I_B = 9.85 \mu\text{A}$$

Here,

$$\begin{aligned}\beta &= \frac{I_c}{I_B} \\ &= \frac{4.56 \text{ mA}}{9.85 \mu\text{A}} \\ &= 463\end{aligned}$$

As, V_{BB} is fixed, so only one value of I_B can be measured. The value of β is 463 in this experiment.

Discussion :

In this experiment, we have studied the output characteristics of CE (common emitter) configuration of BJT. Common emitter configuration is mostly used because it provides the voltage gain required for most of the day to day applications. The experiment was done successfully.