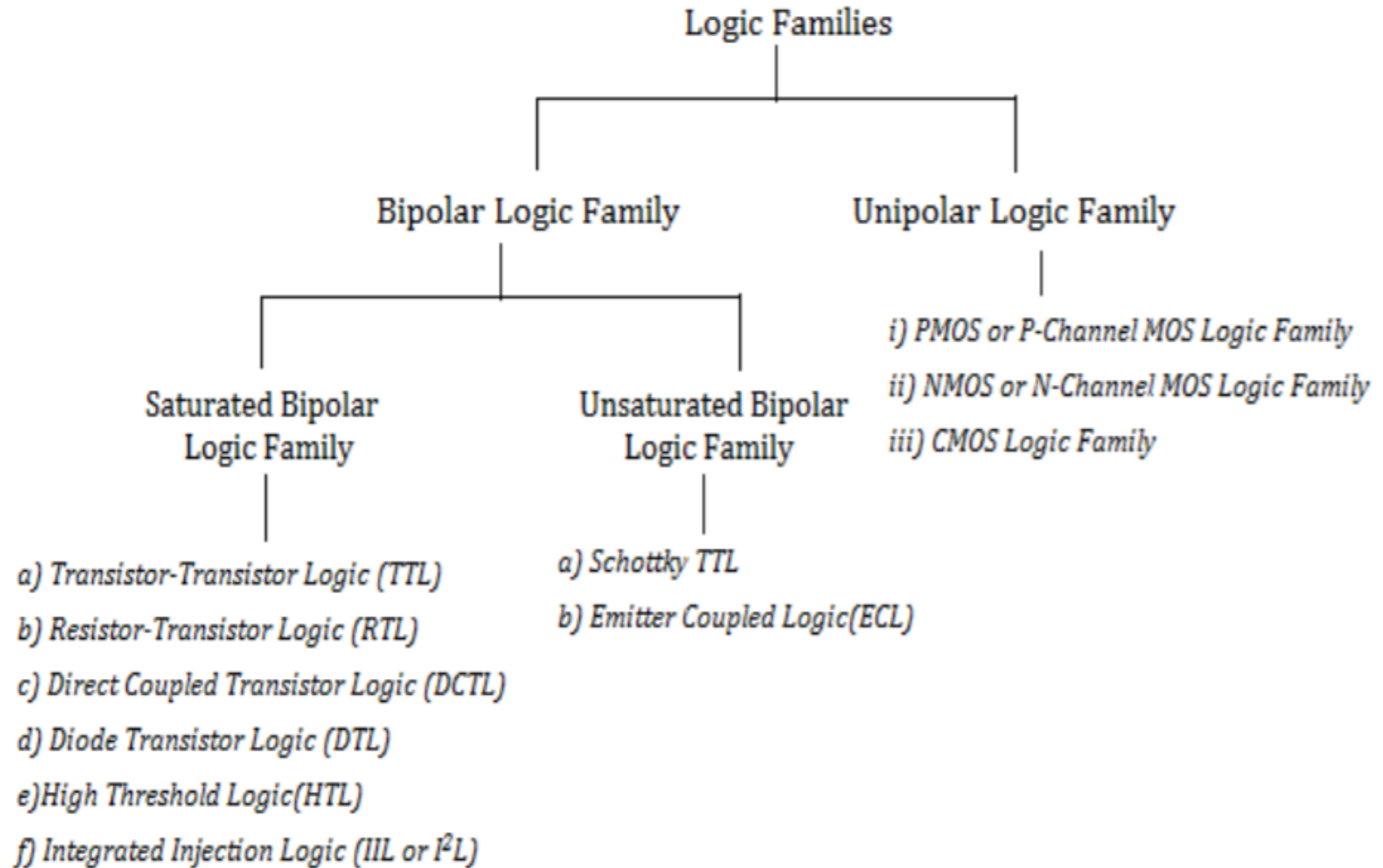


# CSE2209: Digital Electronics and Pulse Techniques

Course Conducted By:

Nowshin Nawar Arony  
Lecturer, Dept of CSE, AUST



# Logic Families

- **Diode Logic (DL)**
- **Diode Transistor Logic (DTL)**
- **Transistor - Transistor Logic (TTL)**
- **Resistor-Transistor Logic (RTL)**
- **Direct Coupled Transistor Logic (DCTL)**
- **Emitter Carbon Logic (ECL)**
- **High Threshold Logic (HTL)**
- **Complementary Metal Oxide Semiconductor Logic (CMOS)**

# Logic System

$$V(1) = 4 \text{ V}$$

Positive Logic

$$V(0) = 0.2 \text{ V}$$

$$V(0) = 4 \text{ V}$$

Negative Logic

$$V(1) = 0.2 \text{ V}$$

# AND Operation

A	B	$V_o$
0 V	0 V	0 V
0 V	5 V	0 V
5 V	0 V	0 V
5 V	5 V	5 V

A	B	$V_o$
V(0)	V(0)	V(0)
V(0)	V(1)	V(0)
V(1)	V(0)	V(0)
V(1)	V(1)	V(1)

Positive Logic

AND Gate

A	B	$V_o$
V(1)	V(1)	V(1)
V(1)	V(0)	V(1)
V(0)	V(1)	V(1)
V(0)	V(0)	V(0)

Negative Logic

OR Gate


# Diode Logic (DL)

A diode is a terminal electrical device that allows current to flow in one direction.




- Registers and diodes are used to implement logic.
- The purpose of diode is to perform OR and AND operation, and logic switch.
- Disadvantages: diodes can not perform NOT operation, diode cannot work for multiple states, states, only one stage at a time, tend to degrade signals quickly.

## Forward Biased

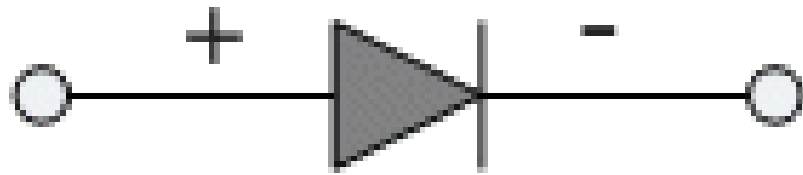


0.7v

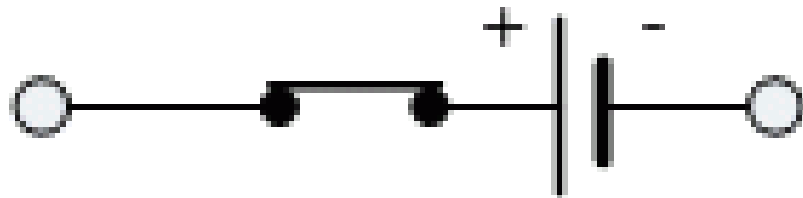


Forward Bias  
(switch closed)


## Reversed Biased

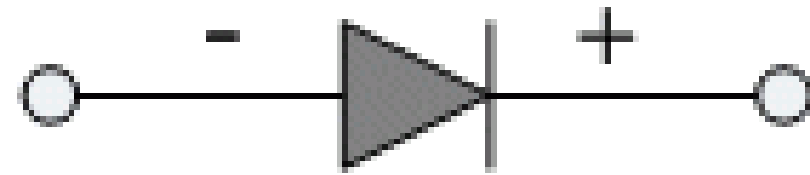

0.7v

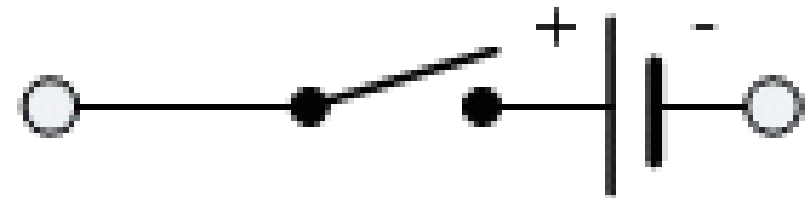


Reverse Bias  
(switch open)

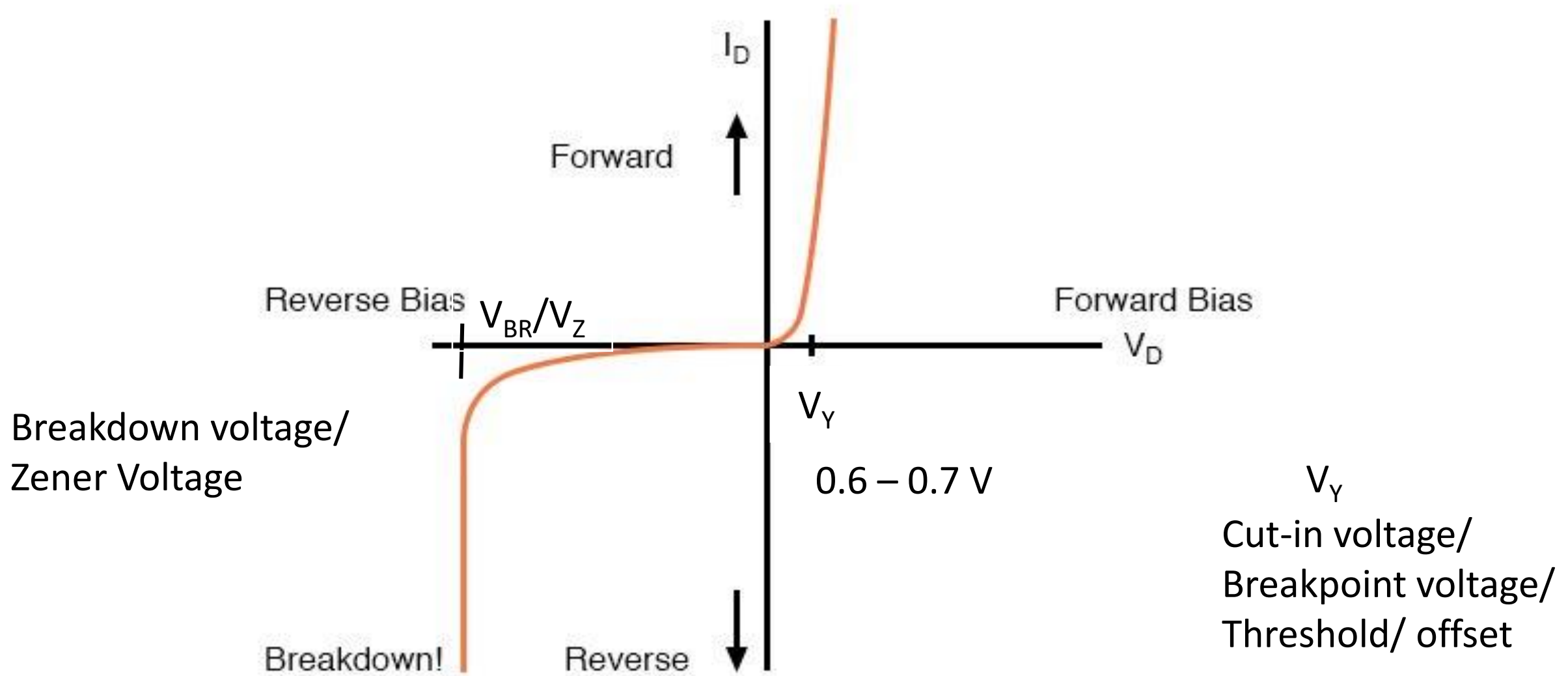


V-I characteristics of Silicon Diode


# Ideal Case

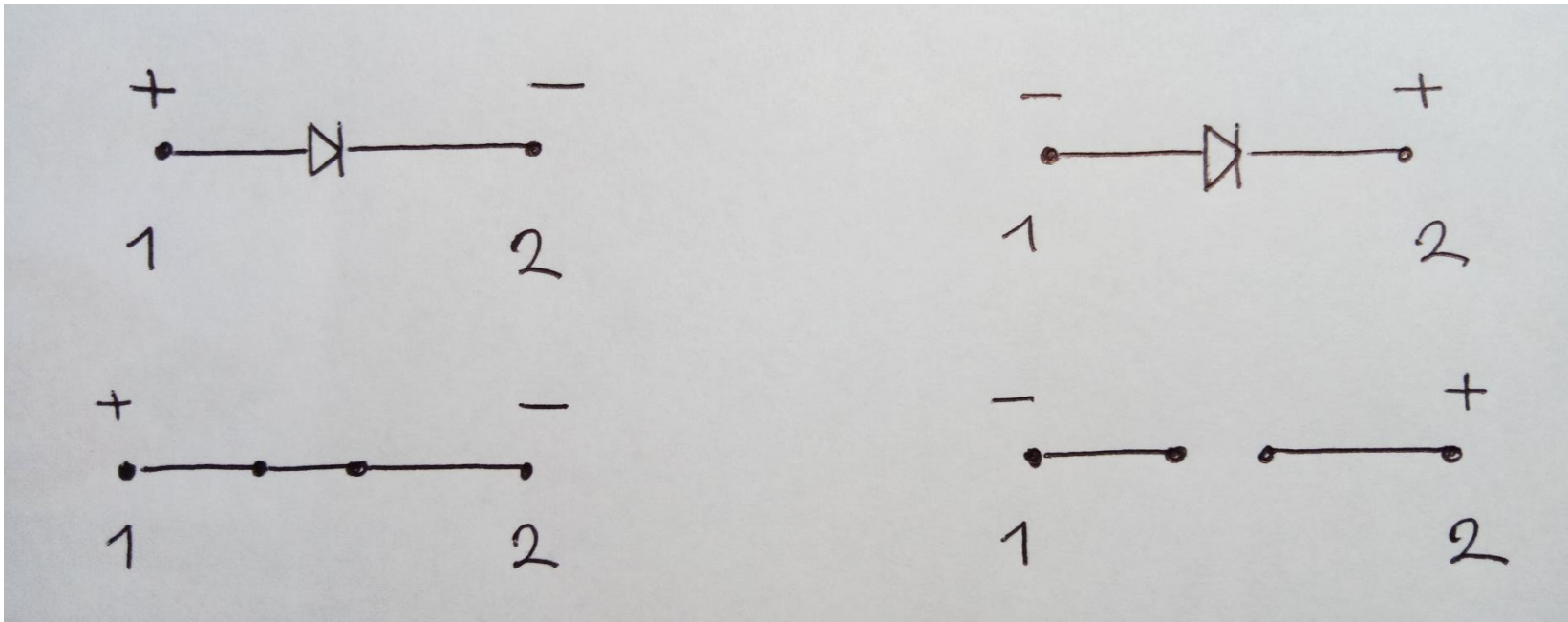


# Constant Voltage Source Model

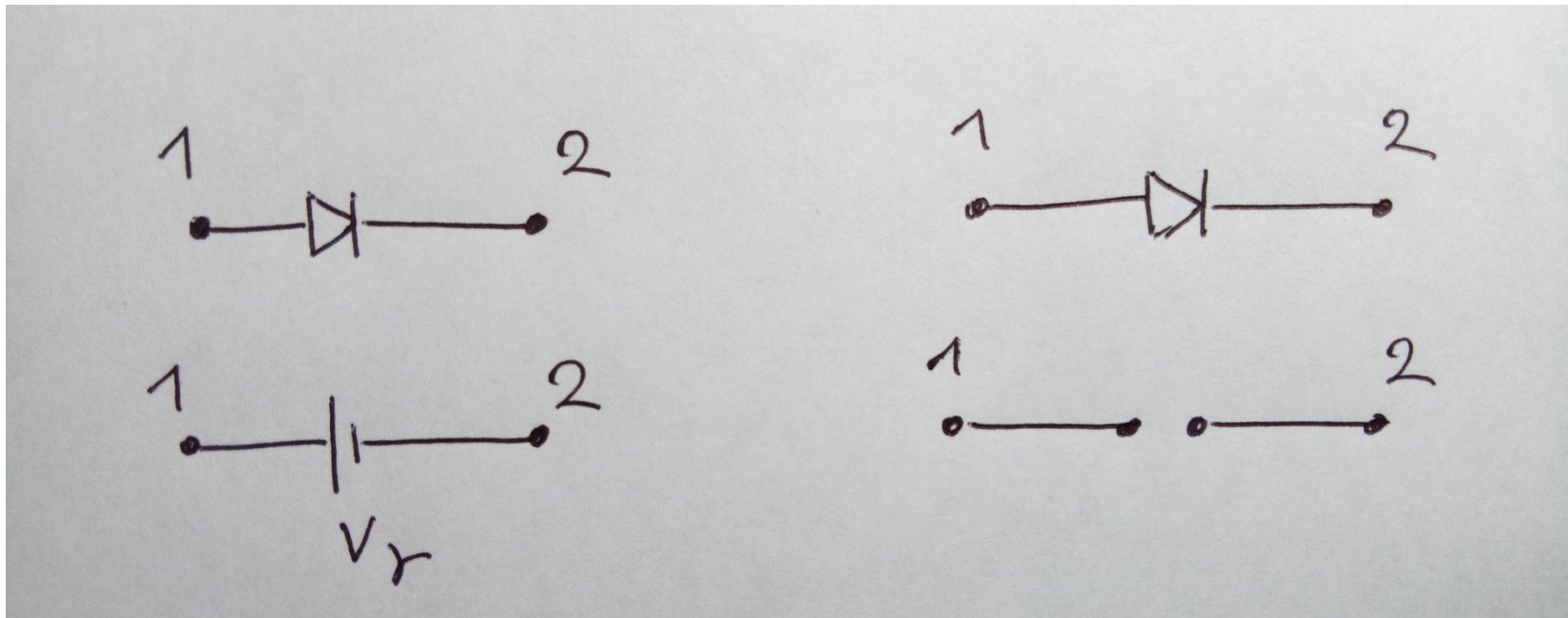


# Piece-wise Linear Model

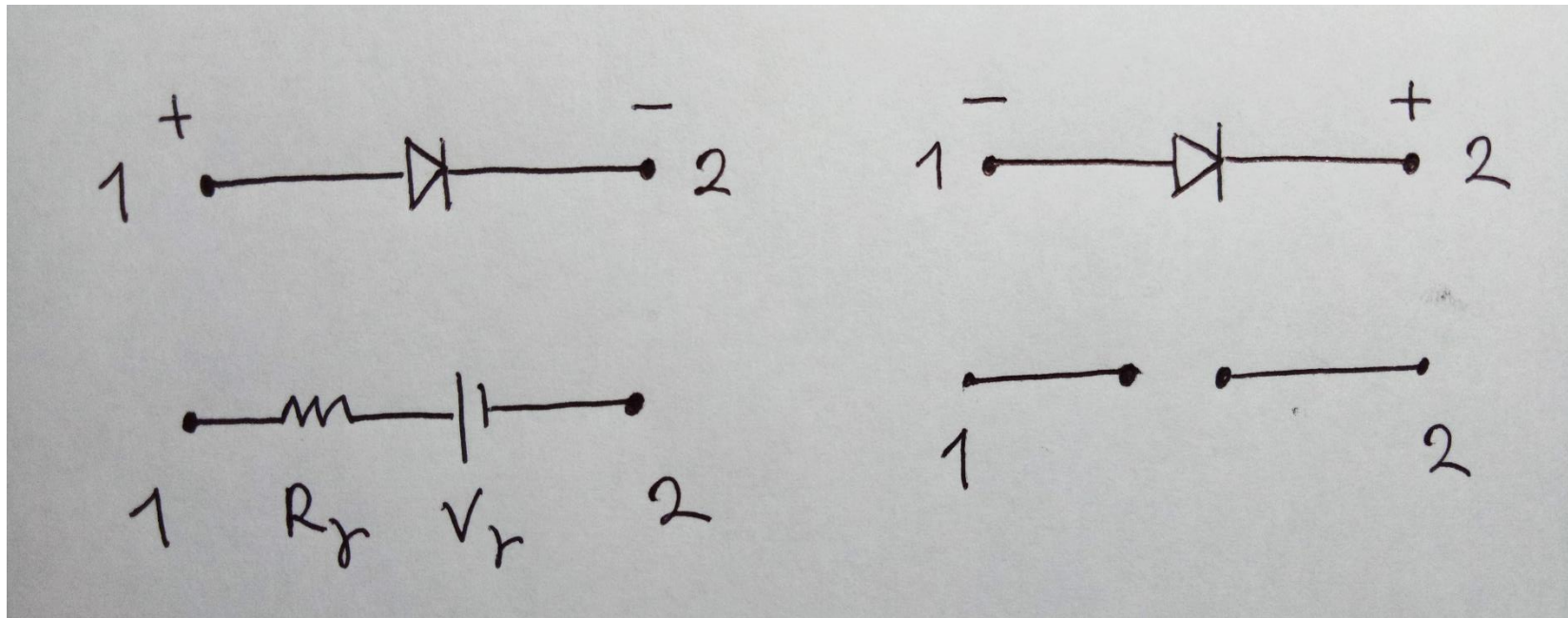

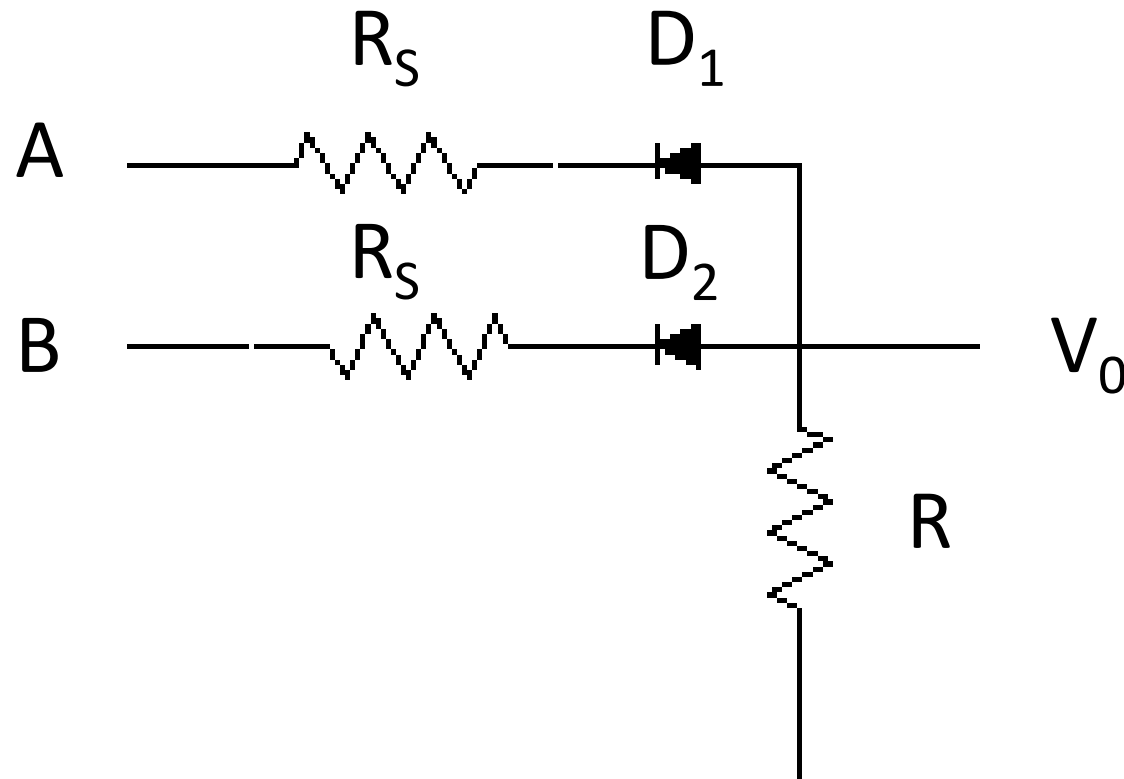Prove that this circuit works like a negative logic OR gate.




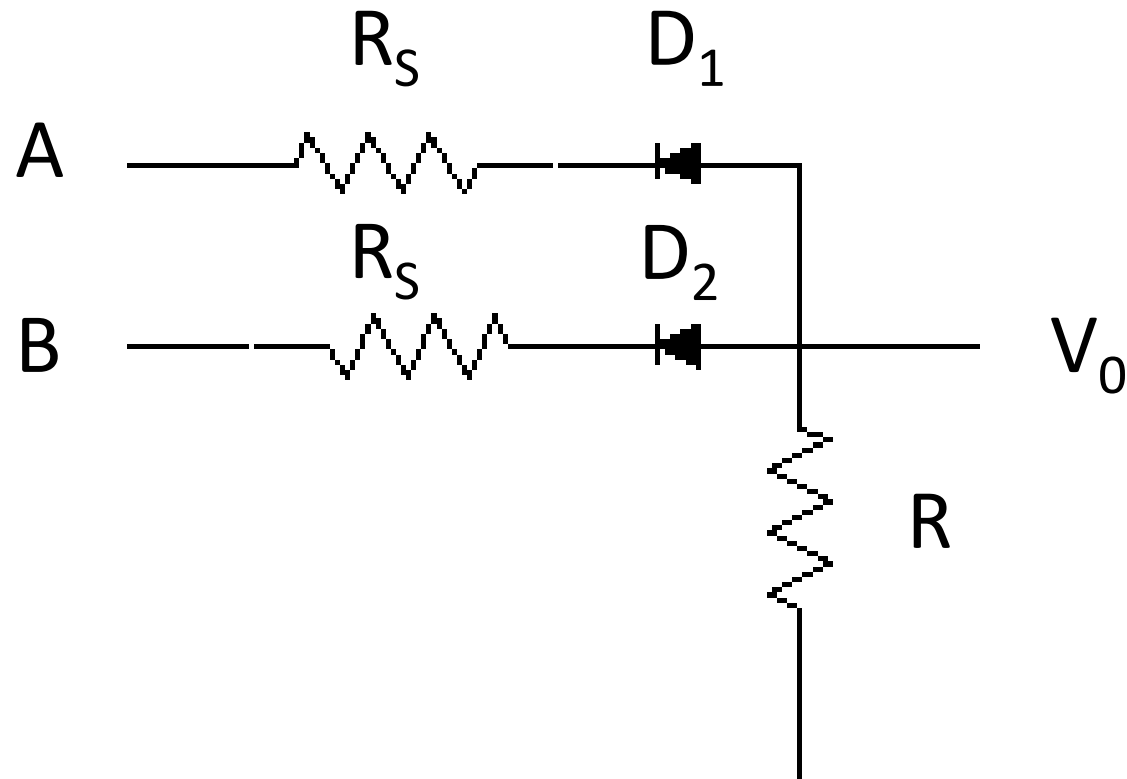Prove that this circuit works like a positive logic AND gate.






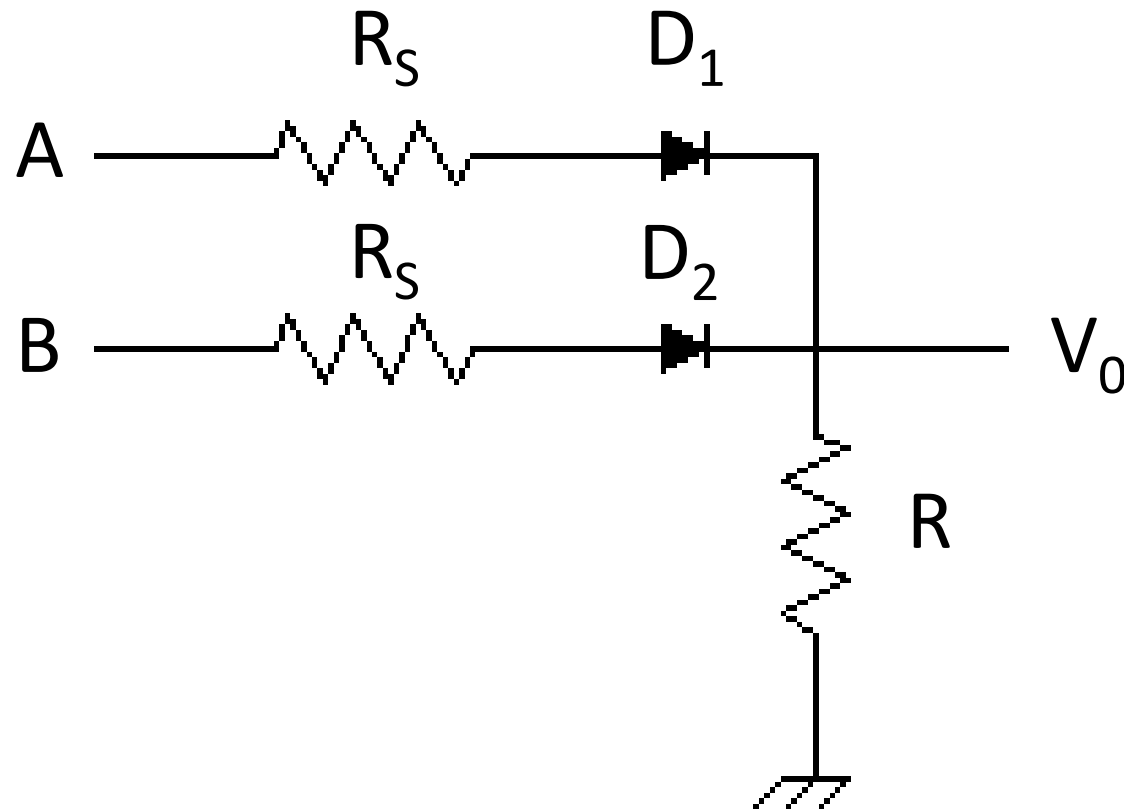Prove that this circuit works like a negative logic AND gate.



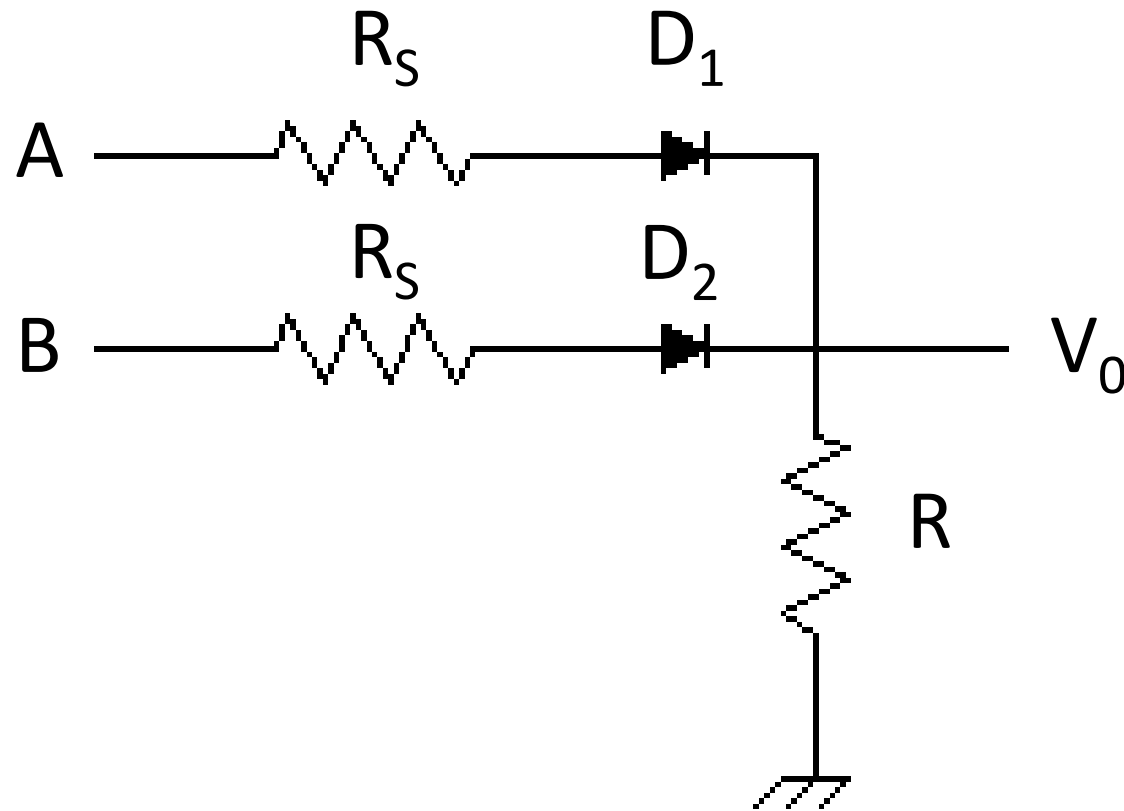Prove that this circuit works like a positive logic OR gate.




# Transistor


A transistor is a semiconductor device used to amplify or switch electronic signals and electrical power.

There are two types of transistor, namely NPN transistor and PNP transistor.

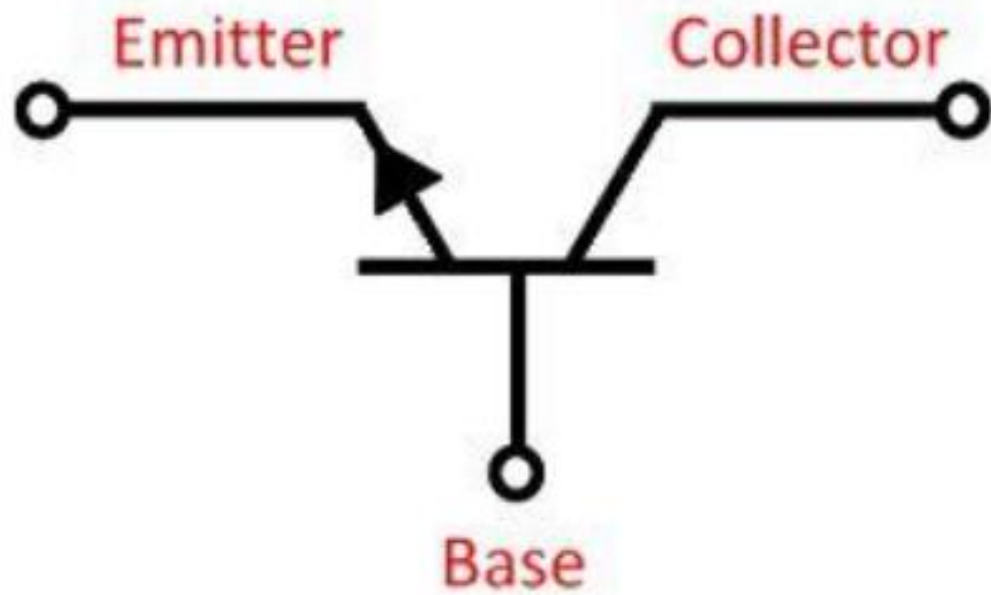- The transistor which has two blocks of n-type semiconductor material and one block of P-type semiconductor material is known as NPN transistor.
- Similarly, if the material has one layer of N-type material and two layers of P-type material then it is called PNP transistor.



NPN Transistor

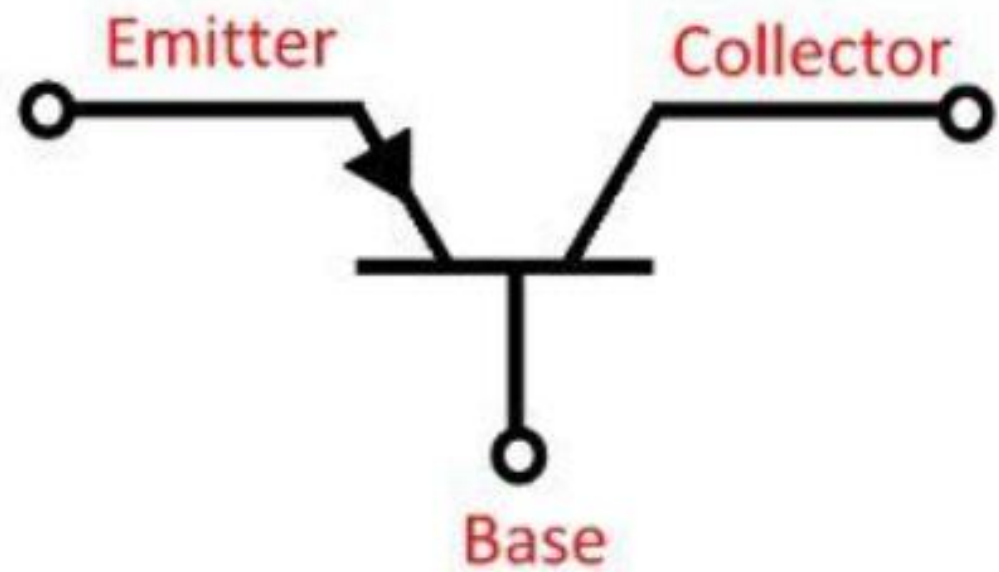


PNP Transistor

Circuit Globe

Common Emitter Gain,

$$h_{fe} = \frac{I_c}{I_B}$$

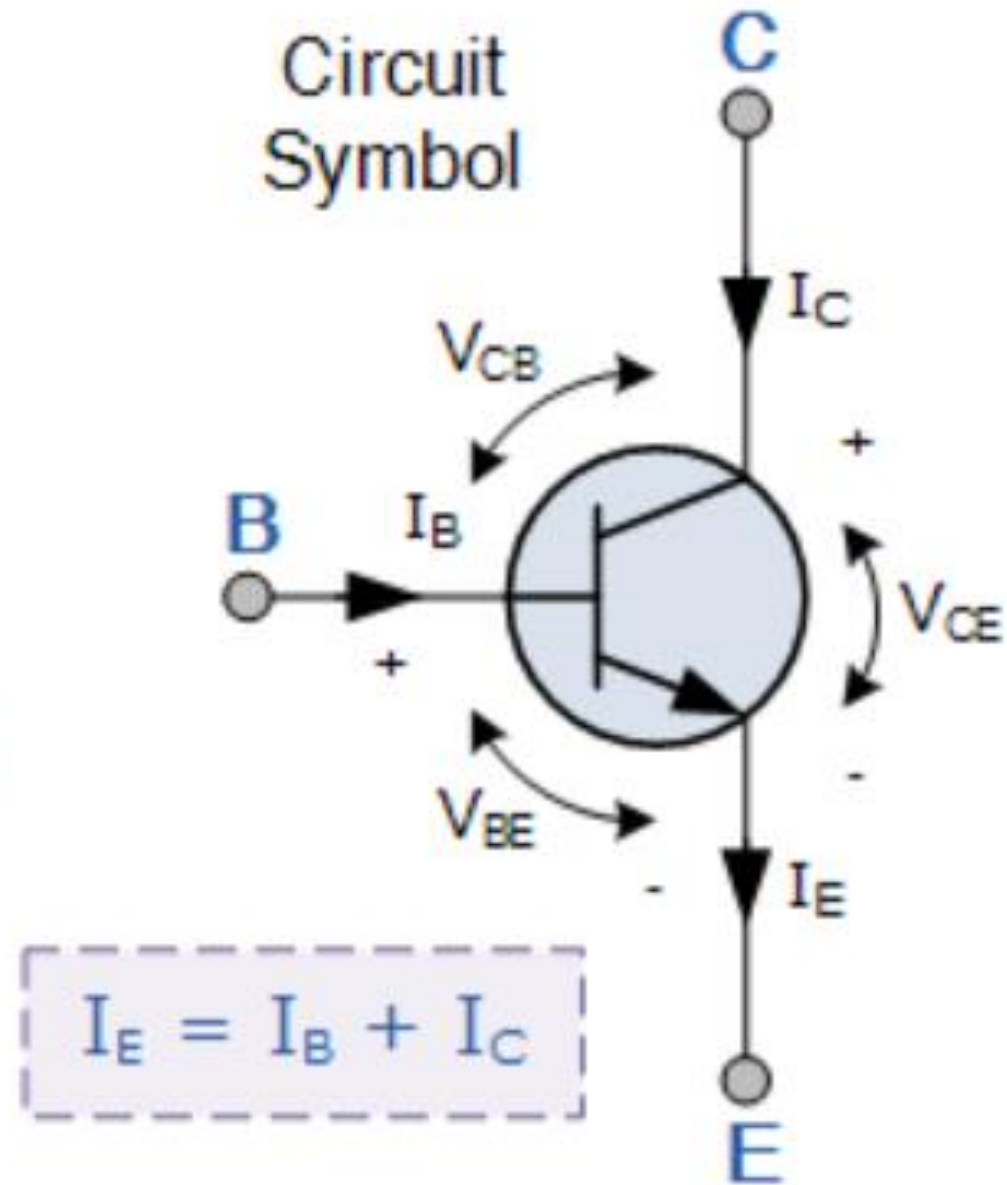


# Transistor Operation Modes

Four distinct modes of operation-

- Saturation -- The transistor acts like a short circuit. Current freely flows from collector to emitter.
- Cut-off -- The transistor acts like an open circuit. No current flows from collector to emitter.
- Active -- The current from collector to emitter is proportional to the current flowing into the base.
- Reverse-Active -- Like active mode, the current is proportional to the base current, but it flows in reverse. Current flows from emitter to collector.

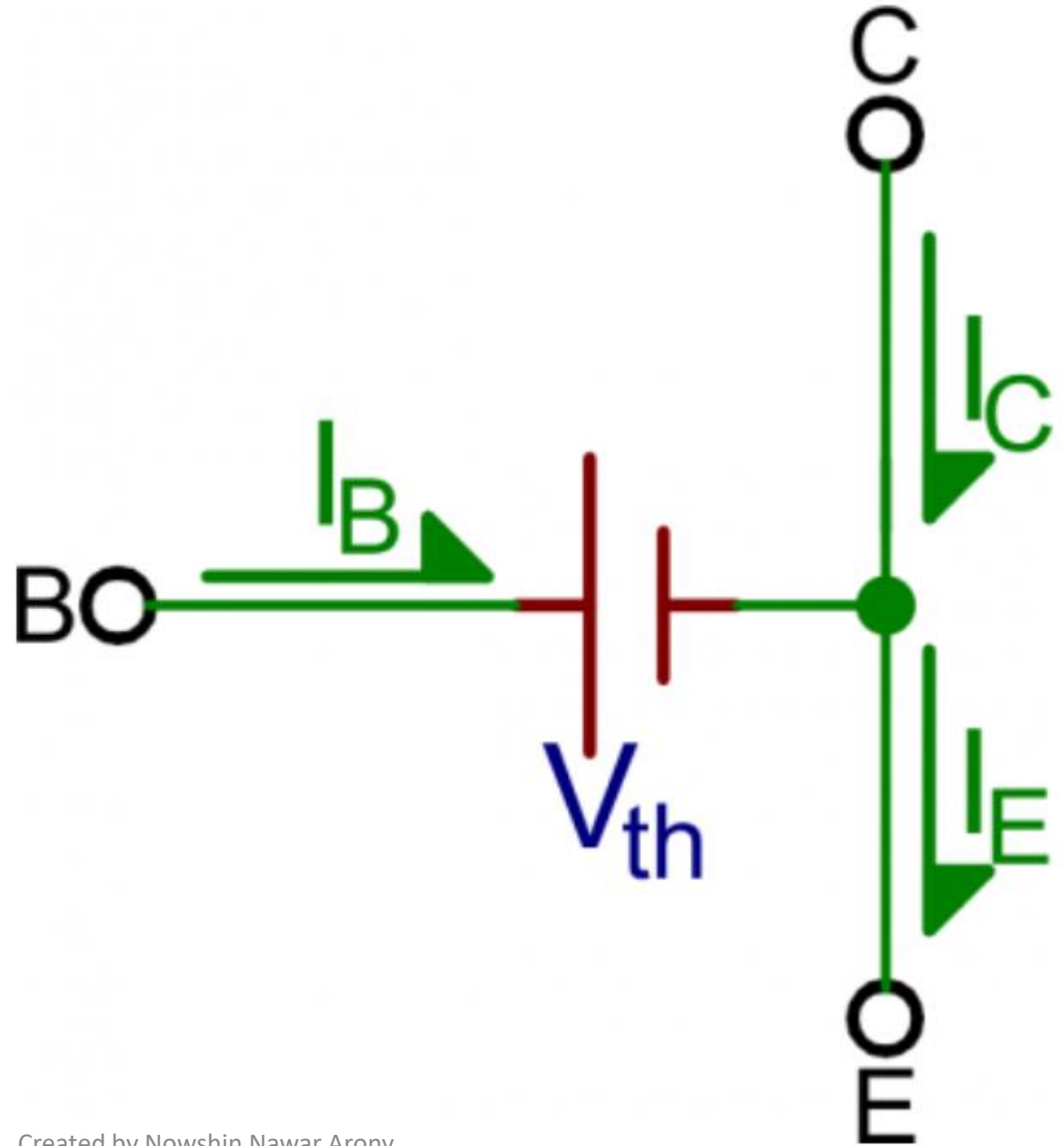
## Saturation Mode

Saturation is the on mode of a transistor. A transistor in saturation mode acts like a short circuit between collector and emitter.



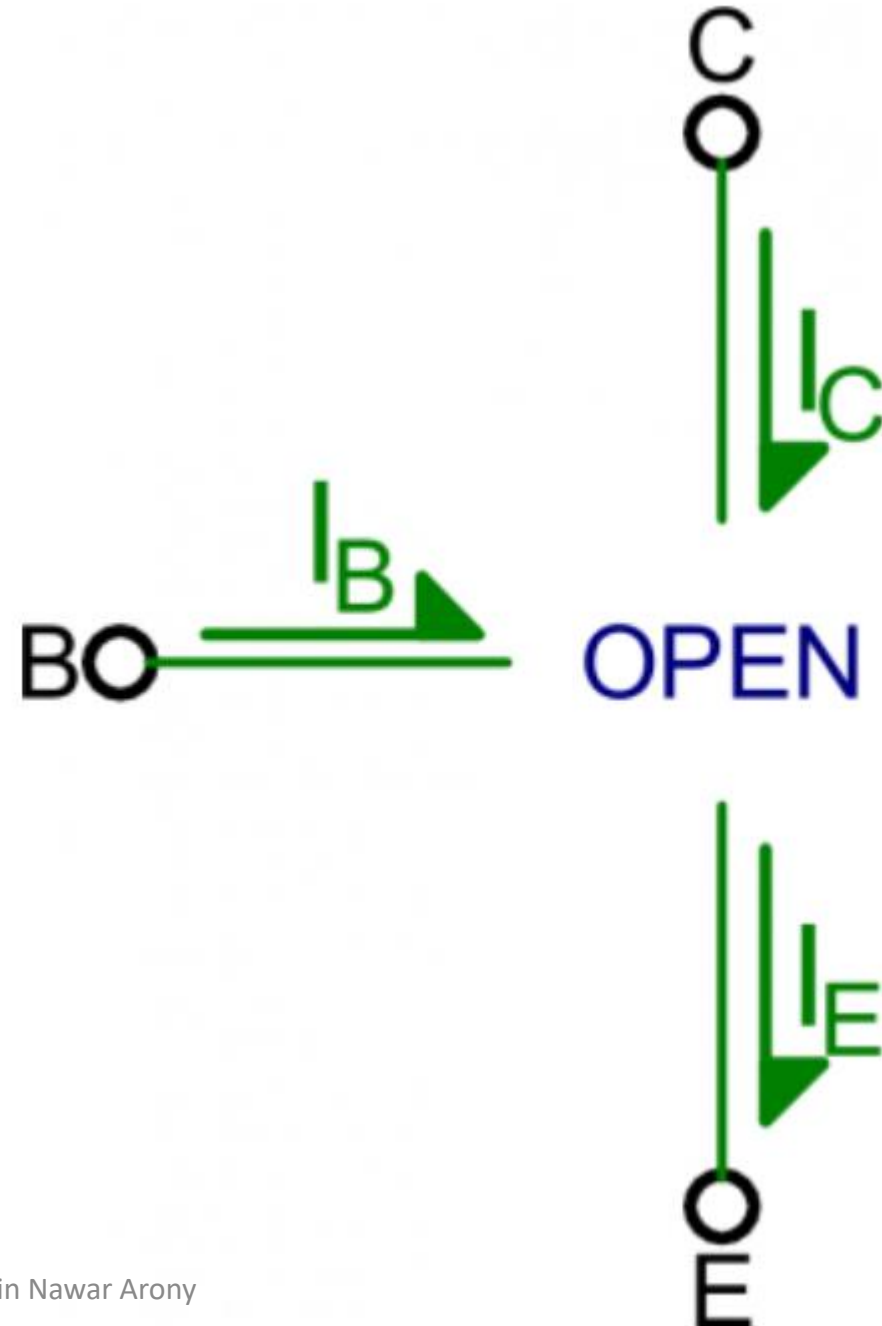
## Cutoff Mode

Cutoff mode is the opposite of saturation. A transistor in cutoff mode is off -- there is no collector current, and therefore no emitter current. It almost looks like an open circuit.





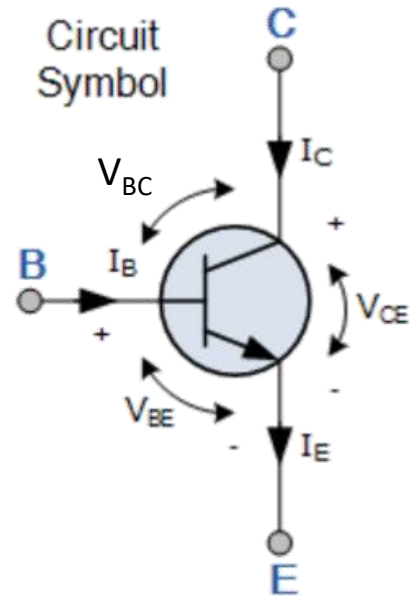


BE	BC	Transistor State
$(V_{BE} < 0.7V) R$	$(V_{BC} < 0.7V) R$	Cut off $I_C = I_B = I_E = 0$
$(V_{BE} > 0.7V) F$	$(V_{BC} < 0.7V) R$	Active $I_C = h_{fe} * I_B$
$(V_{BE} < 0.7V) R$	$(V_{BC} > 0.7V) F$	Inverse active
$(V_{BE} > 0.7V) F$	$(V_{BC} > 0.7V) F$	Saturation $I_C \leq h_{fe} * I_B$ $V_{CE} (sat) = 0.2V$ $V_{BE} (sat) = 0.8V$

**Table 3-1 Typical  $n$ - $p$ - $n$  transistor-junction voltages<sup>†</sup> at 25°C**

Material	$V_{CE(sat)}$	$V_{BE(sat)} \equiv V_o$	$V_{BE(active)}$	$V_{BE(cut in)} \equiv V_\gamma$	$V_{BE(cutoff)}$
Si	0.2	0.8	0.7	0.5	0.0
Ge	0.1	0.3	0.2	0.1	-0.1

Pg = 79 in Book

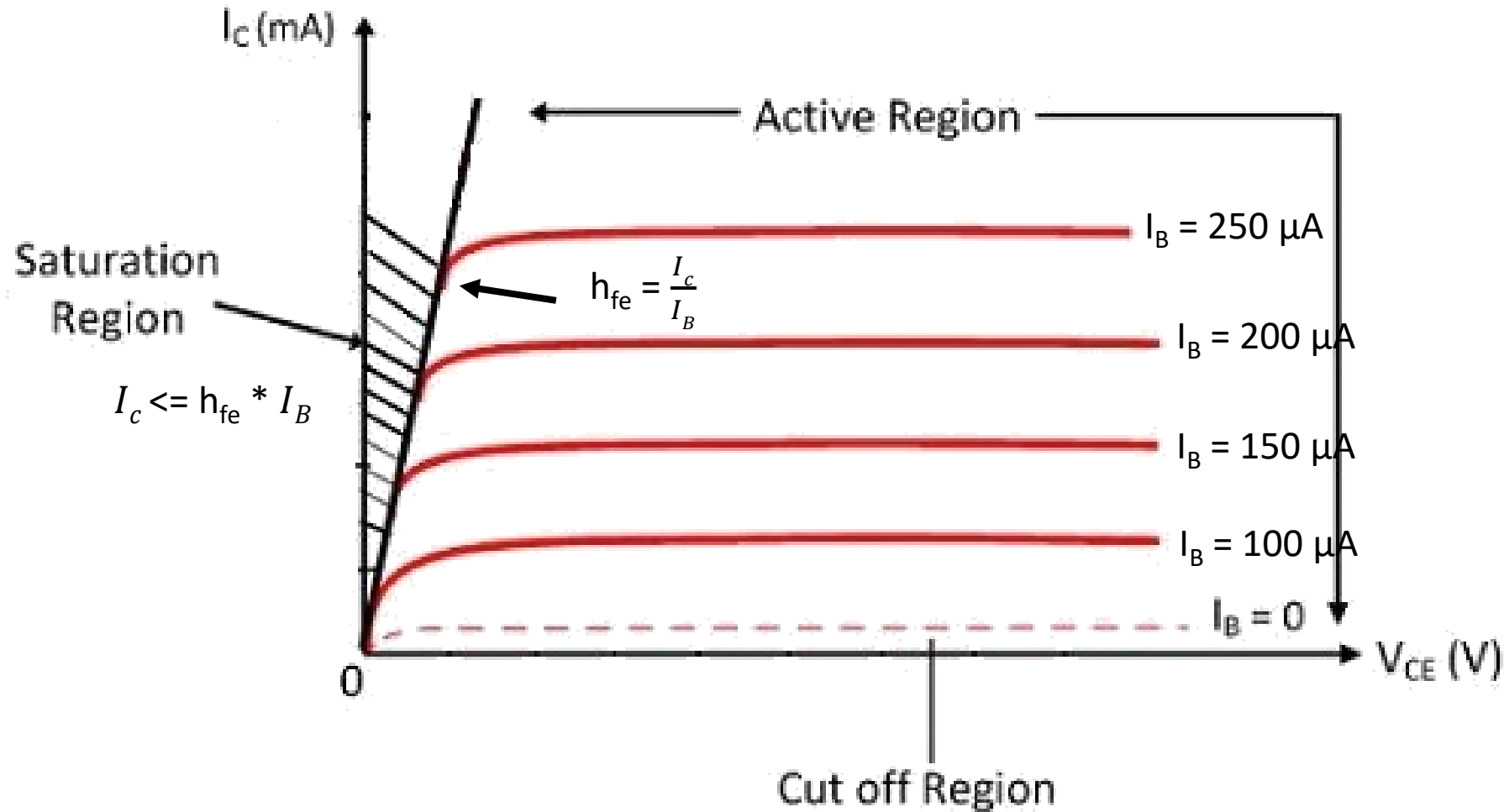
# Output characteristics of npn transistor



**Output Characteristic Curve**
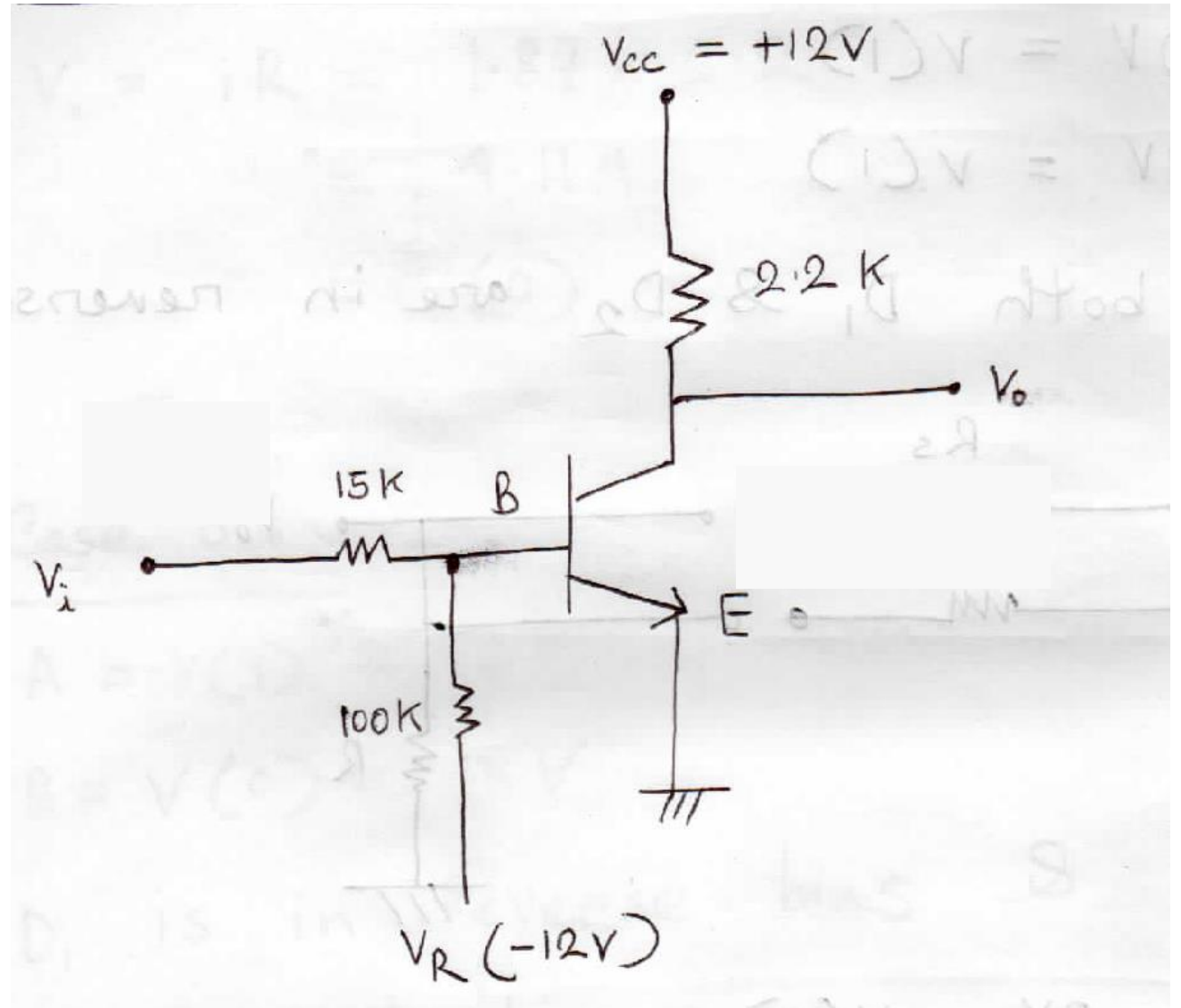
# Transistorized NOT Gate (Positive Logic)

- Prove that the circuit works like a positive logic NOT gate.
- Find the minimum value of  $h_{fe}$  for proper operation of the circuit.



# DTL Positive Logic NAND Gate

- Prove that the circuit works like a positive logic NAND gate.
- Prove that the circuit works like a negative logic NOR gate.
- Find the minimum value of  $h_{fe}$  and mode operation of the circuit.

