



Case 1:

If  $V_i = 3.6 \text{ V}$  i.e.  $V(1)$  then the corresponding transistor will be in saturation.

Thus,  $V_o = 0.2 \text{ V}$


Case 2:

For  $V_i = 0.2 \text{ V}$  then all the input transistors will be in cut off.

So, the output  $V_o$  will be dependent on fan out.


If  $N = 5$ , then  $V_o$  is loaded by five  $450 \Omega$  resistors in parallel

(or  $90 \Omega$ )

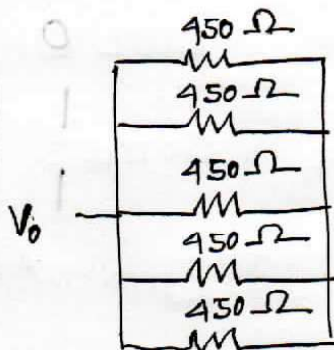

These resistance are connected to

$$V_{BE(sat)} \approx 0.8 \text{ V}$$

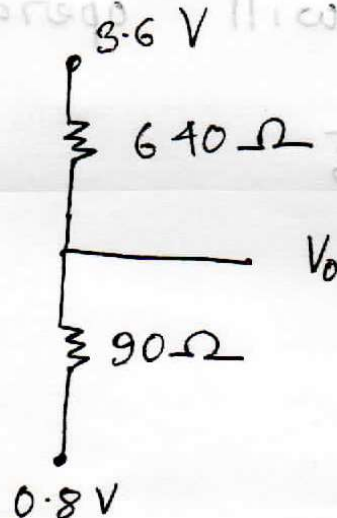

By superposition,

$$V_0 = \frac{640}{640 + 90} * 0.8 + \frac{90}{640 + 90} * 3.6$$
$$= 1.14 \text{ V}$$

This must be large enough to drive 5 transistors into saturation.

To be in saturation,

$$I_B = \frac{1.14 - 0.8}{0.45 \text{ K}} = 0.755 \text{ mA}$$



$$I_c = \frac{3.6 - 0.2}{0.64 \text{ k}} = 5.31 \text{ mA}$$

then ckt will operate ~~is~~ if

$$h_{fe(\min)} = \frac{5.31}{0.76}$$

$$= 7$$

$$2.0 \text{ A} * \frac{12.0 \text{ V}}{12.0 \text{ V} + 8.0 \text{ V}} + 8.0 \text{ A} * \frac{8.0 \text{ V}}{12.0 \text{ V} + 8.0 \text{ V}} = 0 \text{ V}$$

This must be large enough to drive