

CSE2209: Digital Electronics and Pulse Techniques



Course Conducted By:

Nowshin Nawar Arony
Lecturer, Dept of CSE, AUST



Chapter 2

Clipper Circuit

- A clipper circuit passes that part of an input signal which lies above or below some reference voltage.

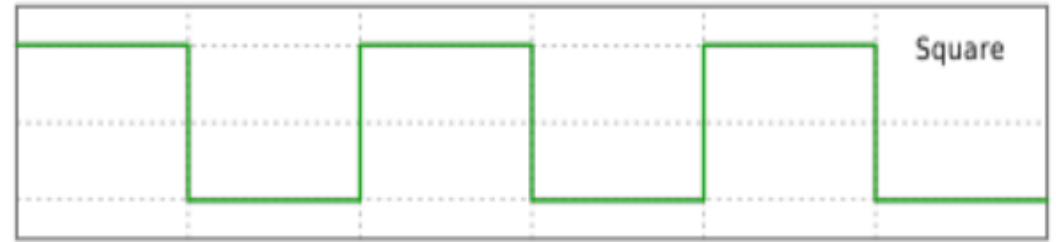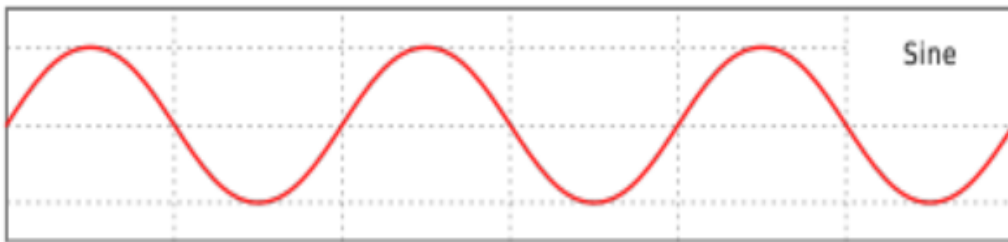


Circuit 1

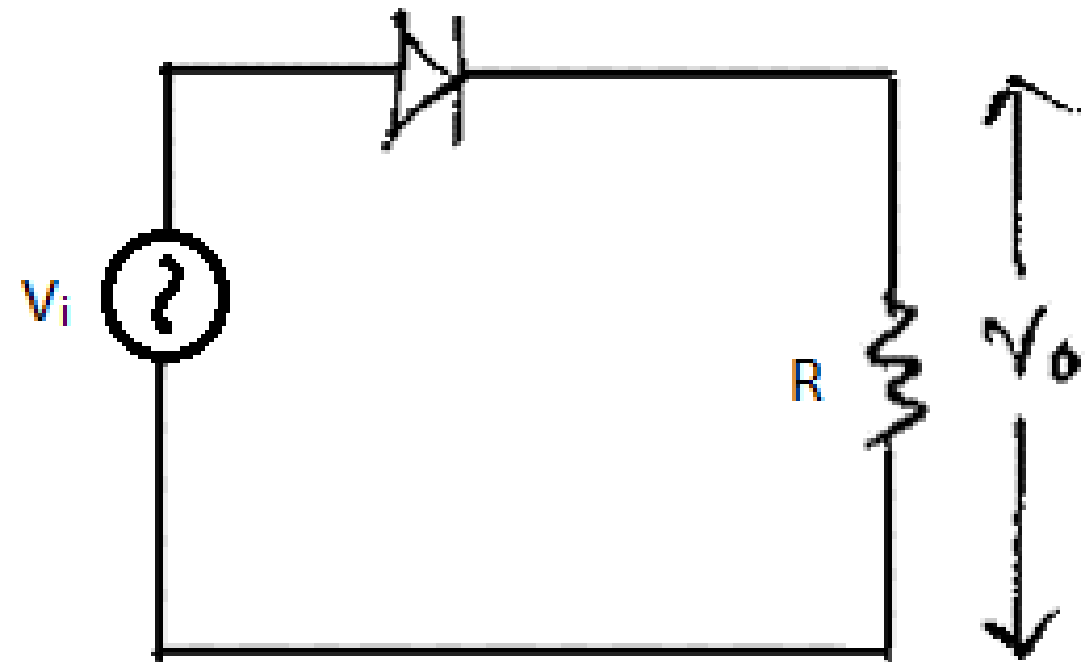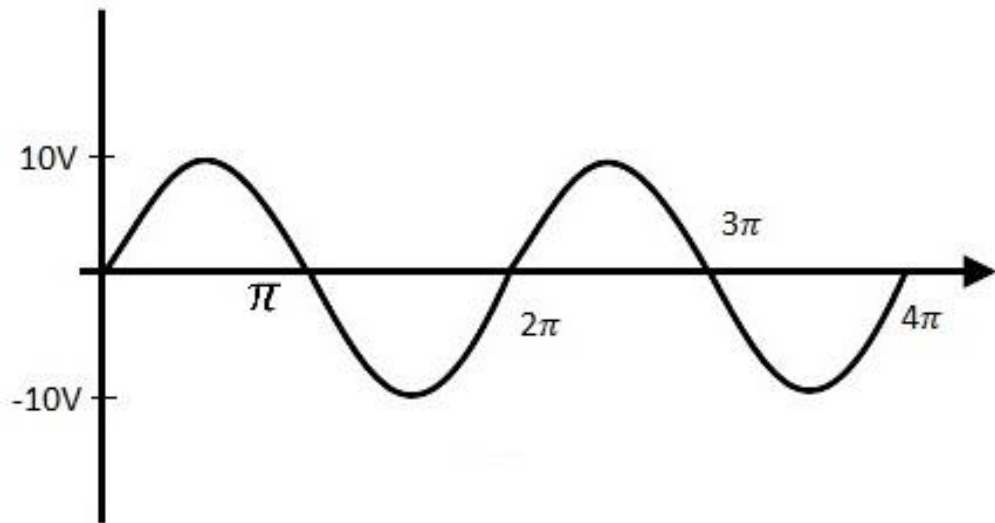

Step 1: Find conditions for diode on and off. Draw circuit ignoring resistance

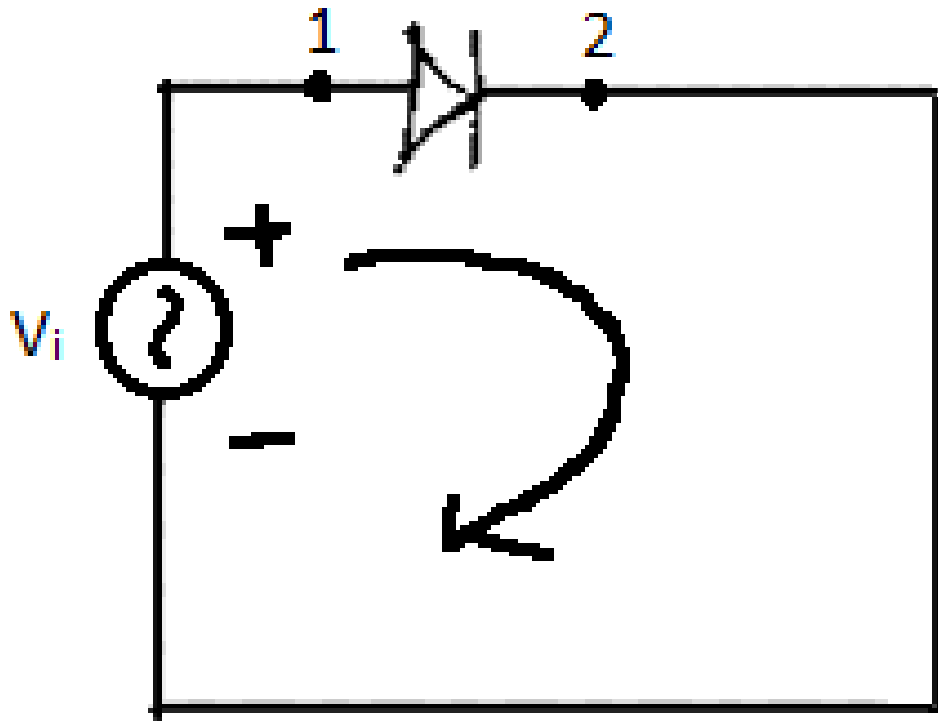
No need to consider $V_Y = 0.6$ for forward bias.




Diode ON	Diode Off
$V_{12} > 0$ $V_i > 0$	$V_{12} < 0$ $V_i < 0$

Step 2: Draw circuit and waveform for diode On and Off conditions


Diode ON

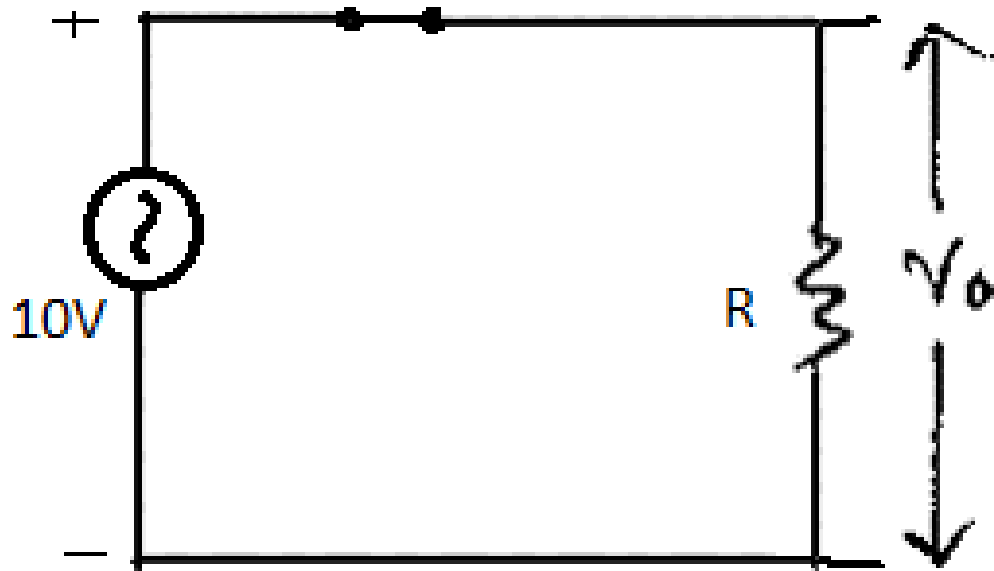


Diode Off

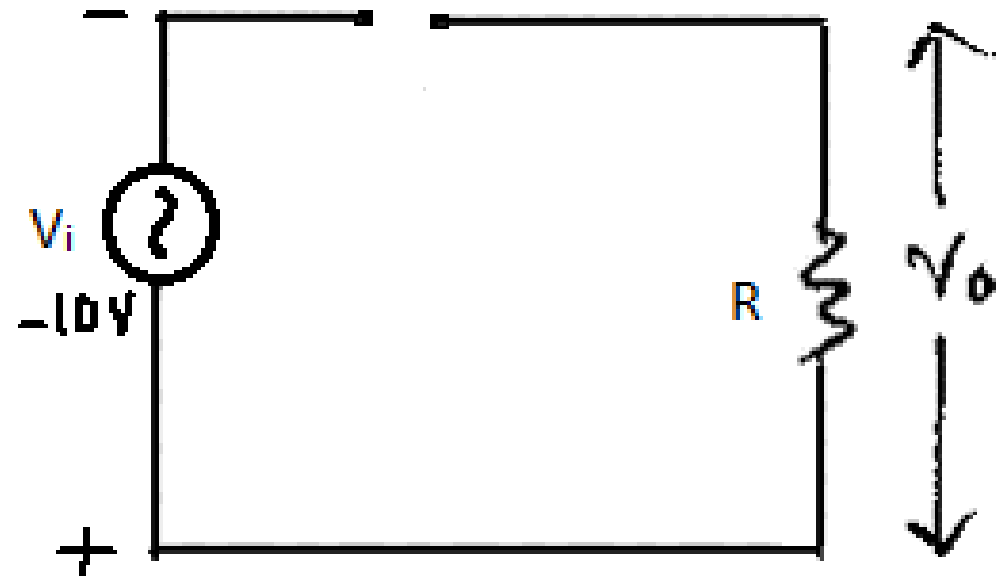



Input Wave

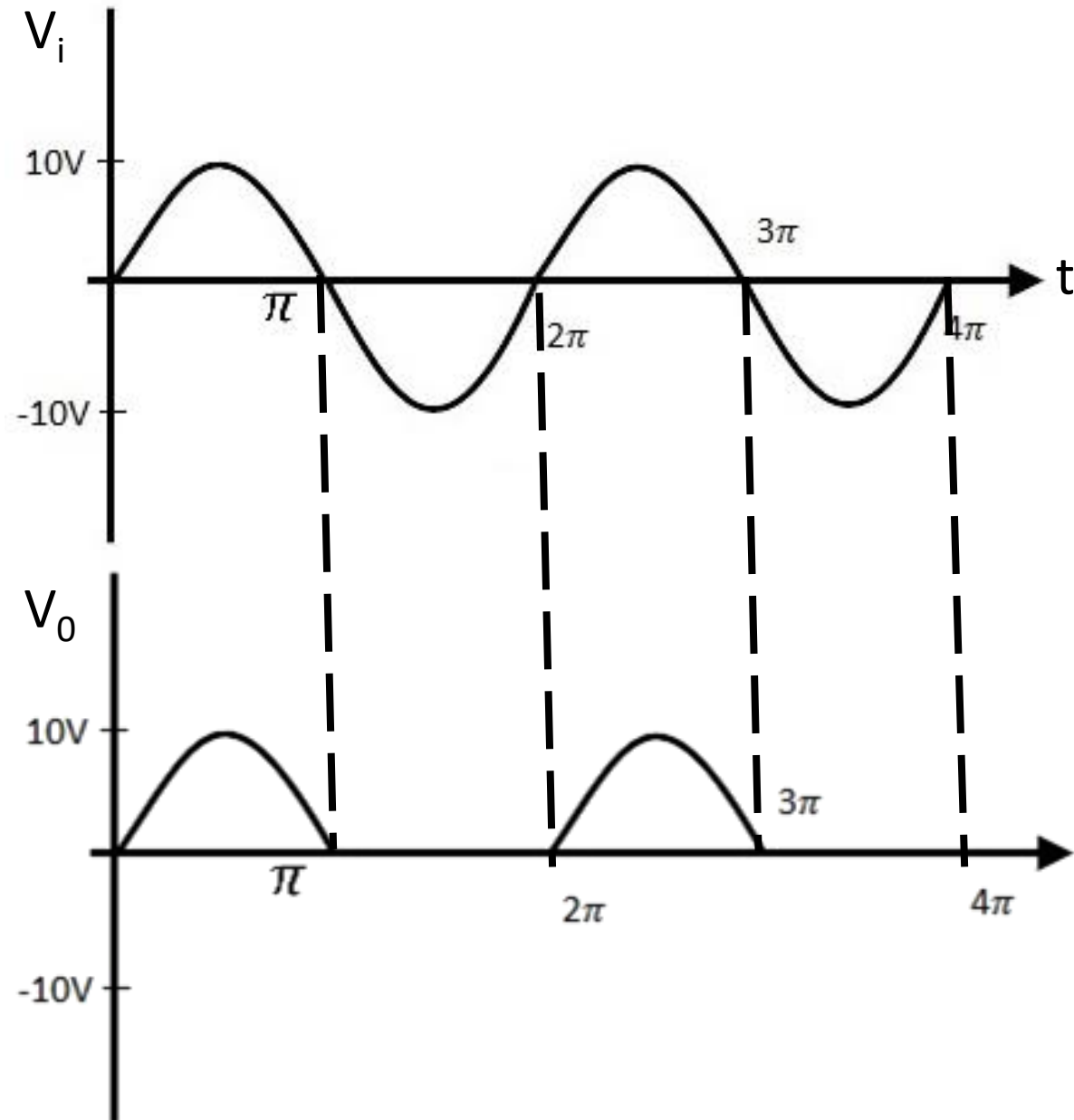


Output Wave

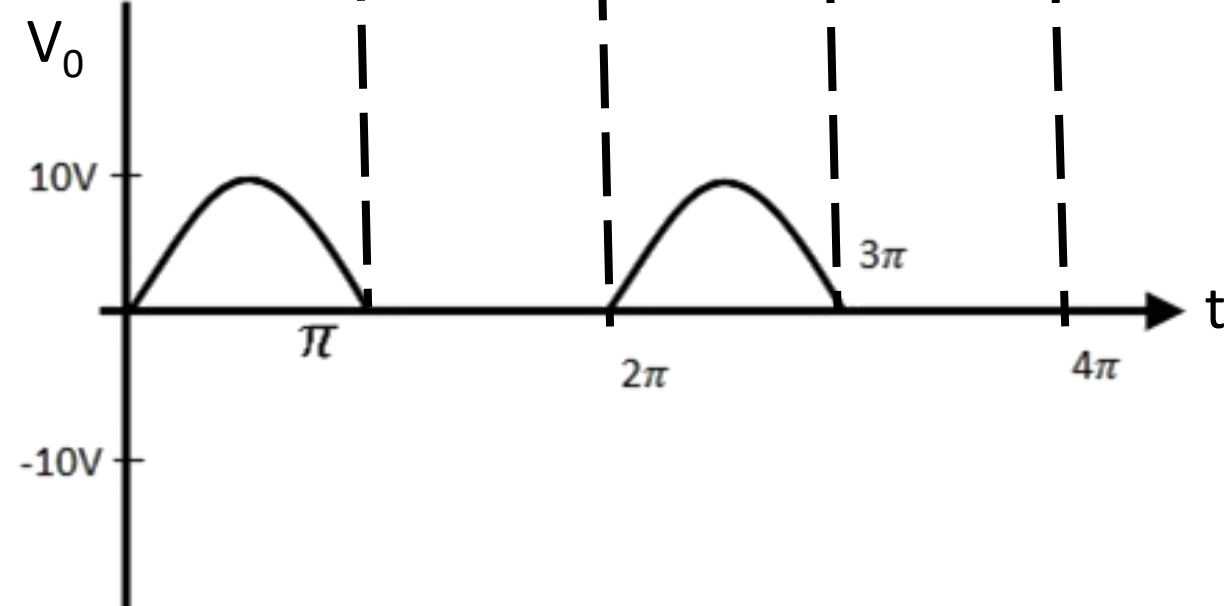

Circuit 2

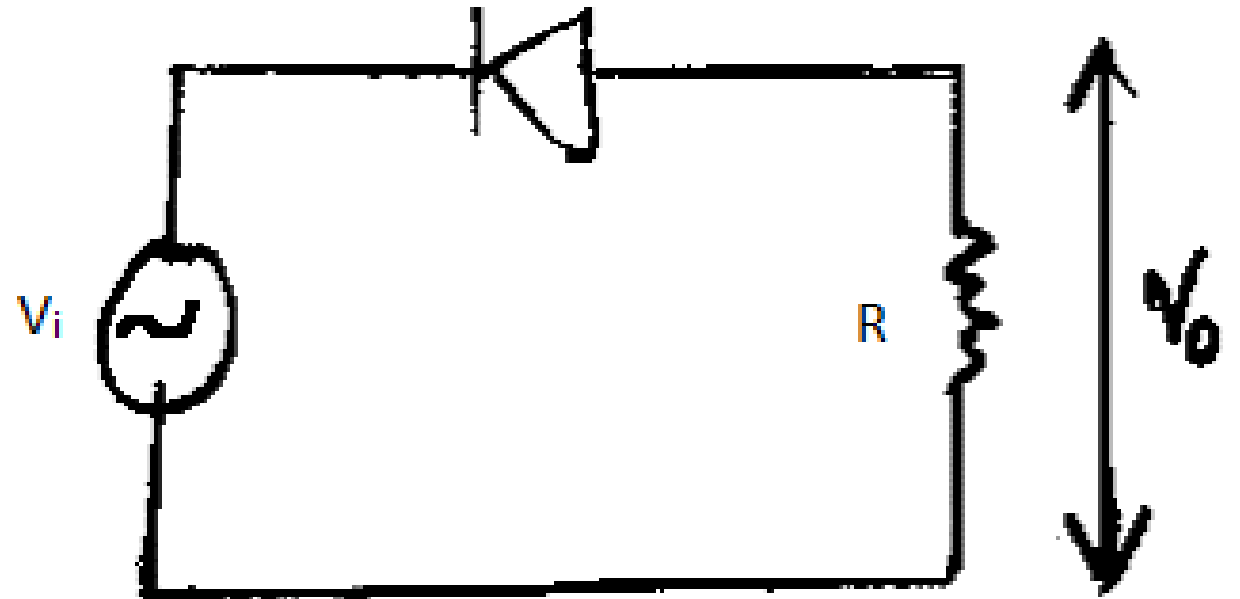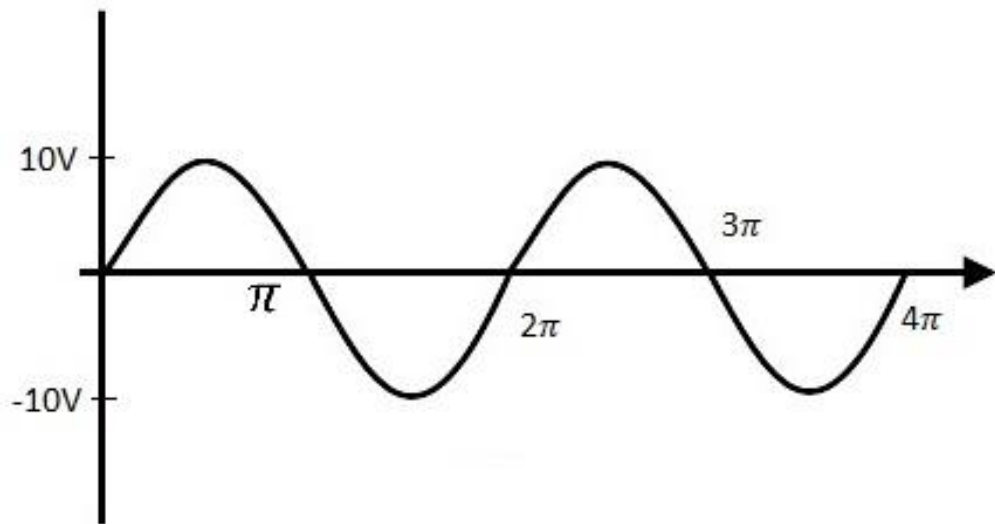


Step 1:

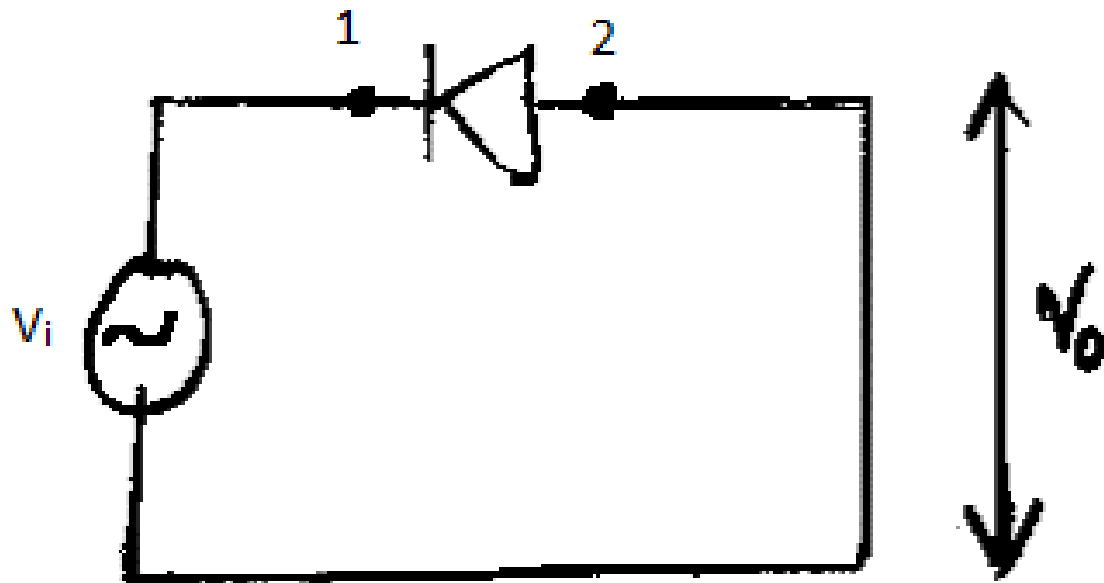

Diode ON	Diode Off
$V_{21} > 0$ $-V_{12} > 0$ $\Rightarrow V_{12} < 0$ $V_i < 0$	$V_{21} < 0$ $-V_{12} < 0$ $\Rightarrow V_{12} > 0$ $V_i > 0$


Step 2:

Diode ON

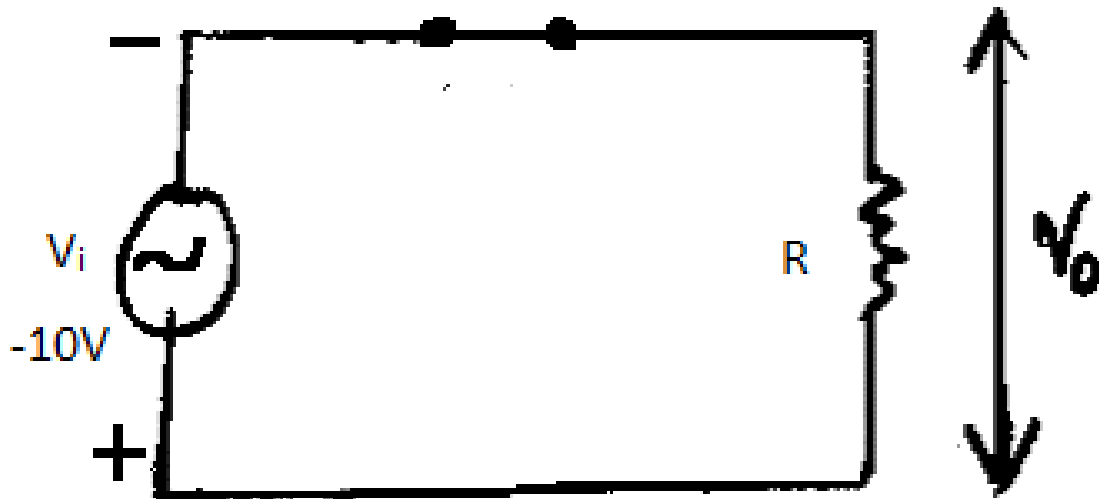


When $V_i < 0$, $V_o = V_i$

Diode Off

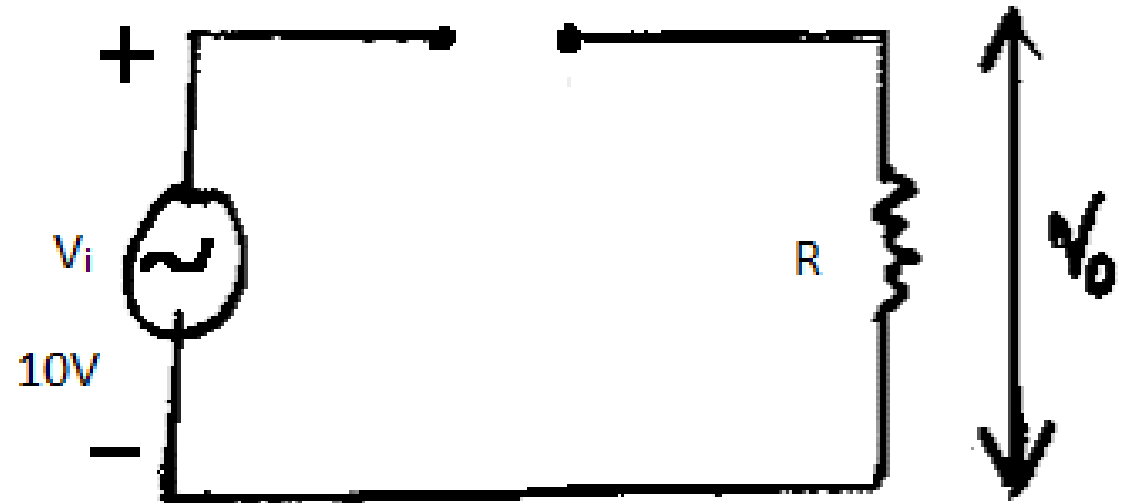


When $V_i > 0$, $V_o = 0V$

Input Wave

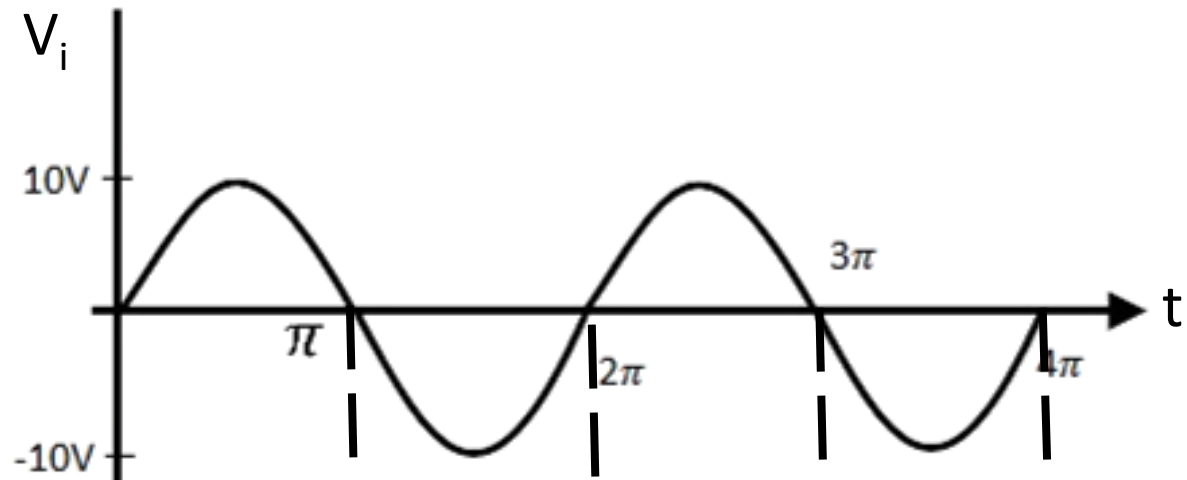



Output Wave

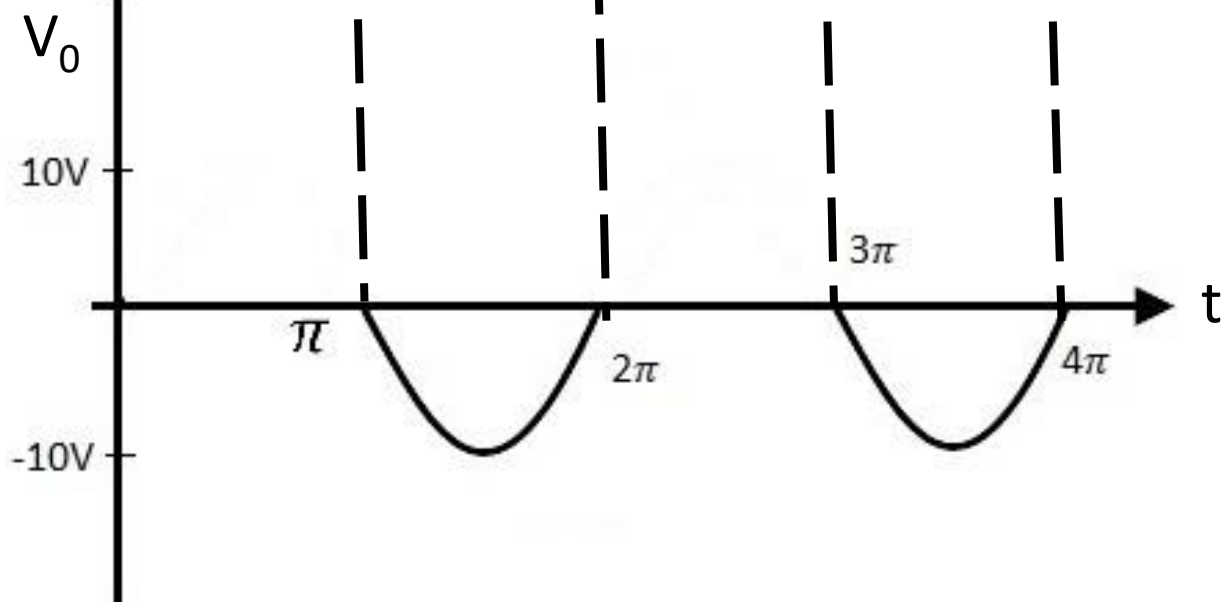


Output Voltage

$V_i < 0$	$V_i > 0$
$V_o = V_i$	$V_o = 0 \text{ V}$

Circuit 3

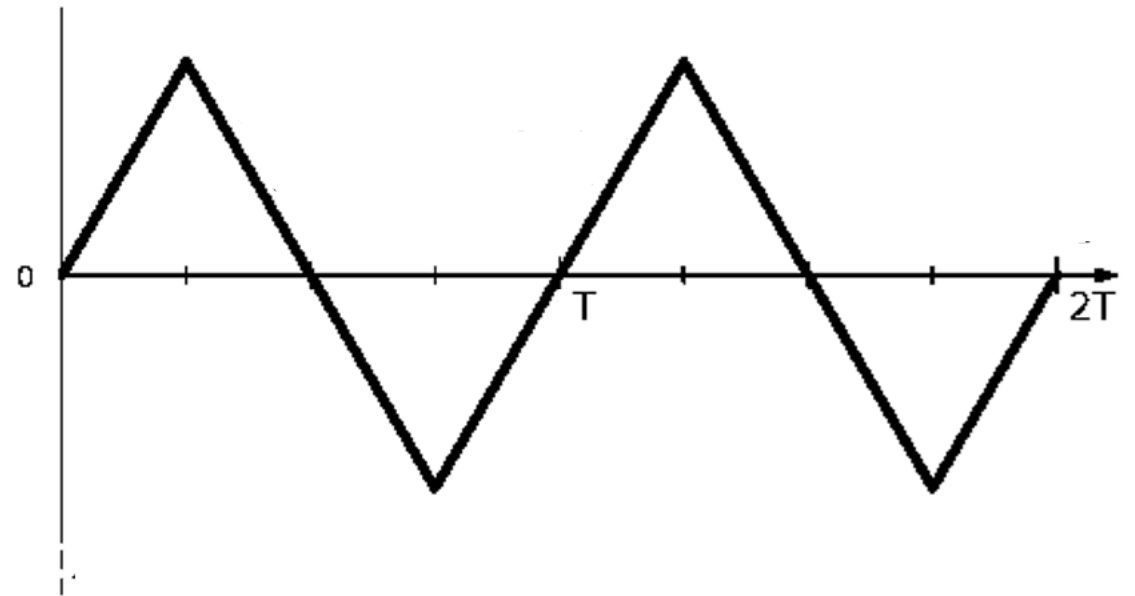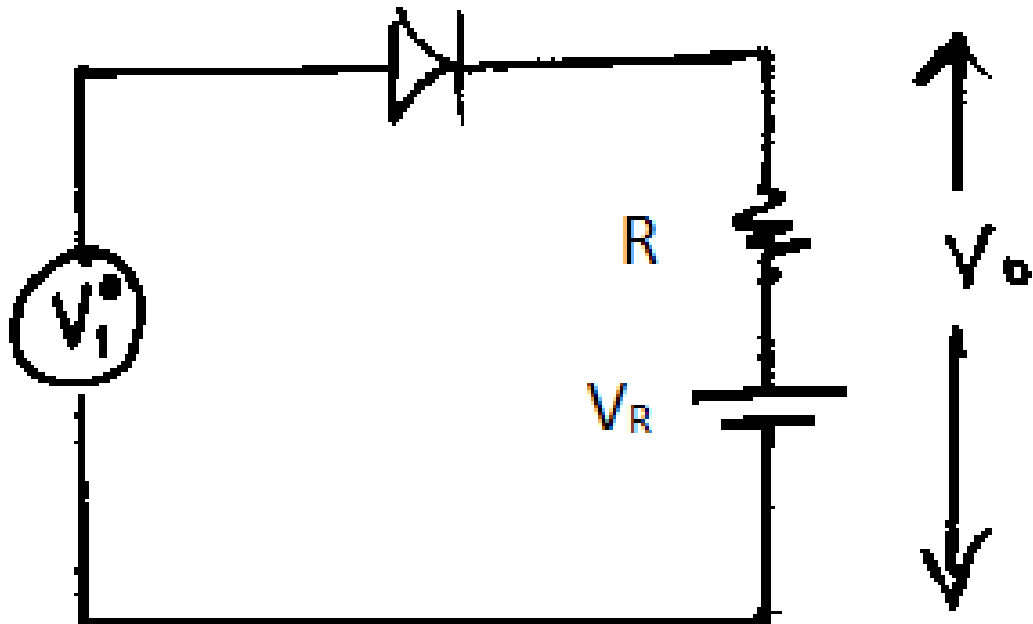

Step 1:

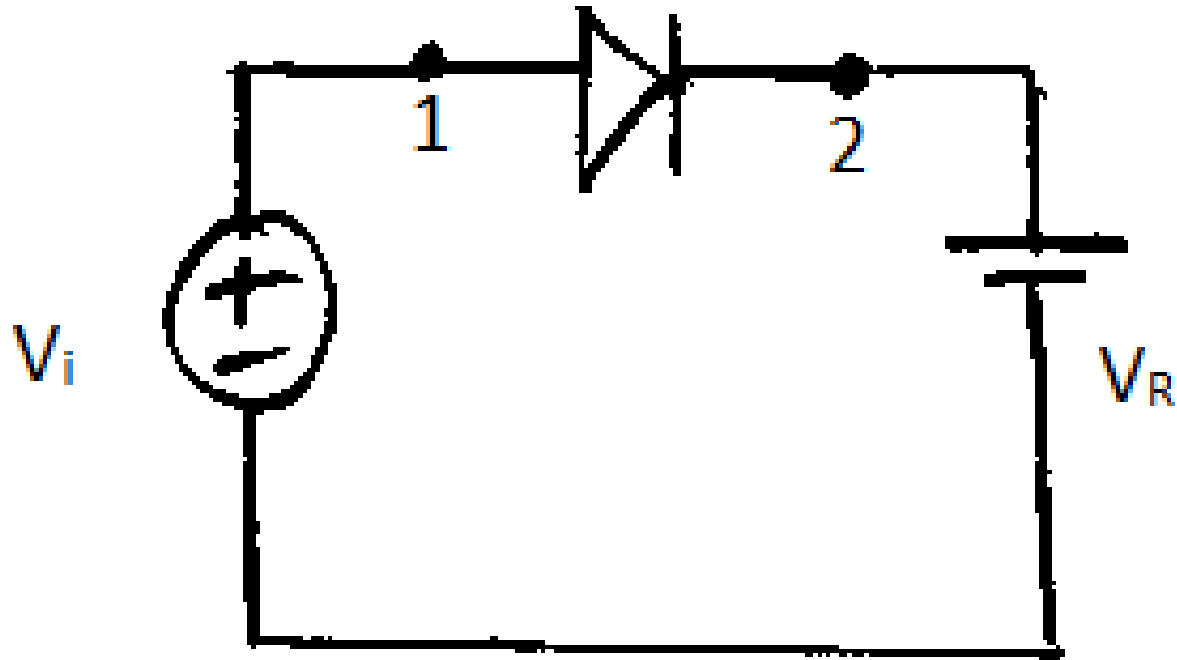


Output Equation,

Applying KVL,

$$-V_i + V_{12} + V_R = 0$$
$$V_{12} = V_i - V_R$$

Step 1:

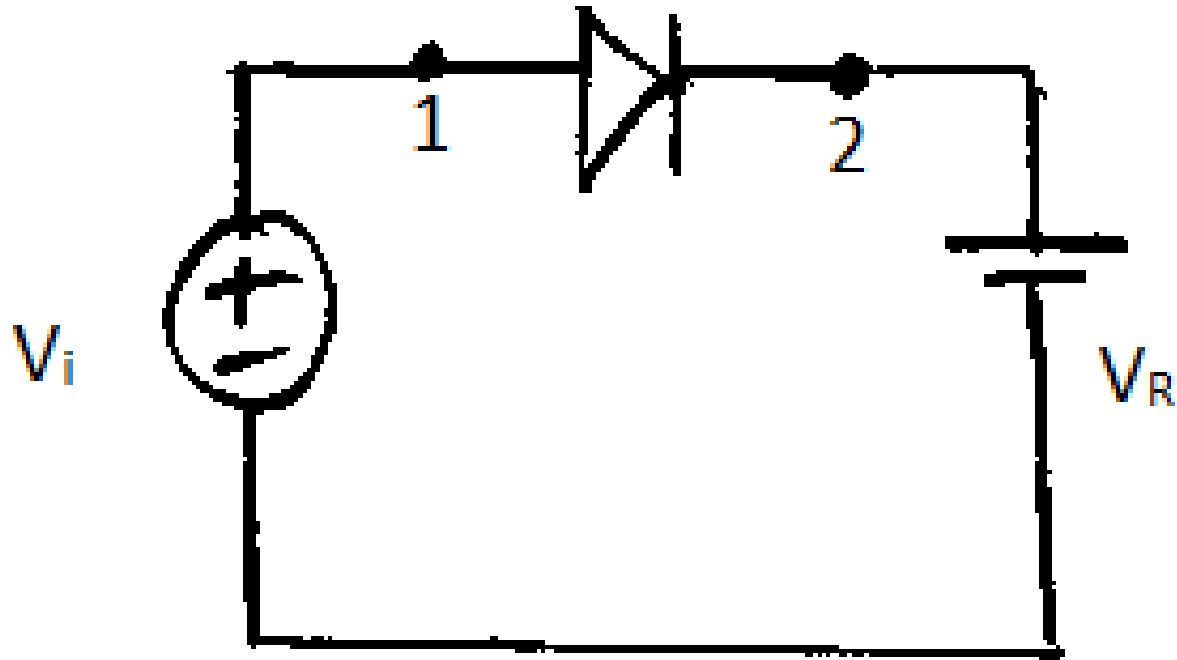

Diode ON


When $V_{12} > 0$

So,

$$V_i - V_R > 0$$

$$V_i > V_R$$

Step 1:

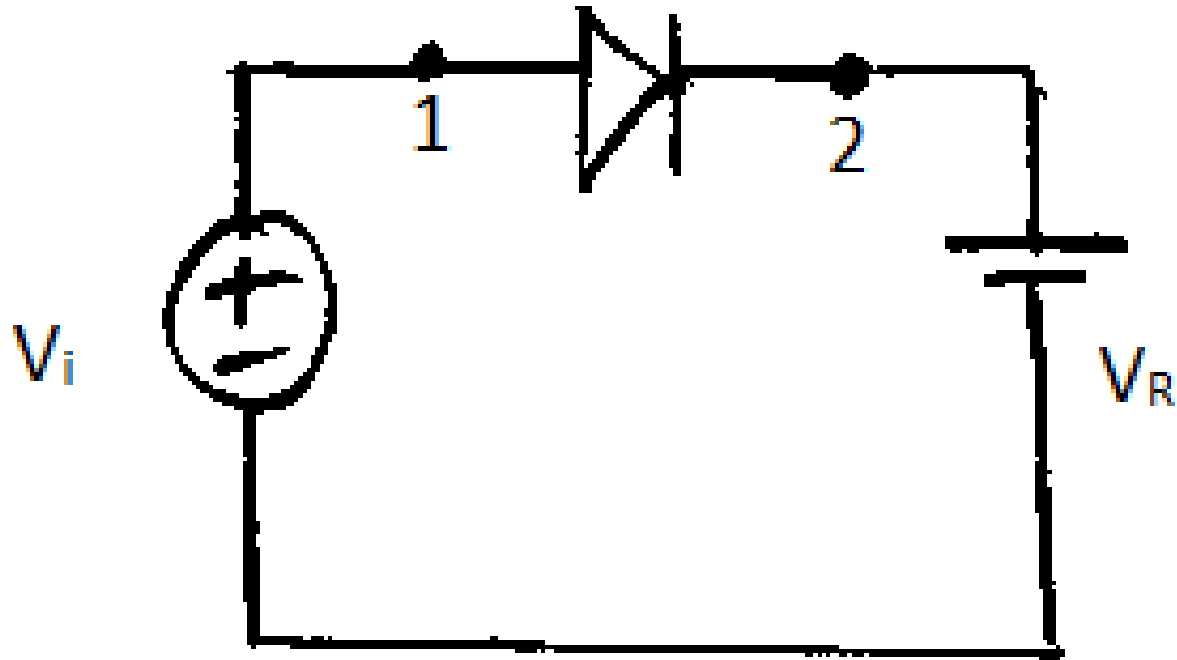

Diode OFF

When $V_{12} < 0$


So,

$$V_i - V_R < 0$$

$$V_i < V_R$$

Step 2:


Diode ON

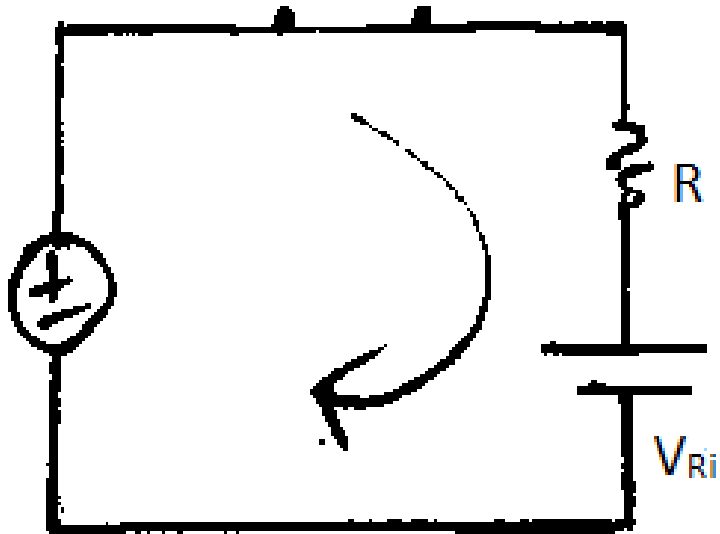

$$V_0 = V_i$$

When $V_i > V_R$, $V_0 = V_i$


Diode Off

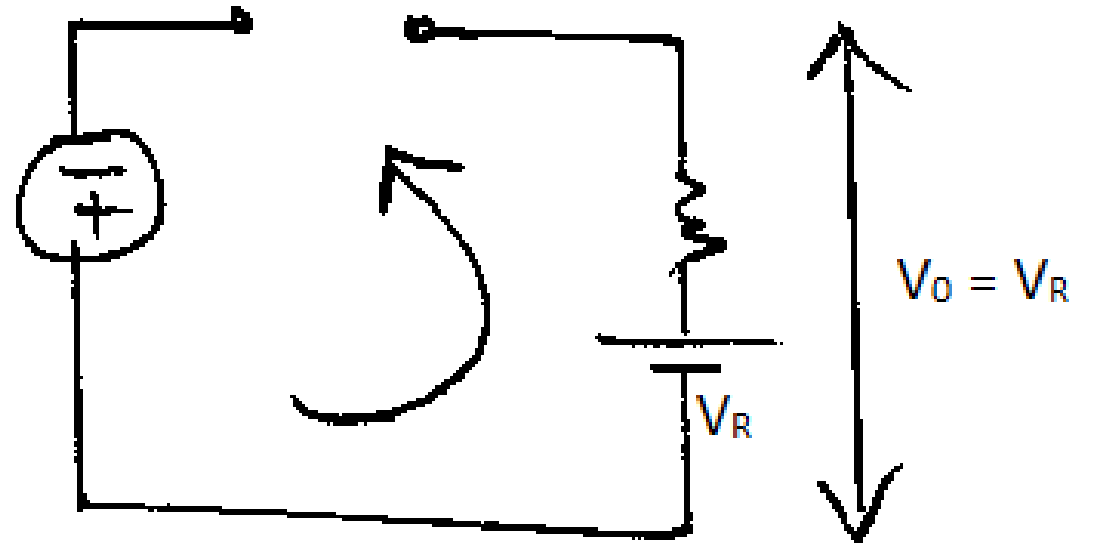

$$V_0 = V_R$$

When $V_i < V_R$, $V_0 = V_R$


Input Wave

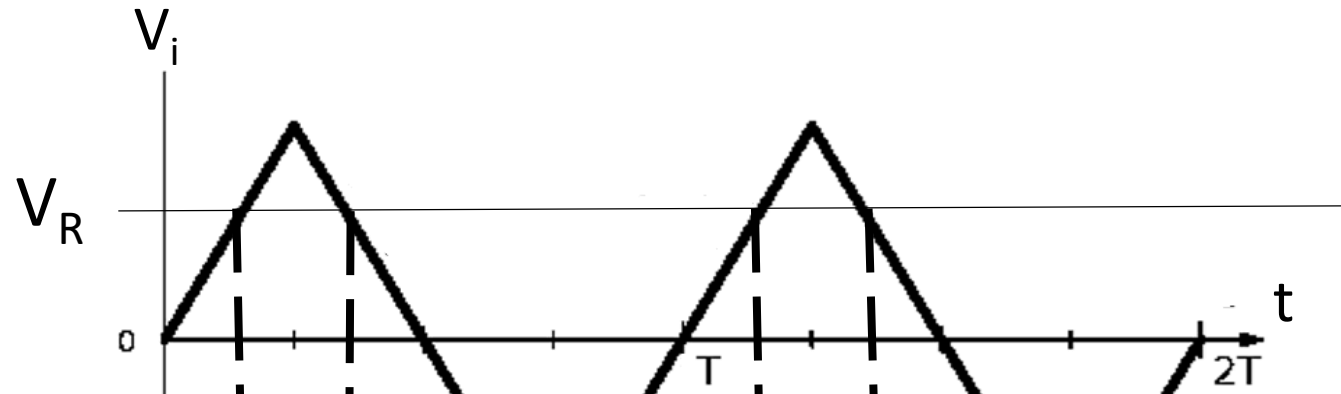


Output Voltage

$V_i < V_R$	$V_i > V_R$
$V_0 = V_R$	$V_0 = V_i$


Output Wave

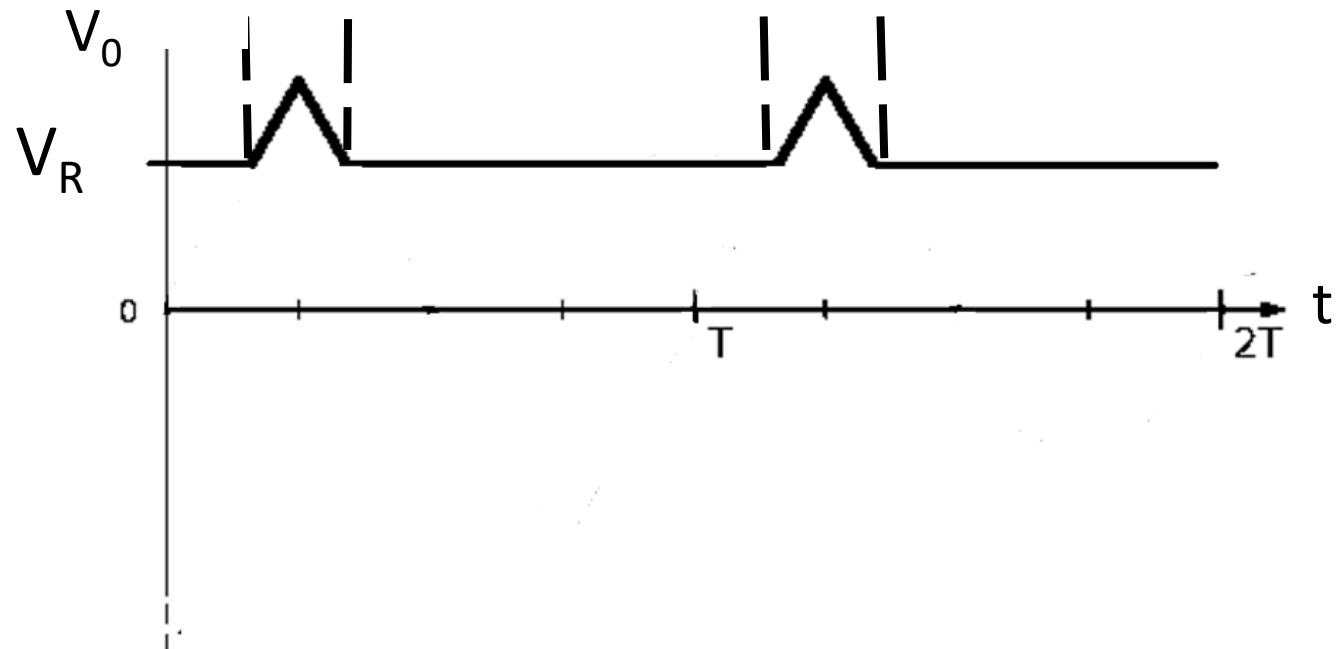

Input Wave

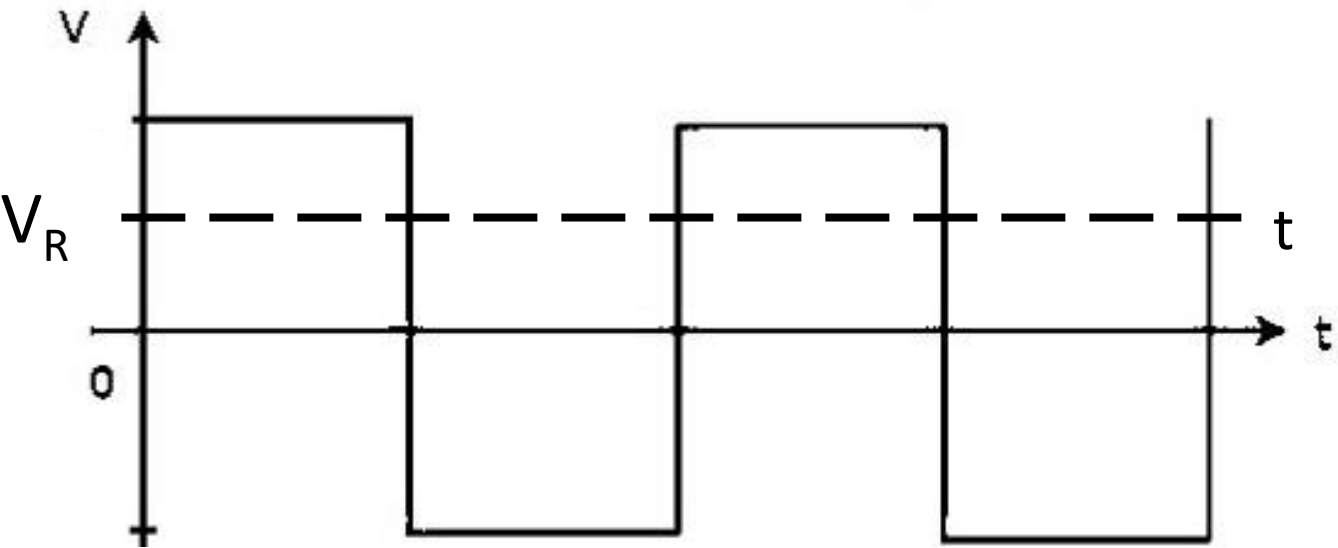



Output Wave

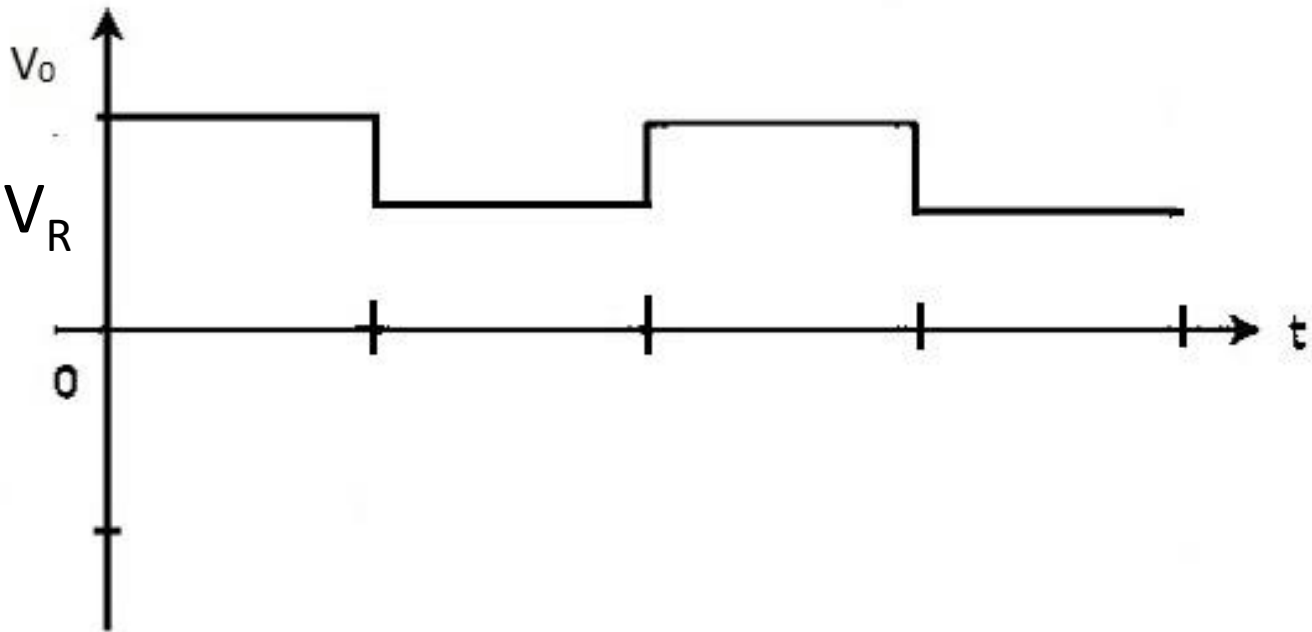


Output Voltage

$V_i < V_R$	$V_i > V_R$
$V_o = V_R$	$V_o = V_i$

Circuit 4

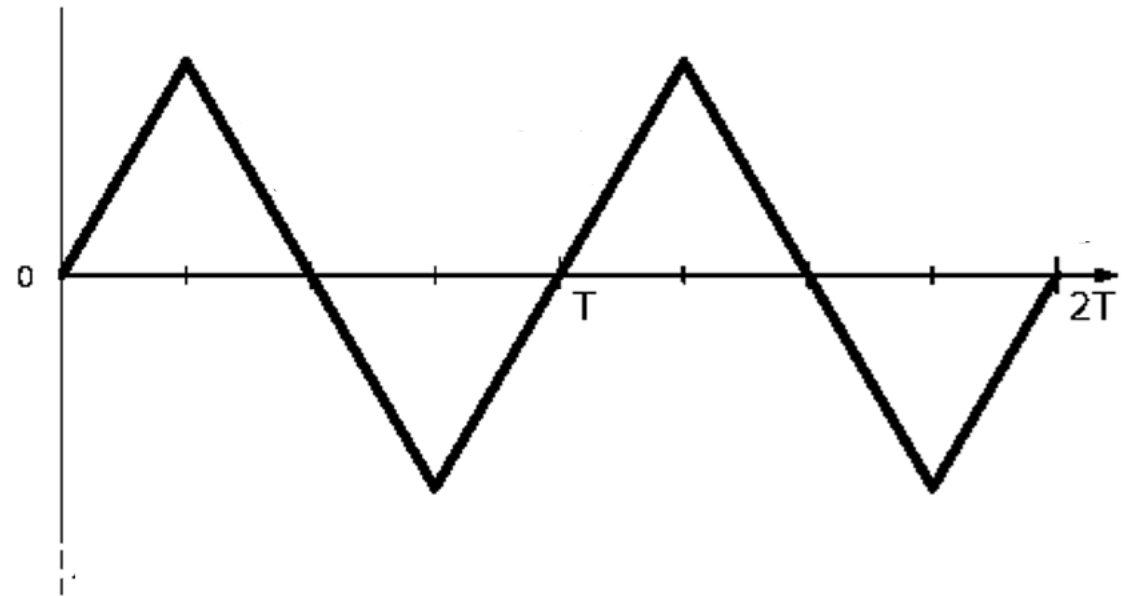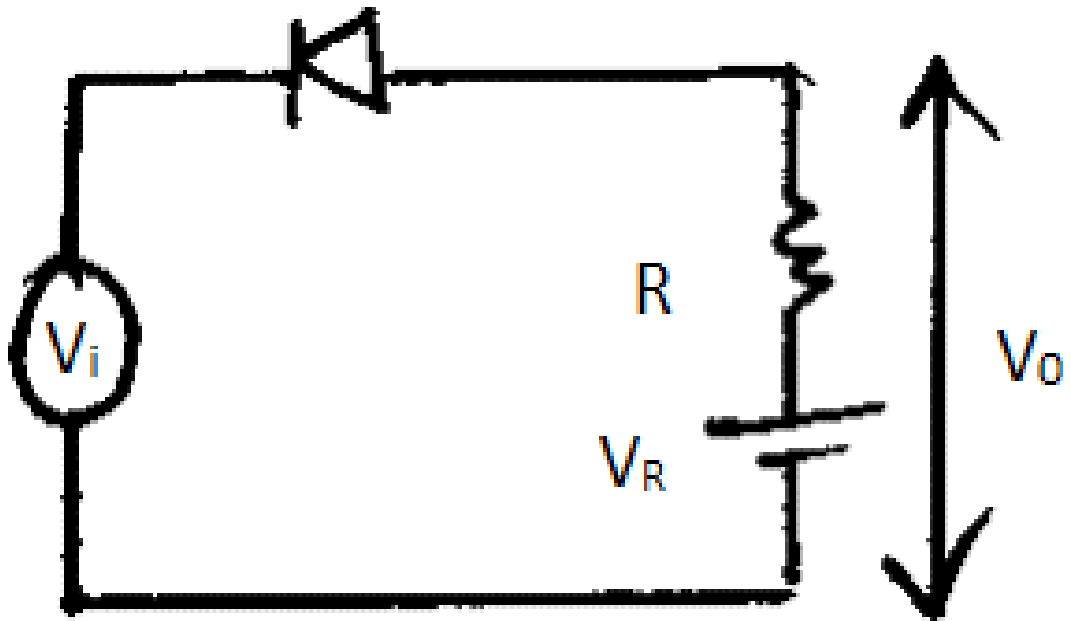

Step 1:

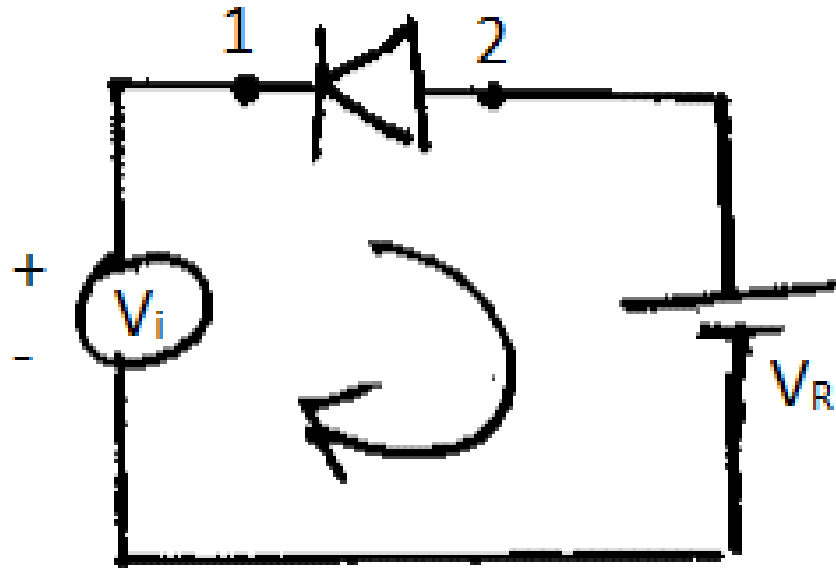


Output Equation,

Applying KVL,

$$-V_i - V_{12} + V_R = 0$$

$$-V_{12} = V_i - V_R$$


$$\Rightarrow V_{21} = V_i - V_R$$

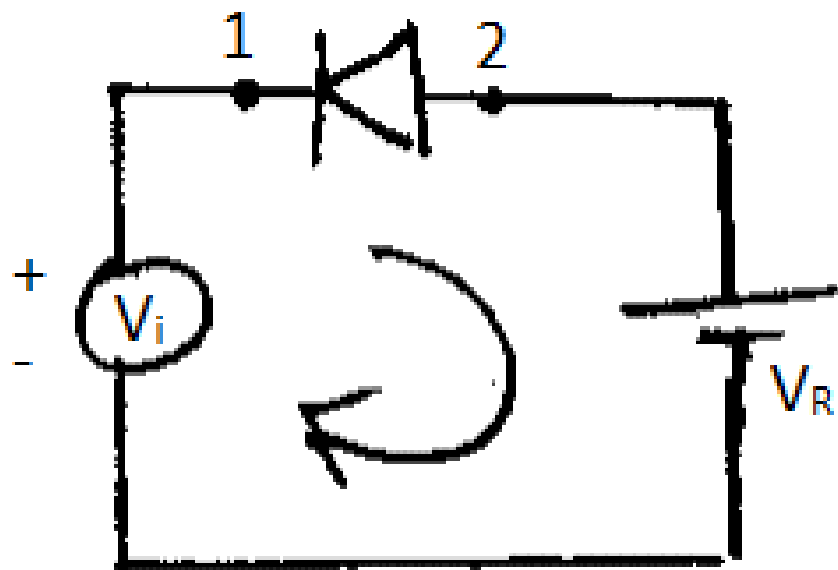

Diode ON	Diode Off
$V_{12} < 0$ $V_{21} > 0$ $\Rightarrow V_{21} > 0$ $V_i - V_R > 0$ $V_i > V_R$	$V_{12} > 0$ $V_{21} < 0$ $\Rightarrow V_{21} < 0$ $V_i - V_R < 0$ $V_i < V_R$


Step 2:

Diode ON

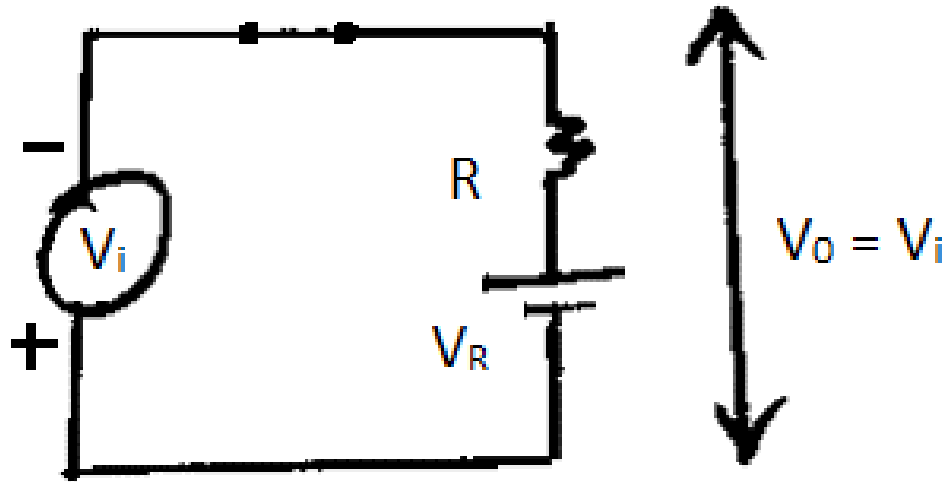


When $V_i < V_R$, $V_0 = V_i$

Diode Off

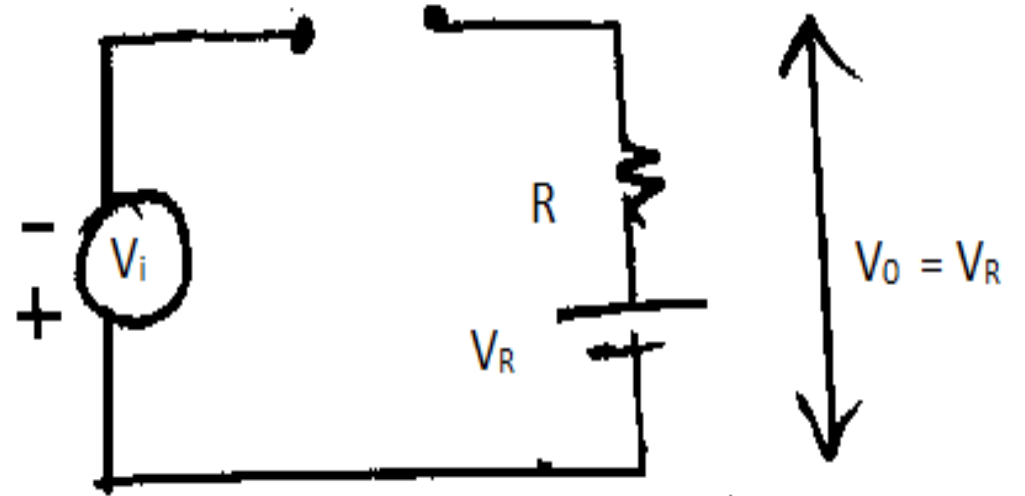


When $V_i > V_R$, $V_0 = V_R$

Input Wave

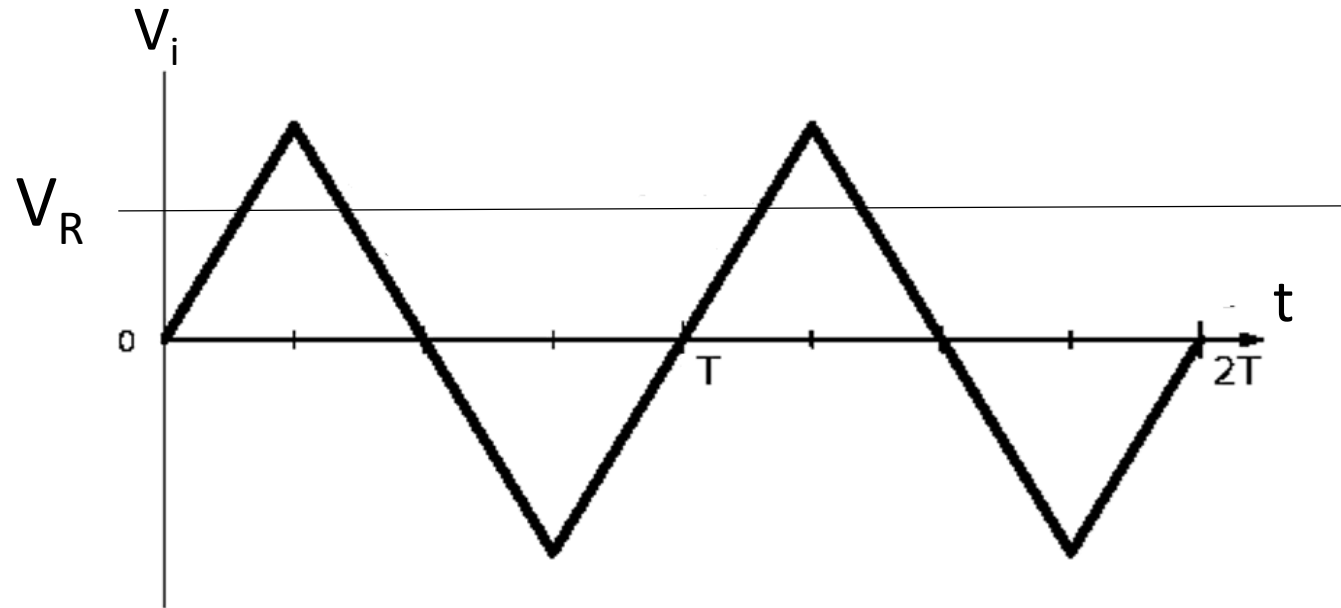



Output Wave

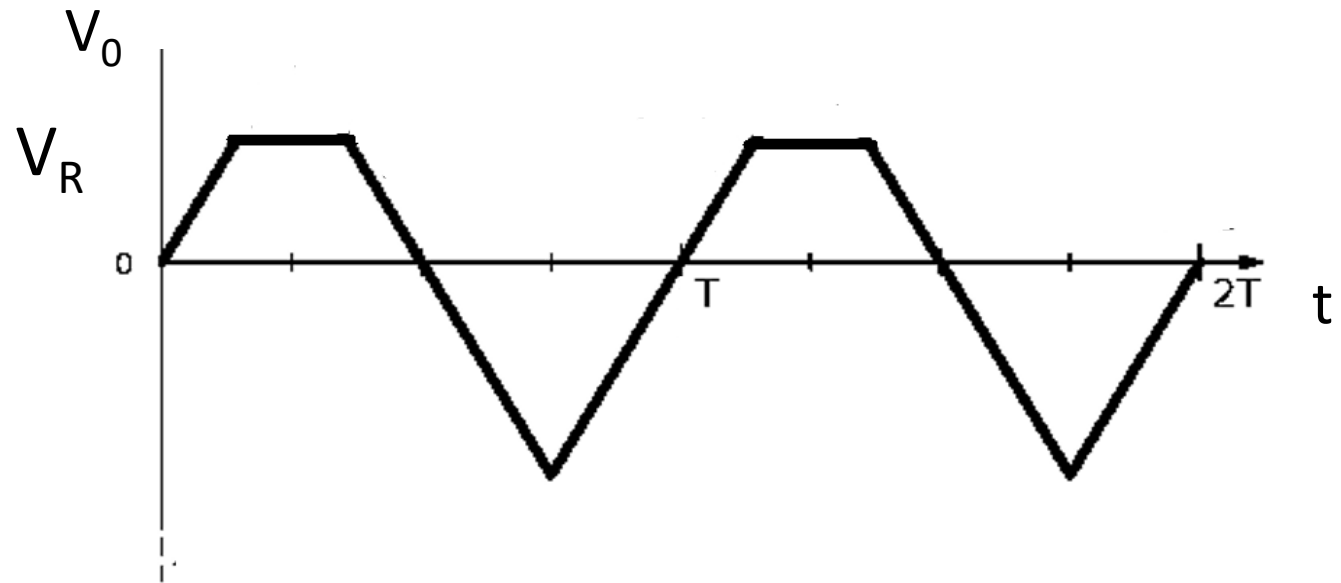


Output Voltage

$V_i > V_R$	$V_i < V_R$
$V_0 = V_R$	$V_0 = V_i$

Circuit 5

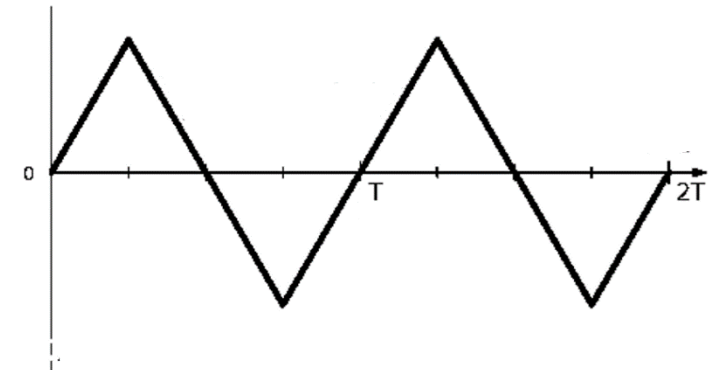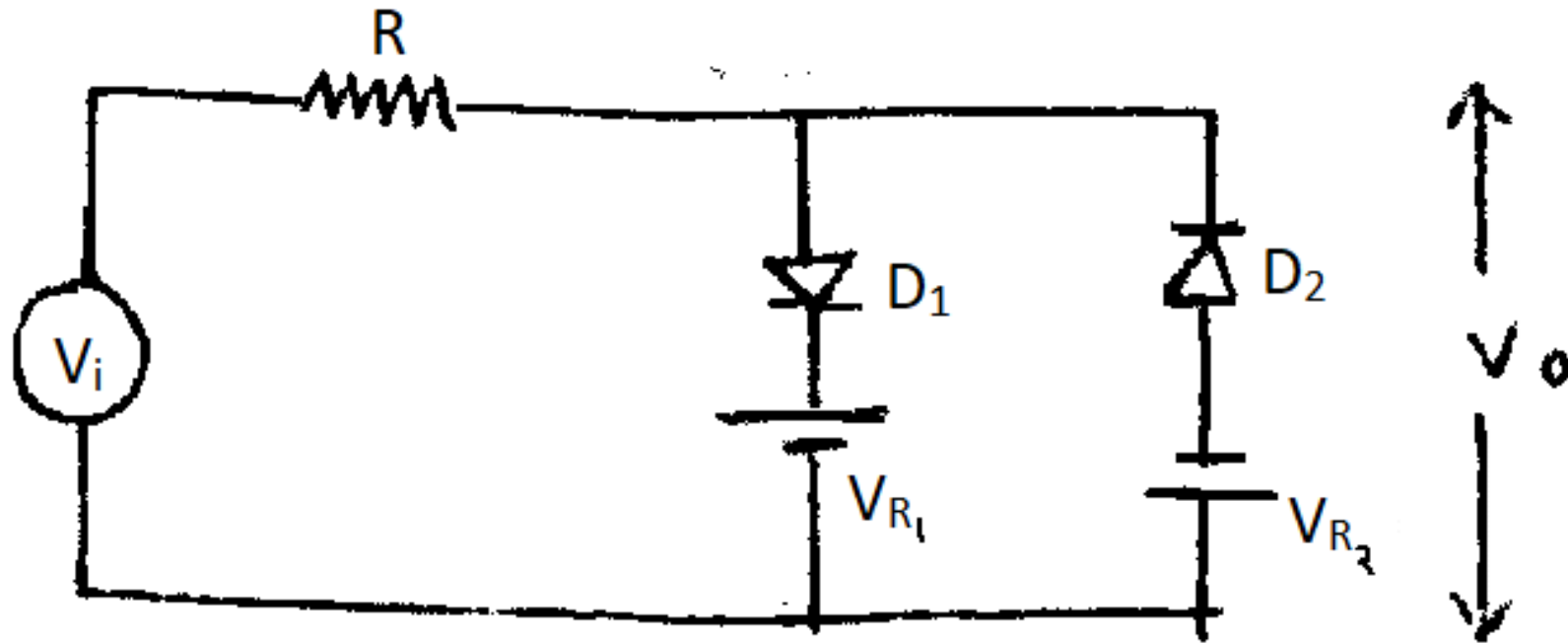


Step 1:

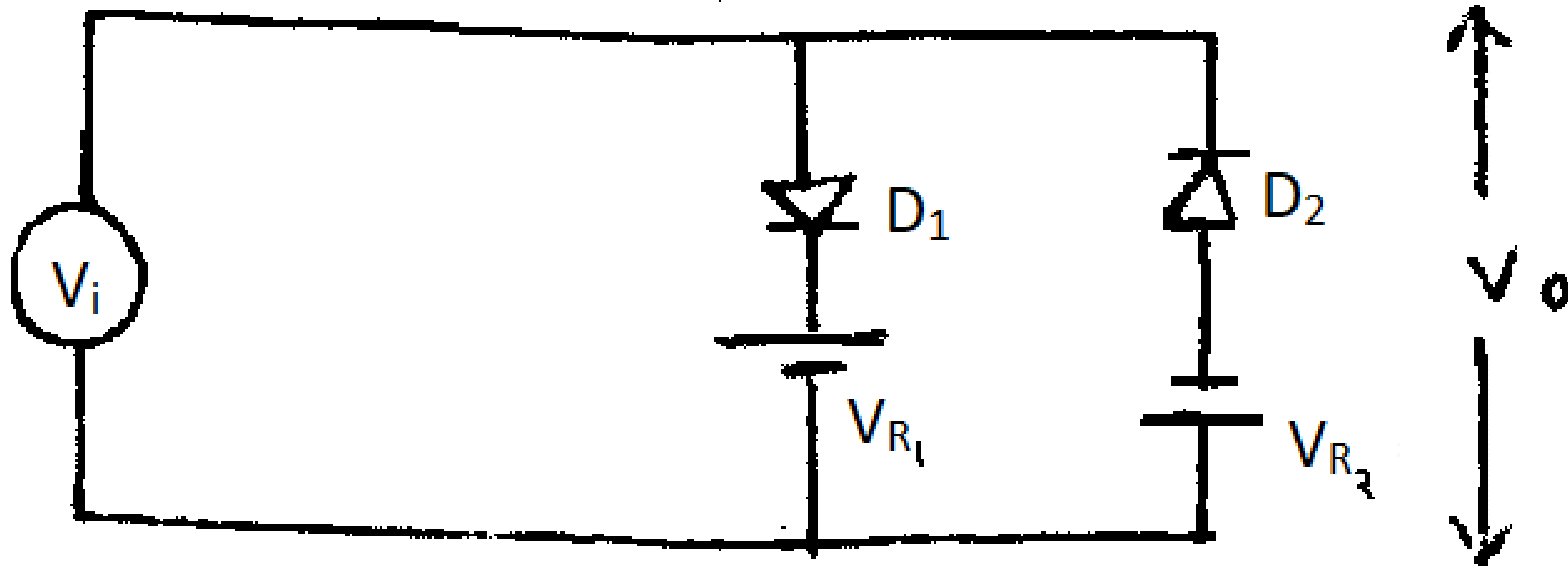


Step 2: Draw circuit and waveform for diode On and Off conditions


For D_1

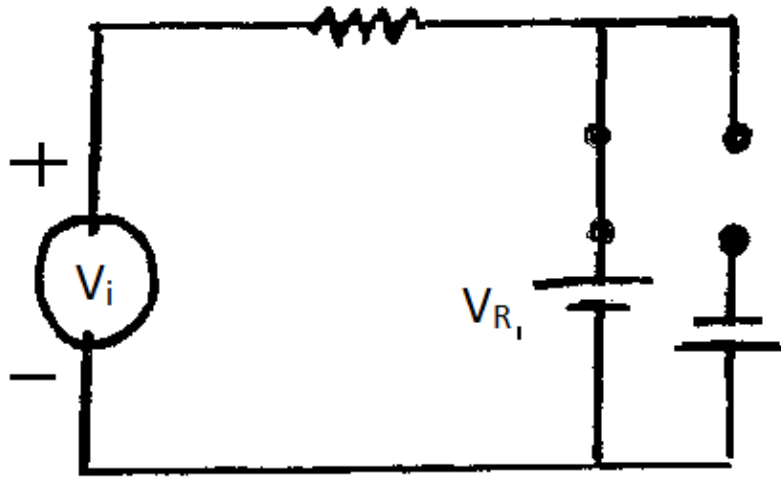

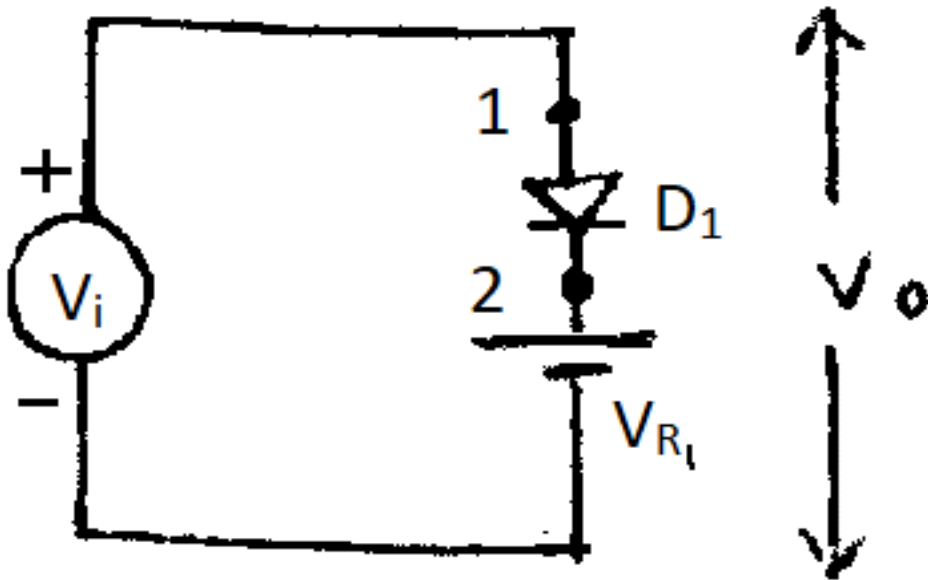Applying KVL,
 $-V_i + V_{12} + V_{R1} = 0$
 $V_{12} = V_i - V_{R1}$



Diode ON	Diode Off
$V_{12} > 0$ $V_i - V_{R1} > 0$ $V_i > V_{R1}$	$V_{12} < 0$ $V_i - V_{R1} < 0$ $V_i < V_{R1}$

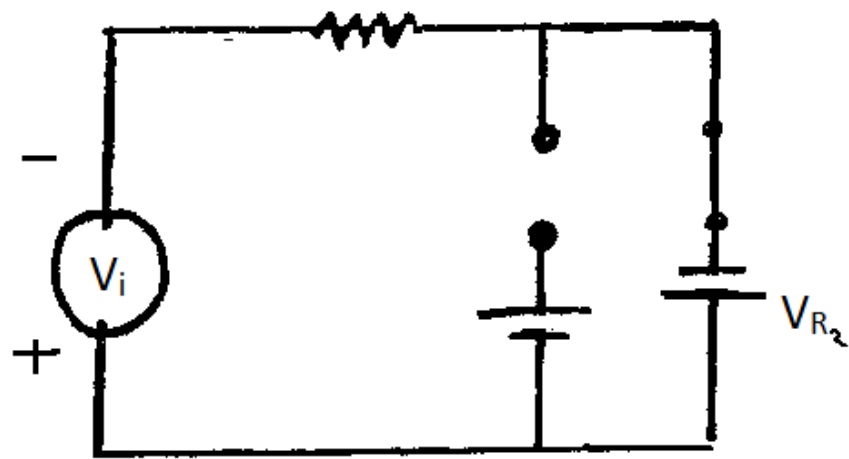


For D_2

Applying KVL,


$$-V_i - V_{34} + V_{R2} = 0$$

$$V_{34} = -V_i + V_{R2}$$


D_2 is ON

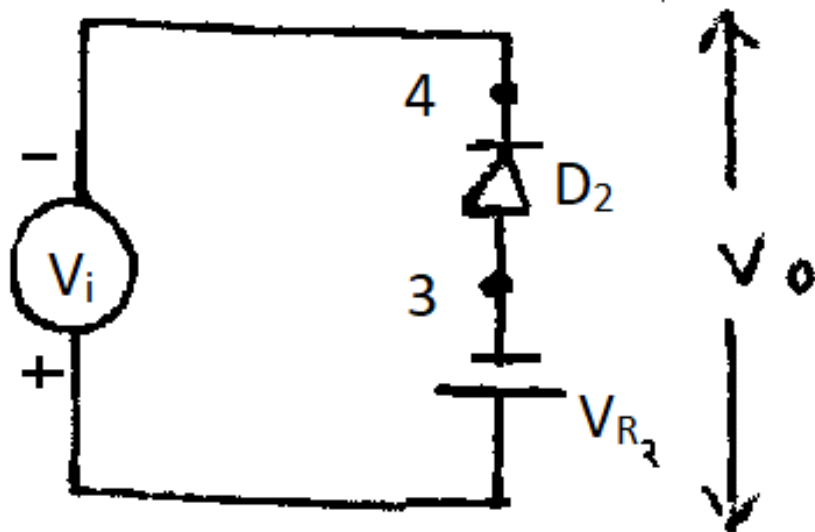


Diode ON	Diode Off
$V_{34} > 0$ $-V_i + V_{R2} > 0$ $V_i < V_{R2}$	$V_{34} < 0$ $-V_i + V_{R2} < 0$ $V_i > V_{R2}$

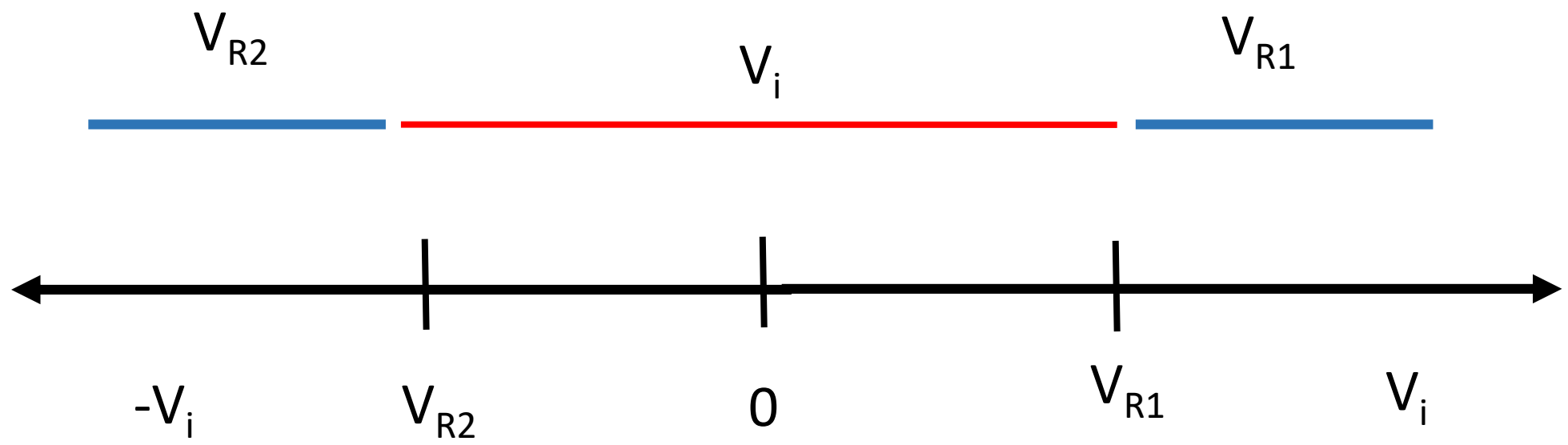

Input Wave

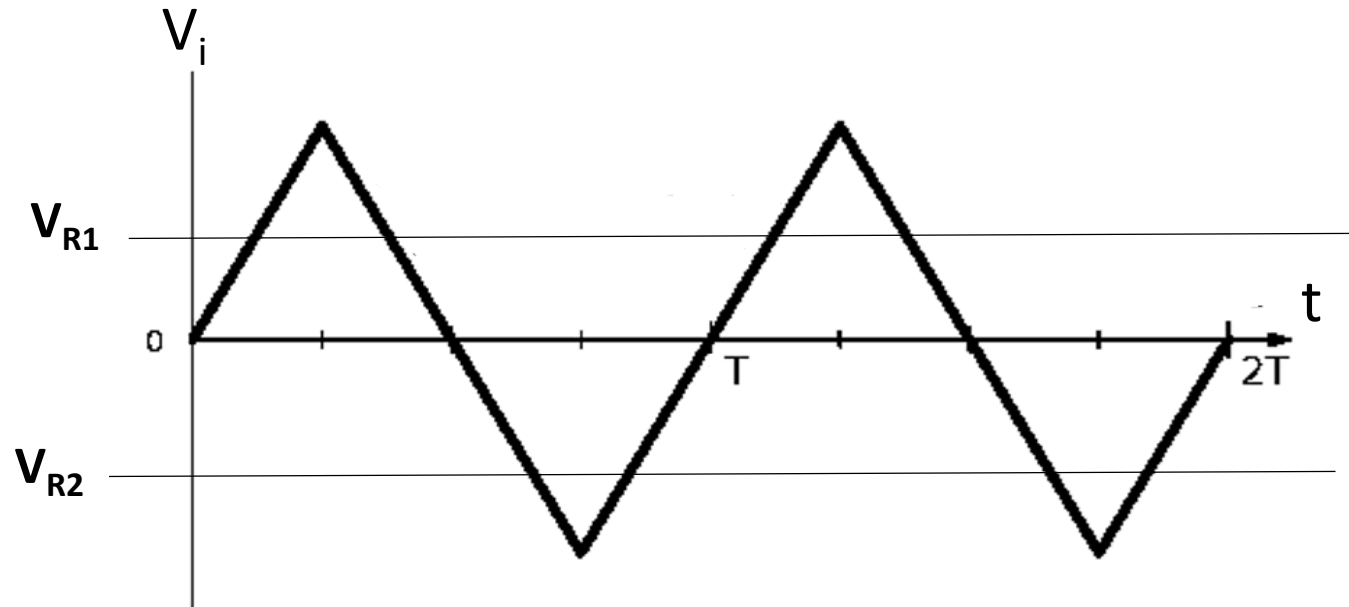

Output Wave

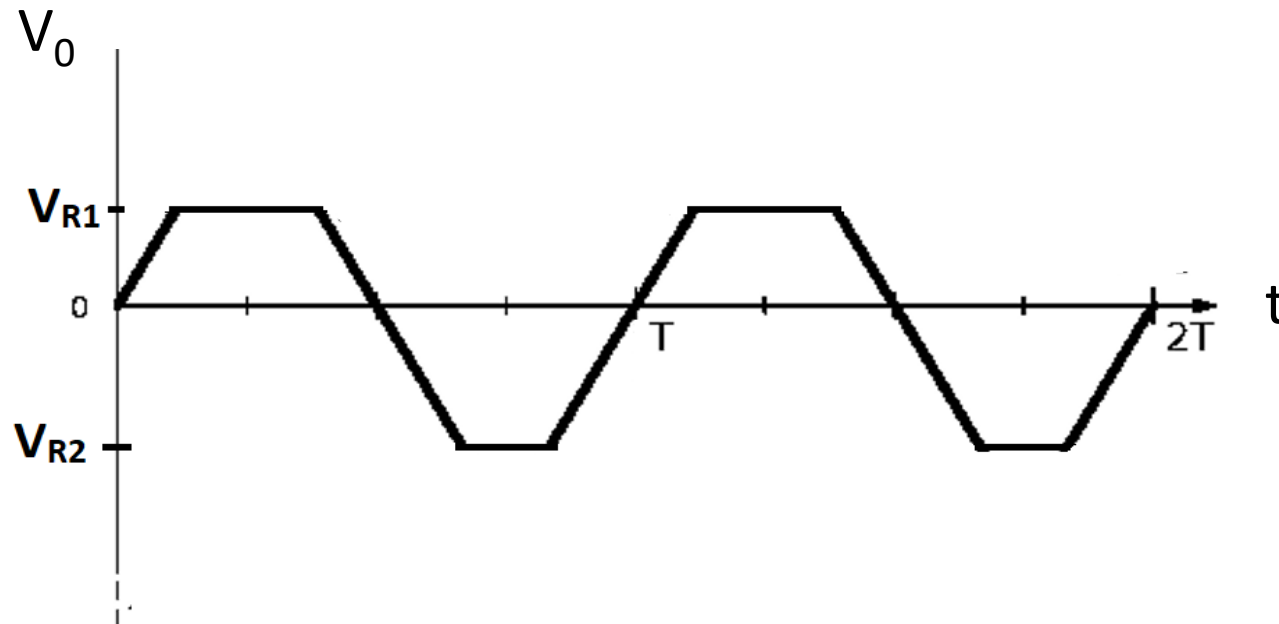

Output Voltage

When

$$V_i < V_{R2}$$

$$V_0 = V_{R2}$$

When

$$V_{R2} < V_i < V_{R1}$$

Then,

$$V_0 = V_i$$

When

$$V_i > V_{R1}$$

$$V_0 = V_{R1}$$

Try yourself

