

**FIGURE 3-1** A positive input voltage is applied to the (-) input of an inverting amplifier.  $R_i$  converts this voltage to a current,  $I$ ;  $R_f$  converts  $I$  back into an amplified version of  $E_i$ .

0 V, so ground potential is at the (-) input. For this reason, the (-) input is said to be at virtual ground.

### Example 3-1

For Fig. 3-1, let  $R_f = 100 \text{ k}\Omega$ ,  $R_i = 10 \text{ k}\Omega$ , and  $E_i = 1 \text{ V}$ . Calculate (a)  $I$ ; (b)  $V_o$ ; (c)  $A_{CL}$ .

Solution (a) From Eq. (3-1a),

$$I = \frac{E_i}{R_i} = \frac{1 \text{ V}}{10 \text{ k}\Omega} = 0.1 \text{ mA}$$

(b) From Eq. (3-2a),


$$V_o = -\frac{R_f}{R_i} \times E_i = -\frac{100 \text{ k}\Omega}{10 \text{ k}\Omega} (1 \text{ V}) = -10 \text{ V}$$

(c) Using Eq. (3-2b), we obtain

$$A_{CL} = -\frac{R_f}{R_i} = -\frac{100 \text{ k}\Omega}{10 \text{ k}\Omega} = -10$$

This answer may be checked by taking the ratio of  $V_o$  to  $E_i$ :
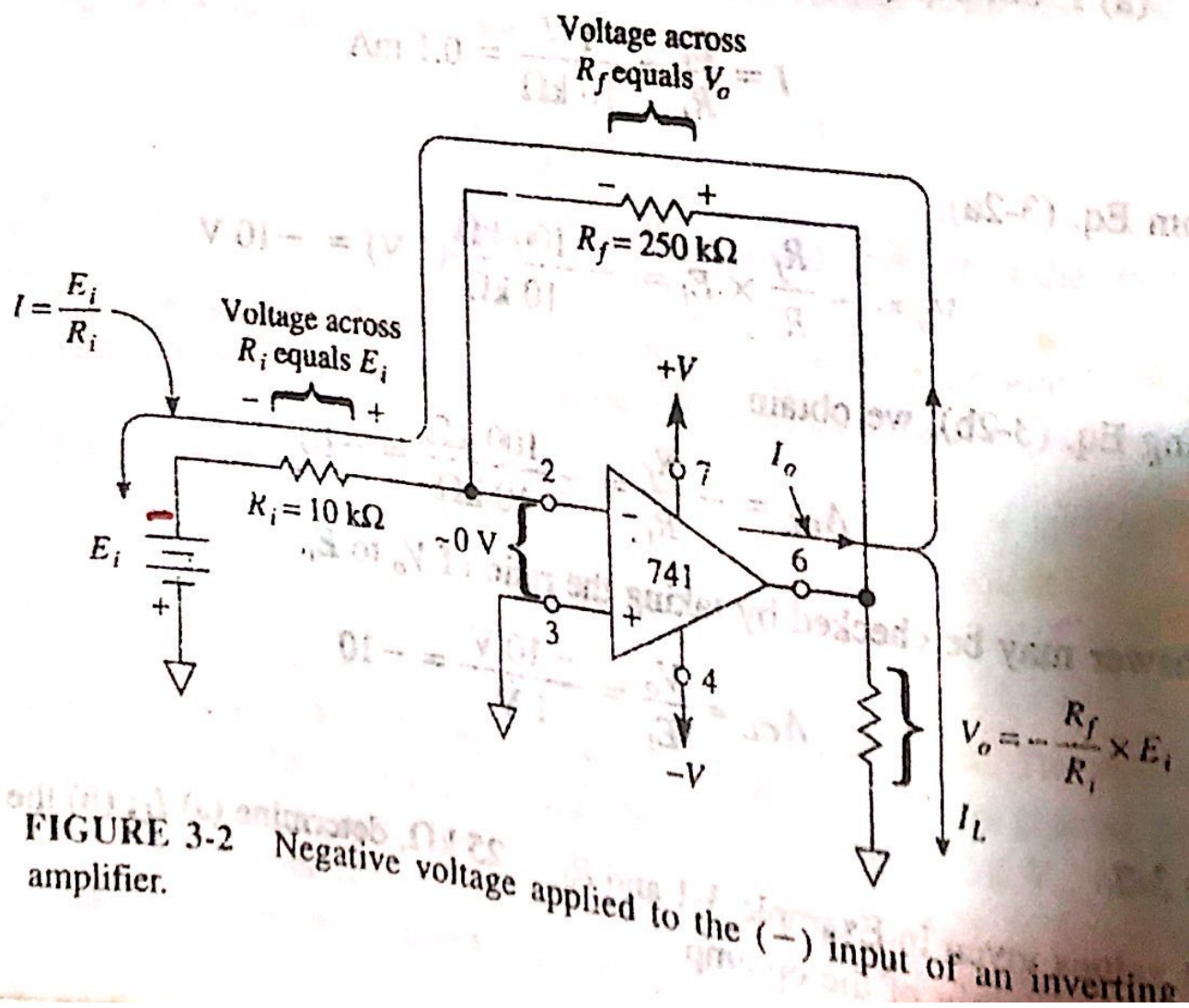
$$A_{CL} = \frac{V_o}{E_i} = \frac{-10 \text{ V}}{1 \text{ V}} = -10$$





### Example 3-3

For Fig. 3-2, let  $R_f = 250 \text{ k}\Omega$ ,  $R_i = 10 \text{ k}\Omega$ , and  $E_i = -0.5 \text{ V}$ . Calculate (a)  $I$ ; (b) the voltage across  $R_f$ ; (c)  $V_o$ .

**Solution** (a) From Eq. (3-1a),

$$I = \frac{E_i}{R_i} = \frac{0.5 \text{ V}}{10 \text{ k}\Omega} = 50 \text{ }\mu\text{A} = 0.05 \text{ mA}$$

(b) From Eq. (3-1b),

$$\begin{aligned} V_{R_f} &= I \times R_f \\ &= (50 \text{ }\mu\text{A})(250 \text{ k}\Omega) \\ &= 12.5 \text{ V} \end{aligned}$$

(c) From Eq. (3-2a),

$$V_o = -\frac{R_f}{R_i} \times E_i = -\frac{250 \text{ k}\Omega}{10 \text{ k}\Omega} (-0.5 \text{ V}) = +12.5 \text{ V}$$

Thus the magnitude of the output voltage does equal the voltage across  $R_f$ , and  $A_{CL} = -25$ .