

# CSE2209: Digital Electronics and Pulse Techniques

Course Conducted By:

Nowshin Nawar Arony  
Lecturer, Dept of CSE, AUST


# Chapter 8

## Field Effect Transistors
 
# MOSFET (Metal-Oxide-Semiconductor Field-effect Transistor)

A metal–oxide–semiconductor field-effect transistor (MOSFET) is a field-effect transistor (FET) with an insulated gate, where the voltage determines the conductivity of the device. It is used for switching or amplifying signals.

- S: Source
- G: Gate
- D: Drain
- Body: Substrate



# Classification of MOSFET


- The one way of classifying MOSFETs is depending upon the type of channel. Namely n-channel and p-channel shortly called as NMOS and PMOS respectively.
- The another way of classifying the MOSFETs is depending upon the availability of channel between source and drain terminals i.e. Enhancement mode MOSFETs and depletion mode MOSFETs.

# MOSFET device types


Thus, there are four basic MOSFET device types there are :

- 1) n-channel enhancement mode MOSFET
- 2) n-channel depletion mode MOSFET
- 3) p-channel enhancement mode MOSFET
- 4) p-channel depletion mode MOSFET.
 
# n-channel Depletion and Enhancement mode




Depletion Mode

 


Enhancement Mode
 
# p-channel Depletion and Enhancement mode





Depletion Mode

 

Enhancement Mode

# NMOS in enhancement mode



G = High, D-S short  
G = Low, D-S open

  




# PMOS in depletion mode

G = High, D-S open  
G = Low, D-S short

  



# NMOS Inverters

$V_i$	NMOS	$V_o$
$V(0)$	OFF	$V_{DD}$
$V(1)$	ON	GND

 

# PMOS Inverters


$V_i$	PMOS	$V_o$
$V(0)$	ON	$V_{DD}$
$V(1)$	OFF	GND

 
 


# Logic Gates Using MOSFET
 
# NOT Gate using NMOS


- Here  $R$  is used to control the current flow.
- When  $V_i = \text{low}$ ,  
then  $Q$  will be open and  $V_o = V_{DD}$
- When  $V_i = \text{high}$ ,  
then  $Q$  will be short and  $V_o = \text{GND}$



  

# NOT Gate using NMOS

 
- Q2 used instead of load. Q2 is always high as Gate is directly connected to  $V_{CC}$ .
- When  $V_i = \text{low}$ , then Q will be open and  $V_o = V_{DD}$
- When  $V_i = \text{high}$ , then Q will be short and  $V_o = \text{GND}$



# NAND Gate using NMOS ( $\overline{AB}$ )


$A$	$B$	$Y$
$V_1$	$V_2$	$V_0$
0	0	$V_{DD}$
0	$V_{DD}$	$V_{DD}$
$V_{DD}$	0	$V_{DD}$
$V_{DD}$	$V_{DD}$	0

$$Y = \overline{AB}$$

 



 
# NAND Gate using PMOS ( $\overline{AB}$ )




# NOR Gate using NMOS ( $\overline{A + B}$ )

$A$	$B$	$Y$
$V_1$	$V_2$	$V_o$
0	0	$V_{DD}$
0	$V_{DD}$	0
$V_{DD}$	0	0
$V_{DD}$	$V_{DD}$	0

$$Y = \overline{A + B}$$

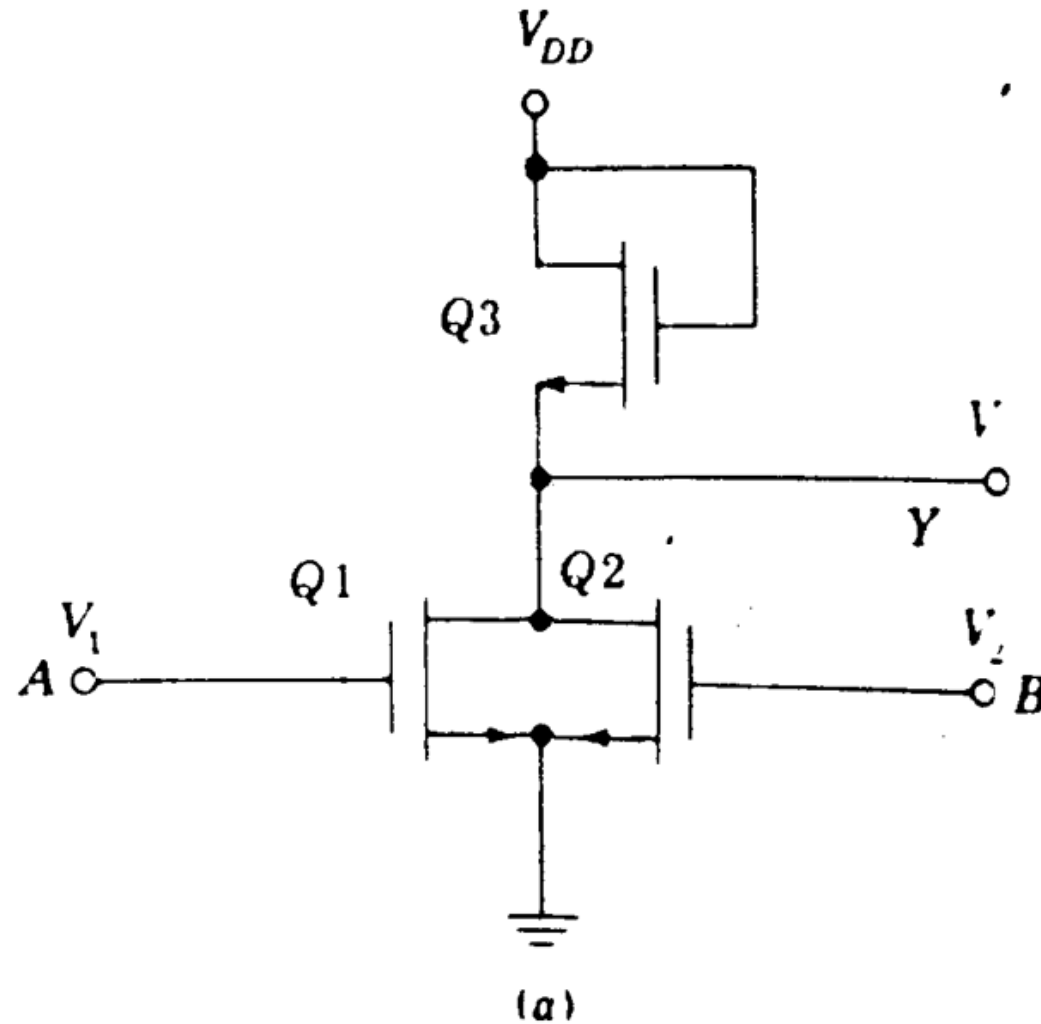

# OR Gate using NMOS ( $A + B$ )

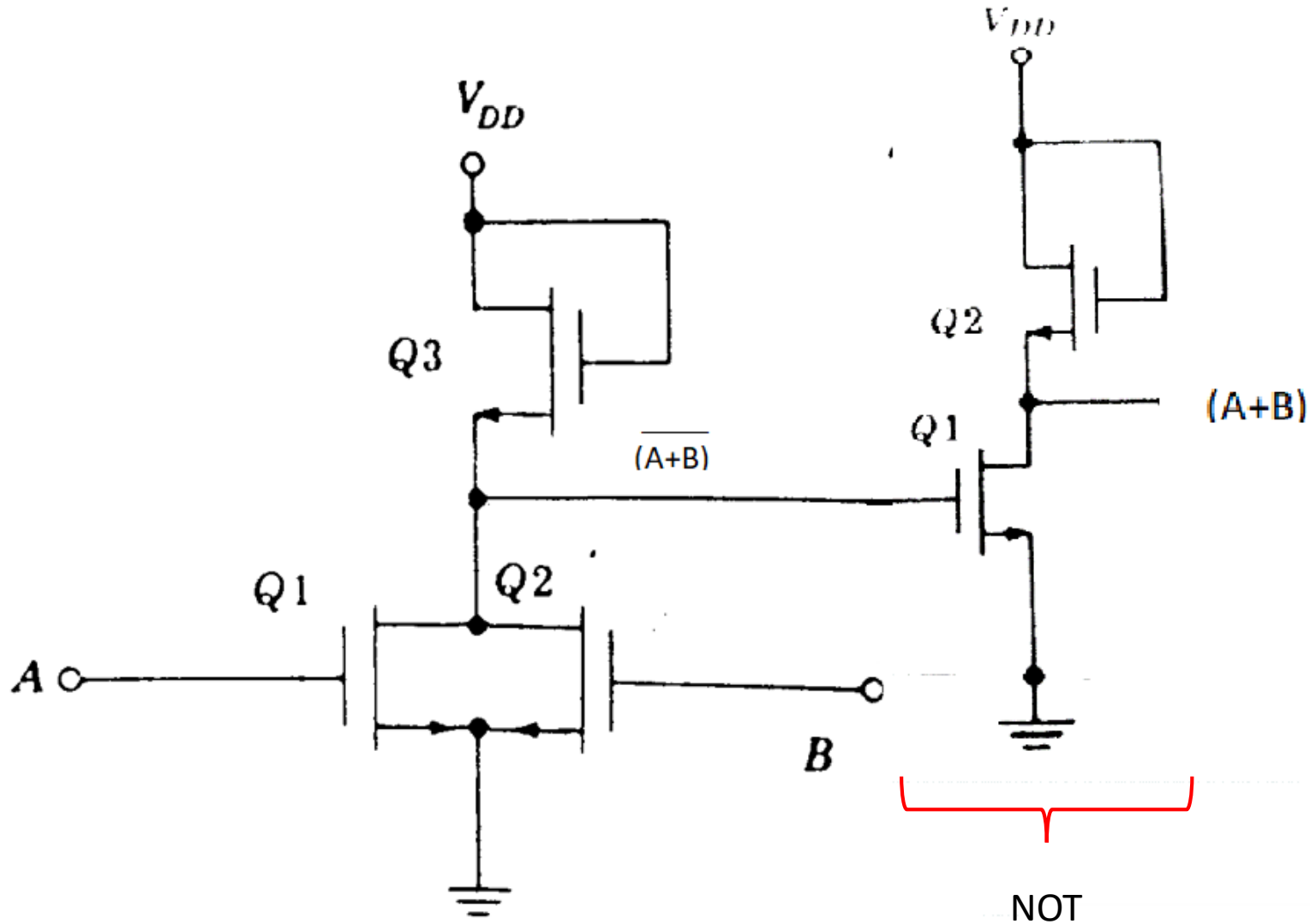

# Draw Circuits using NMOS

1)  $F = A + B$

2)  $F = A + BC$

3)  $F = AB + CD$

4)  $F = A \cdot (\overline{B + C})$

5)  $F = \overline{A} \cdot (\overline{B + C})$


6)  $F = (\overline{A} + B)(A + \overline{B}) + \overline{A}\overline{B}\overline{C}D + \overline{A}\overline{B}\overline{C}\overline{D} + \overline{(C + \overline{E})}$

# CMOS (Complementary MOSFET)

It is possible to construct p-channel and n-channel enhancement MOS devices on the same chip. Such devices are called complementary MOSFETs or CMOS.

The circuit given here works as a CMOS inverter.

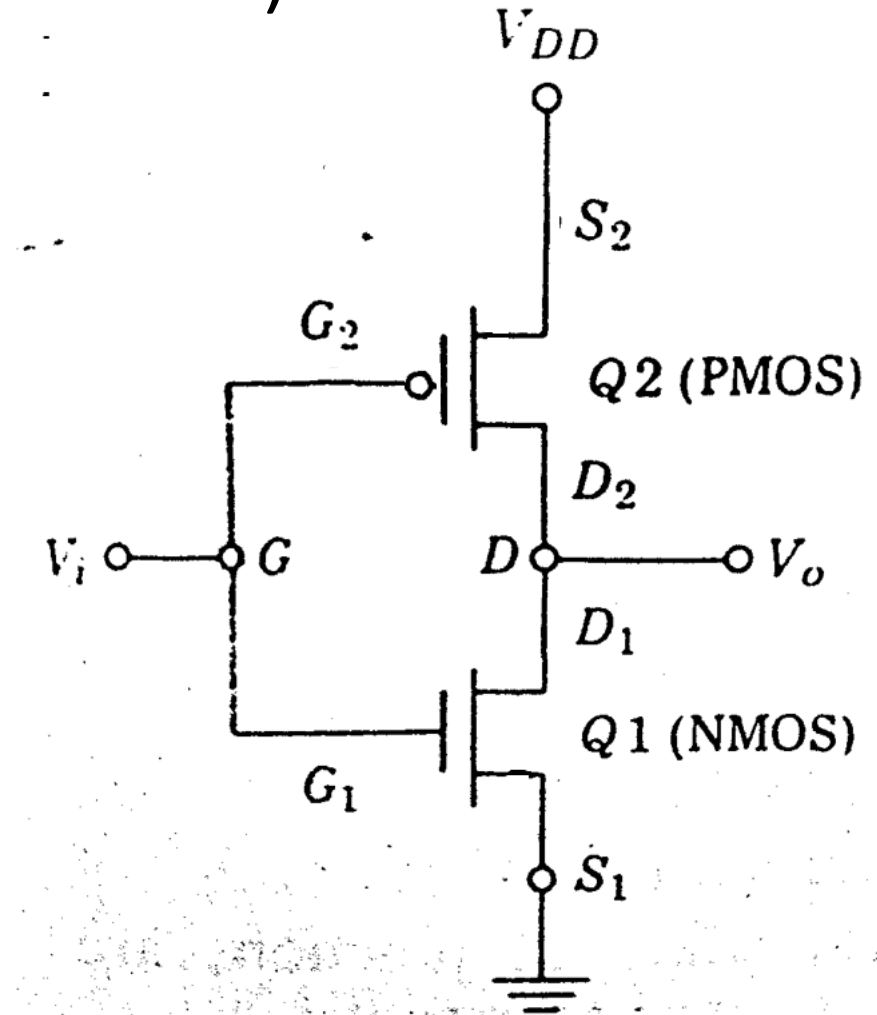
The driver is transistor  $Q_1$  and  $Q_2$  acts as the load.



# CMOS


- $V_i = V(0)$ , then  
PMOS = short, NMOS = open  
 $V_o = V_{DD} = V(1)$
- $V_i = V(1)$ , then  
PMOS = open, NMOS = short  
 $V_o = \text{GND} = V(0)$

$V_i$	$V_o$
Low	$V_{DD}$
High	GND

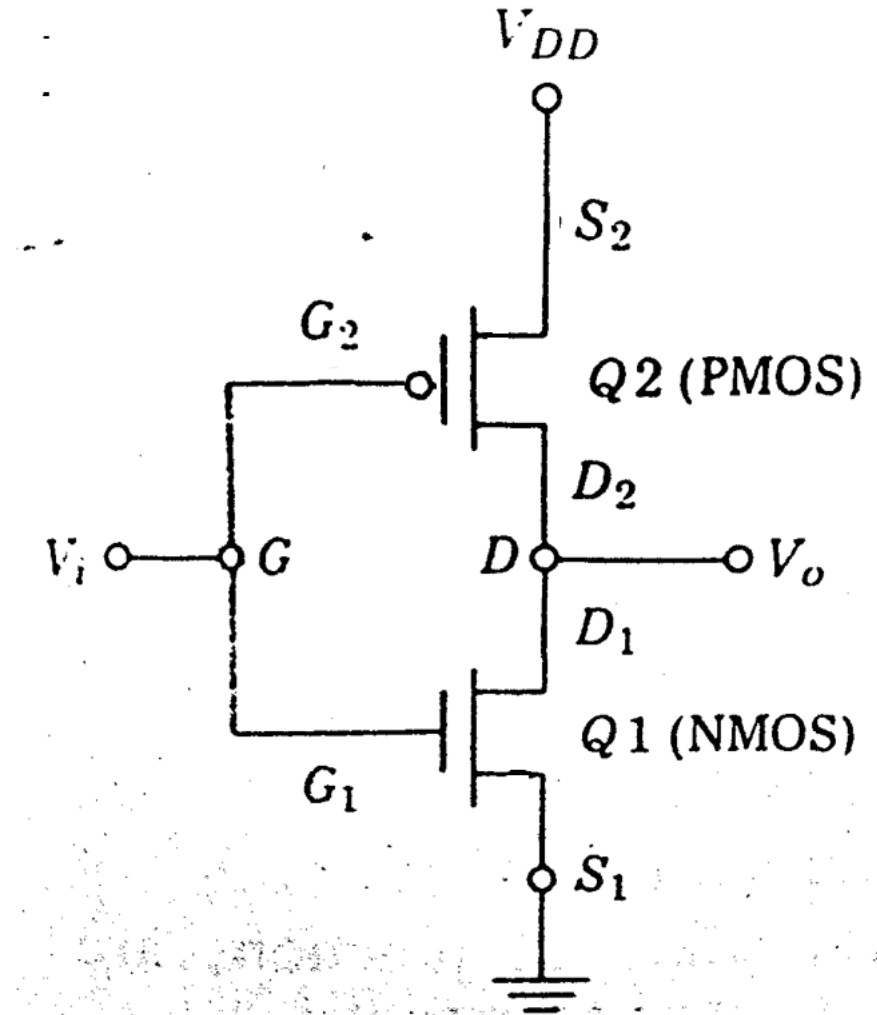


# CMOS NAND

$V_1$	$V_2$	$V_o$
0	0	1
0	1	1
1	0	1
1	1	0

 


# CMOS NOR


$V_1$	$V_2$	$V_o$
0	0	1
0	1	0
1	0	0
1	1	0

 



 

NAND

 

NOR

# Draw Circuits using CMOS

1)  $F = A + B$

2)  $F = A + BC$

3)  $F = AB + CD$

4)  $F = A \cdot (\overline{B + C})$

5)  $F = \overline{A} \cdot (\overline{B + C})$

# Properties/Advantages of CMOS



## CMOS Properties

The desirable features of CMOS gates are the following.

1. The quiescent (static) power dissipation is extremely small (a few nanowatts). Appreciable power is absorbed only when switching from one state to the other. At 1-MHz switching rate the dynamic power increases to a few milliwatts in a 50-pF load (about the same as in a Schottky low-power gate).
2. The noise immunity is better than 40 percent of  $V_{DD}$ . Note that, for  $V_{DD} = 10$  V in the inverter transmission characteristic of Fig. 8-26*b*, a noise voltage of 4V superimposed upon  $V(0) = 0$  reduces the output from  $V(1) = 10$  V by only a fraction of a volt.
3. Propagation delay is about 50 ns per gate, allowing 10-MHz clock rates. Hence, CMOS is faster than MOS but slower than TTL logic.
4. The fan-out is very high, in excess of 50.
5. The logic swing is  $V_{DD}$ , independent of the fan-out.
6. A single power supply is required, and it can be a simple and inexpensive system (because of the small standby current).
7. If  $V_{DD} = 5$  V, then CMOS is TTL compatible.
8. The temperature stability is excellent (Fig. 8-26*b*).

The above advantages are offset by the increased cost because of the additional processing steps required. Also the density of gates for a given chip area is decreased since CMOS requires that PMOS and NMOS devices appear in pairs. For example,<sup>16</sup> a four-input NAND gate requires about 50 mil<sup>2</sup> for CMOS, 30 mil<sup>2</sup> for TTL (low power, Schottky), 11 mil<sup>2</sup> for PMOS, and 5.6 mil<sup>2</sup> for I<sup>2</sup>L (Sec. 9-13).

Millman chap 8  
pg. 263  
Reference of the  
Figure 8.26(b)

 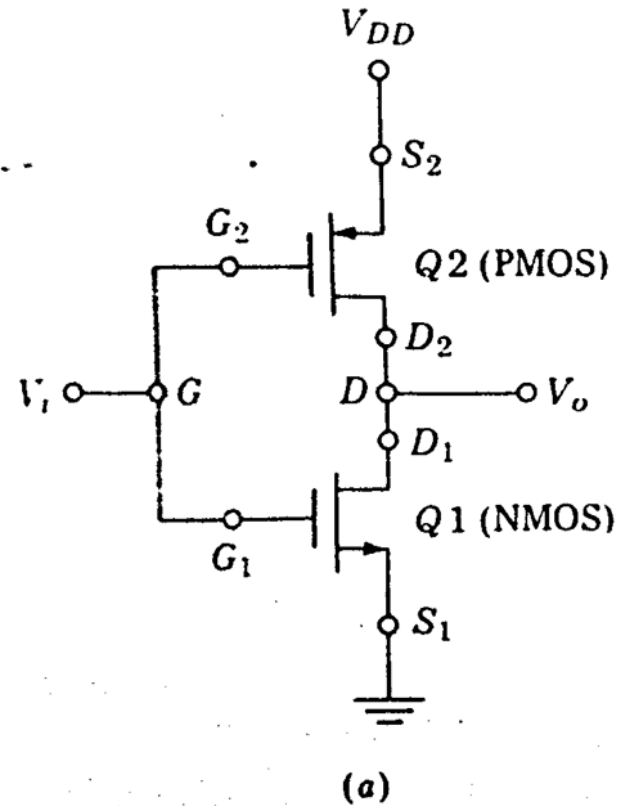

**Figure 8-26** (a) Complementary MOS inverter (b) The transfer characteristics for three values of  $V_{DD}$  and two values of temperature. (Courtesy of Motorola Semiconductor Products, Inc.)

These diagrams  
are only for  
reference.  
No need to draw  
in the Exam.