


CSE2209: Digital Electronics and Pulse Techniques

Course Conducted By:

Nowshin Nawar Arony
Lecturer, Dept of CSE, AUST



Transmission Gate



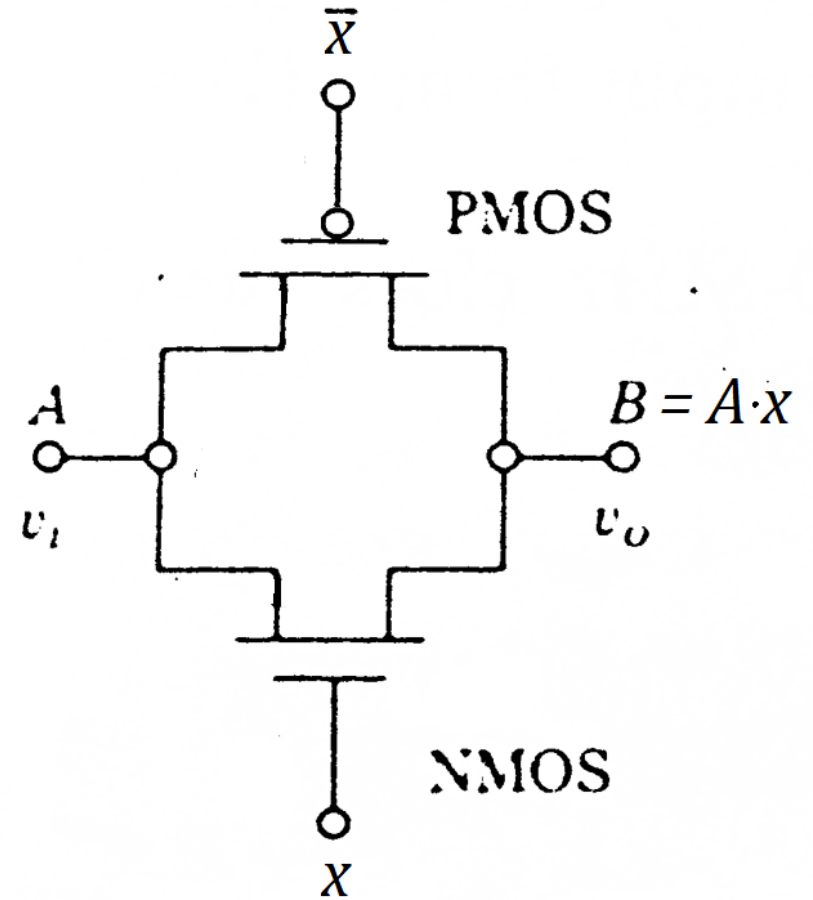
The structure of a CMOS transmission gate is shown in the figure. It consists of an NMOS in parallel with a PMOS such that the gates are controlled by the complementary voltages x applied to the NMOS, and \bar{x} applied to the PMOS. The TG is designed to act as a voltage-controlled switch.




Transmission Gate

X	A	B (output)
1	0	0
1	1	1
0	0	H.I
0	1	H.I

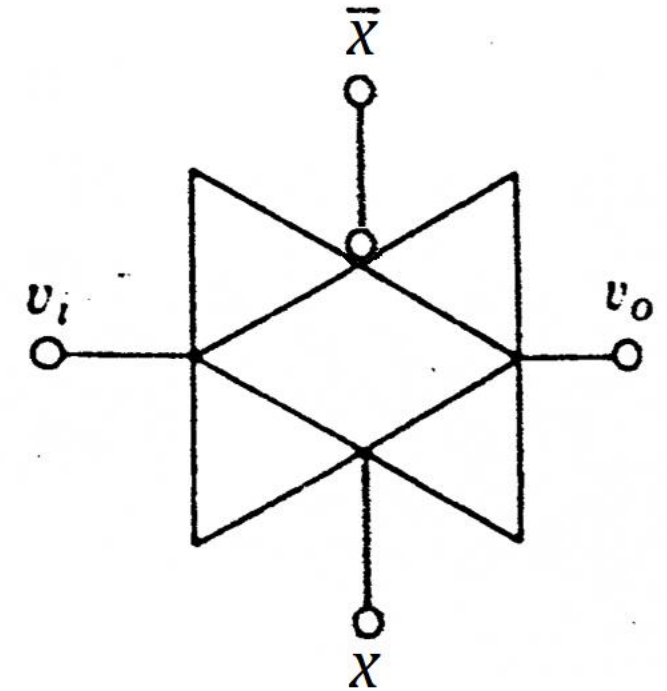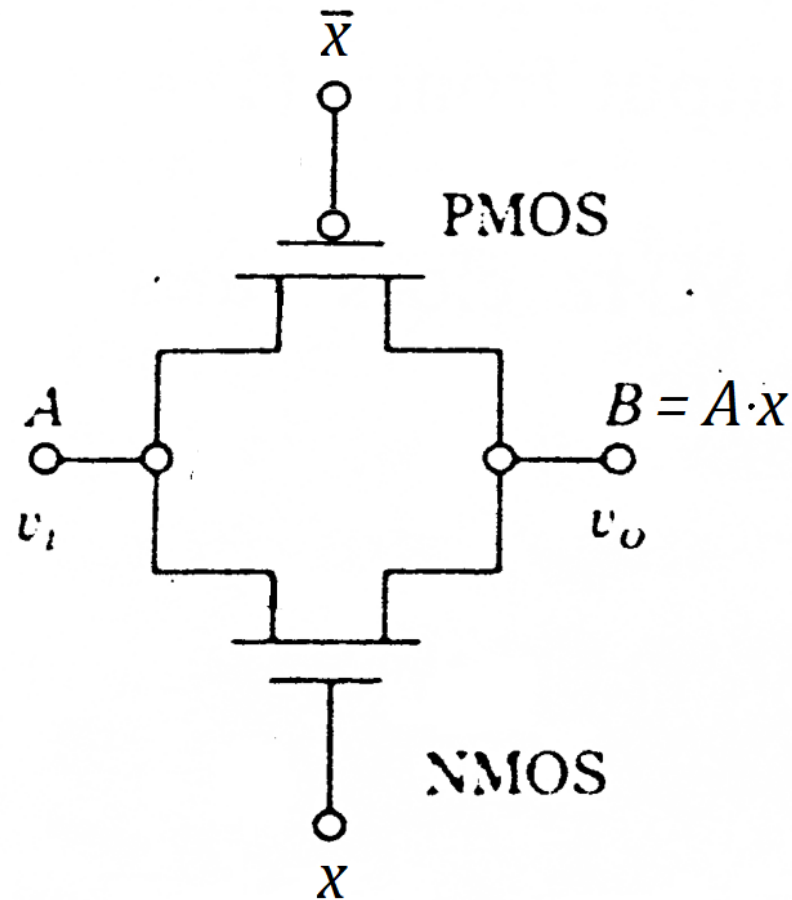

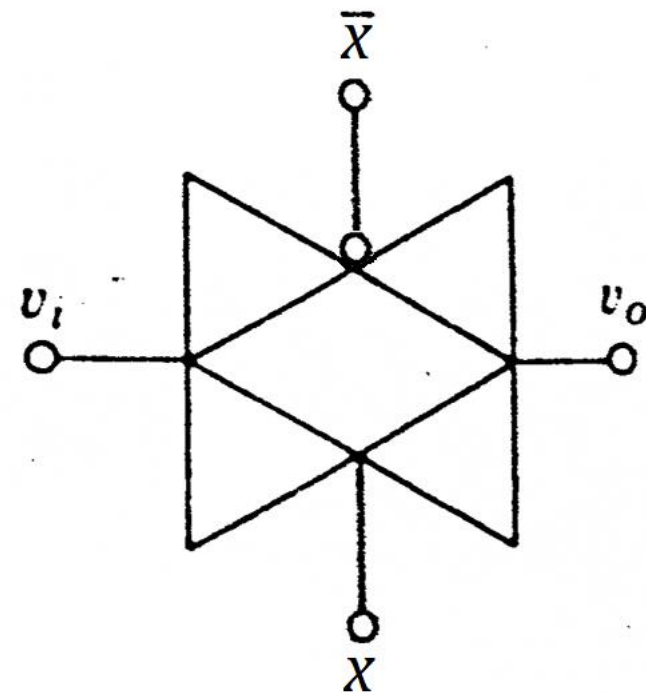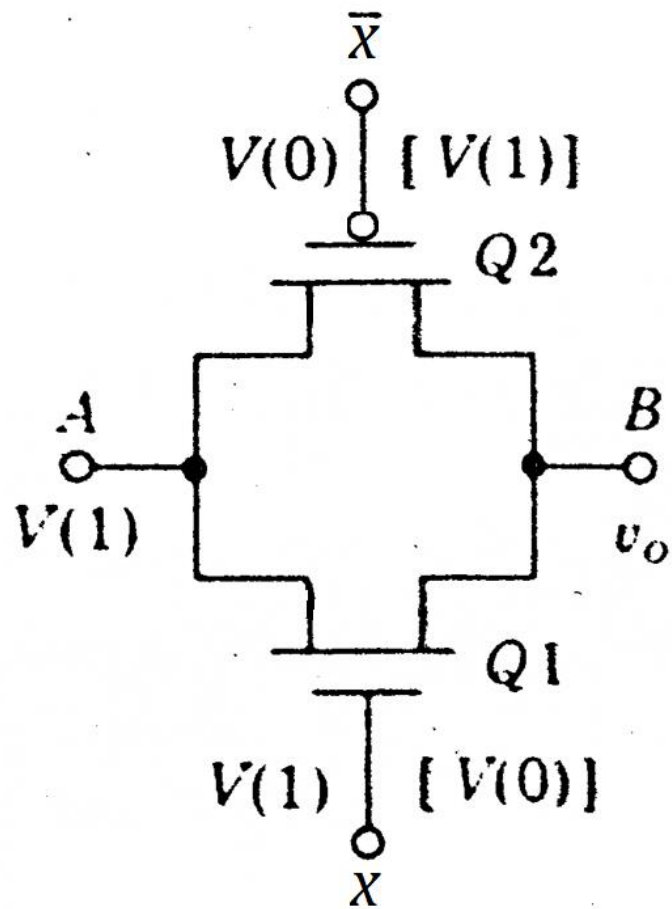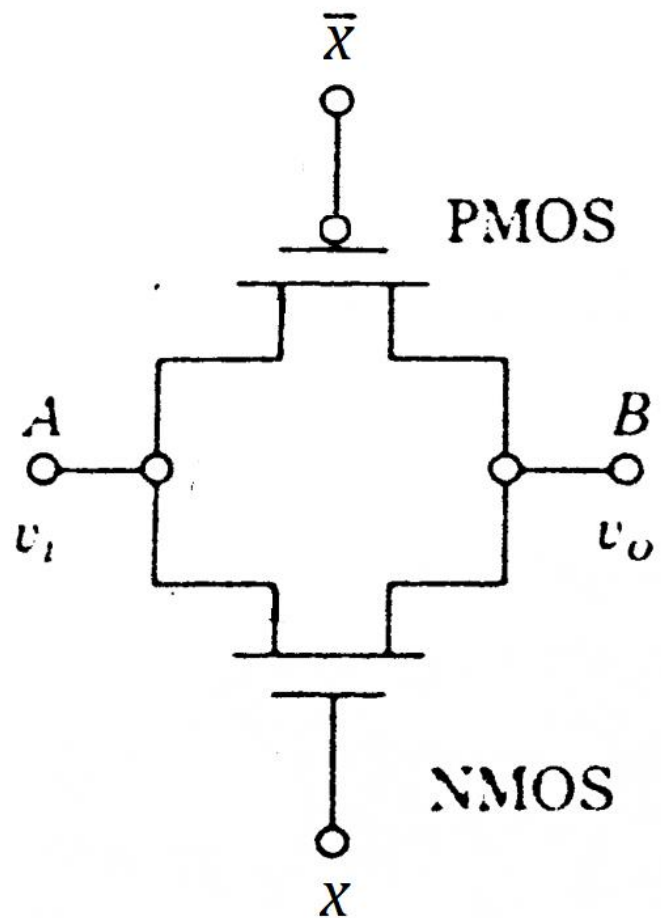

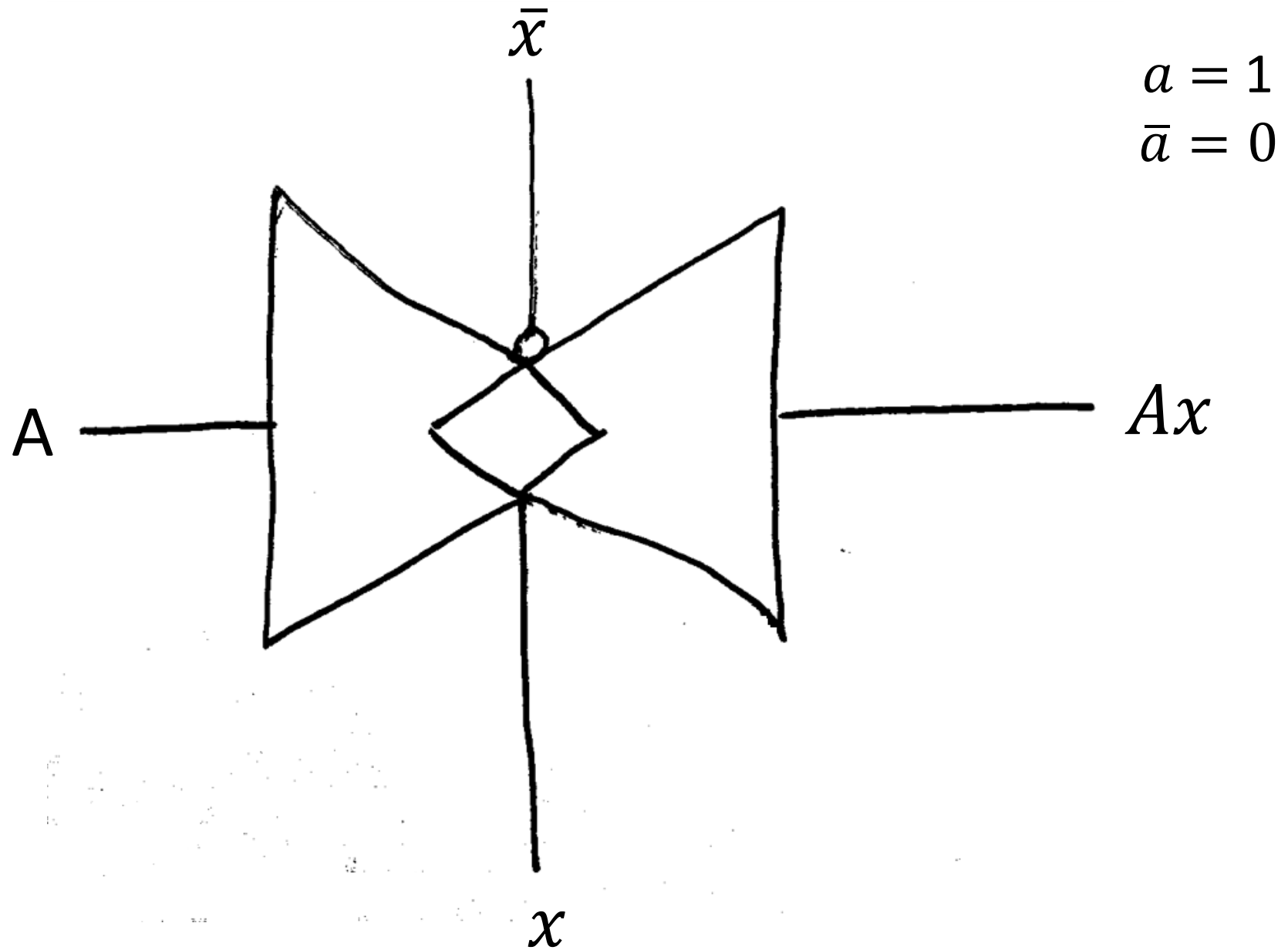


OR using transmission gate

x	y	f
0	0	0
0	1	1
1	0	1
1	1	1

Let **x** be the control signal
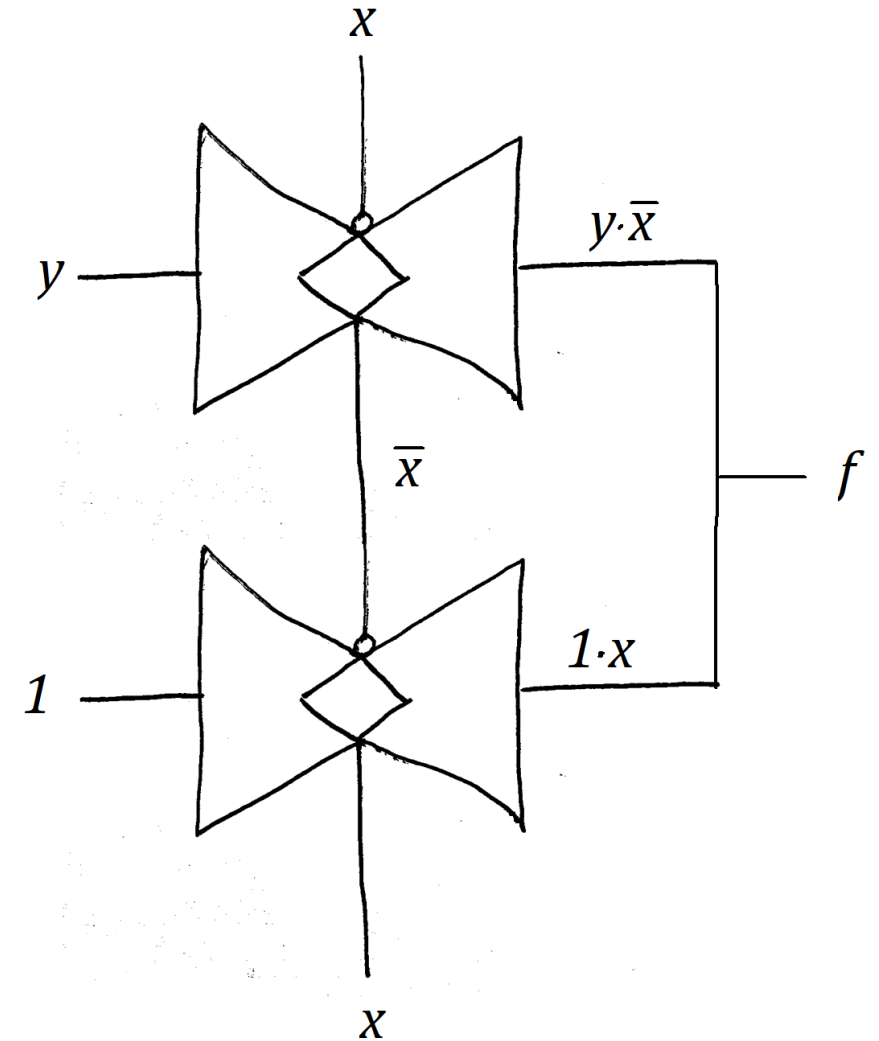
$$\begin{aligned}f(x, y) &= x + y \\&= \bar{x}y + x\bar{y} + xy \\&= \bar{x}y + x(y + \bar{y}) \\&= \bar{x}y + x \cdot 1 \quad [\text{inverse law}]\end{aligned}$$




AND using transmission gate

x	y	f
0	0	0
0	1	0
1	0	0
1	1	1


Let x be the control signal
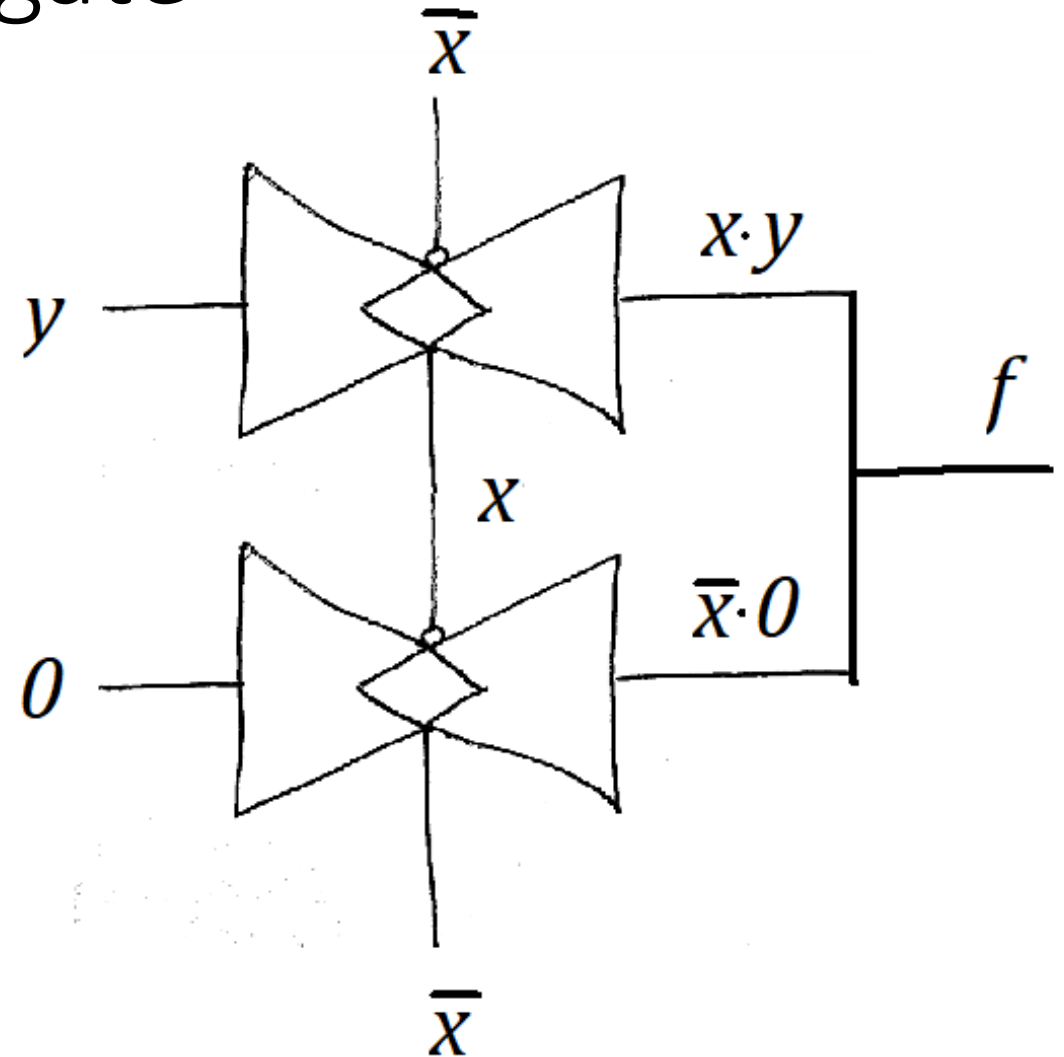
$$\begin{aligned} f(x, y) &= xy \\ &= xy + \bar{x} \cdot 0 \text{ [null law]} \end{aligned}$$



Implementing with Transmission Gate

$$f = xy\bar{z}$$

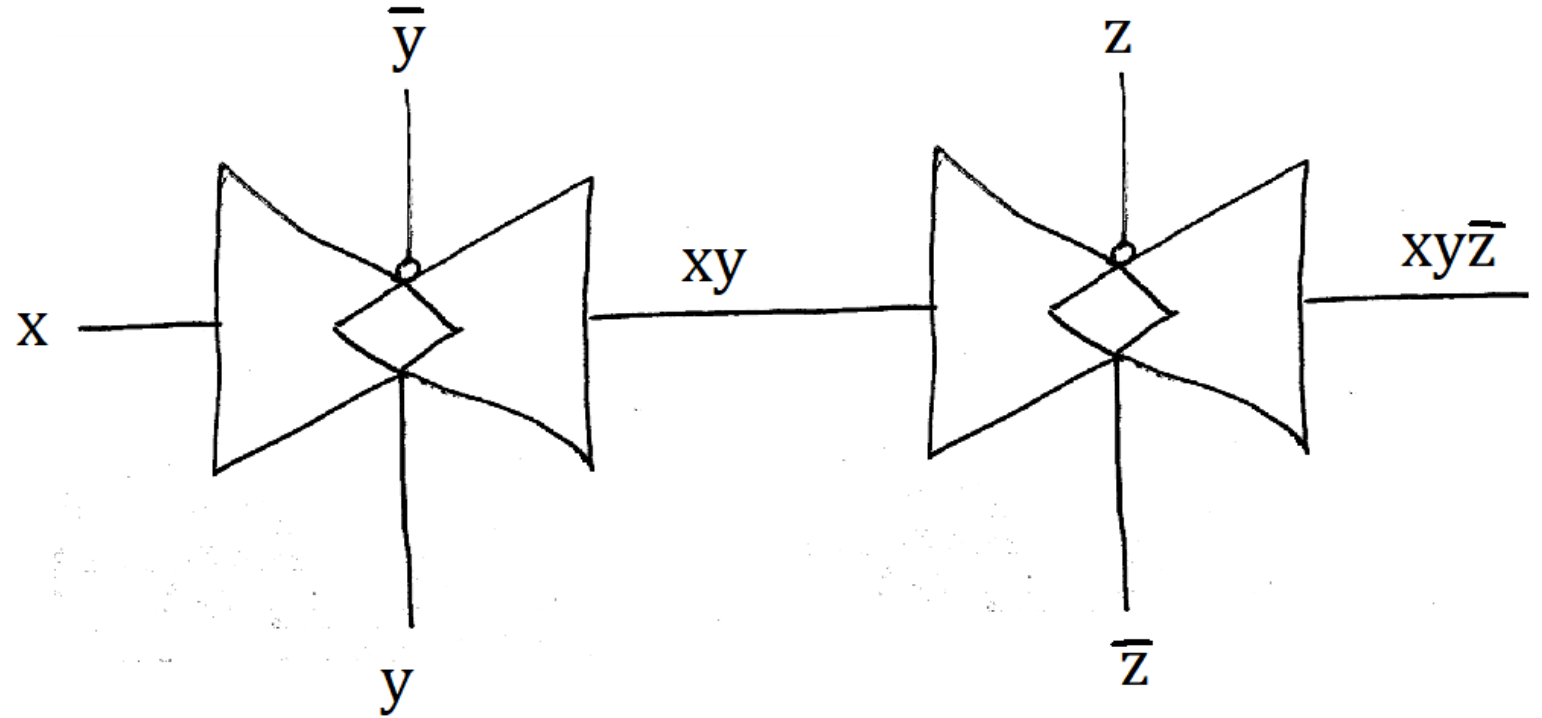


MUX Design Based on CMOS Transmission Gate


2 x 1 MUX

P_0 active, when $S = 0$

P_1 active, when $S = 1$

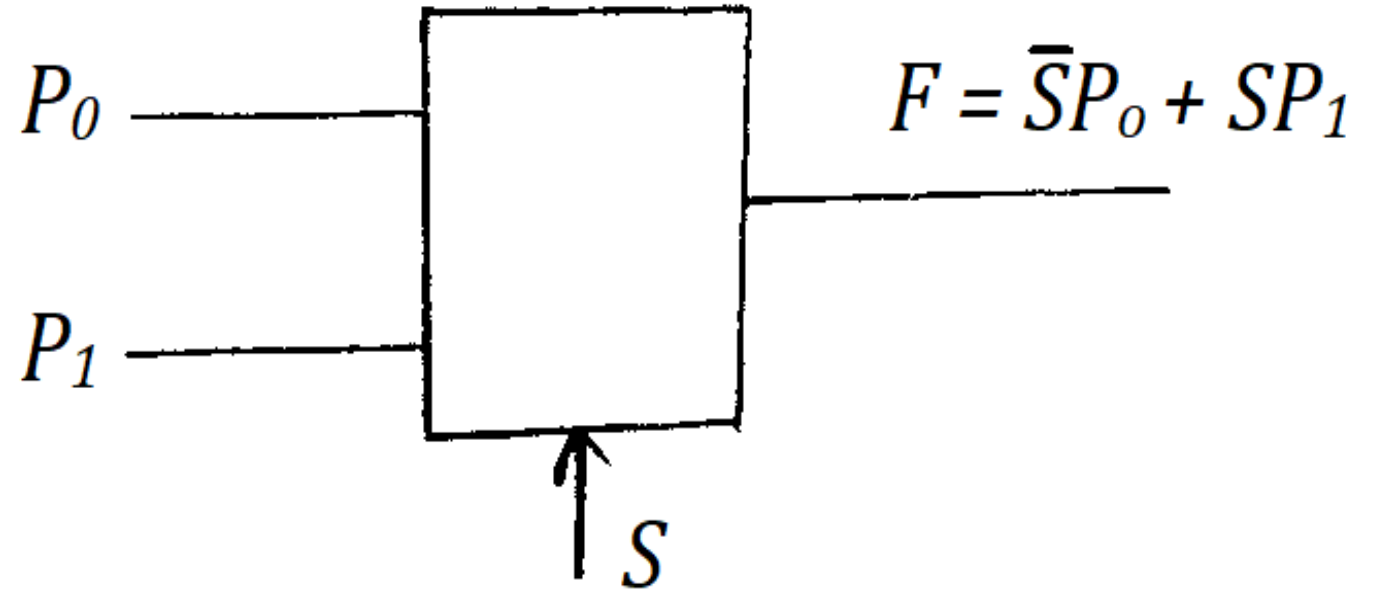


2x1 MUX

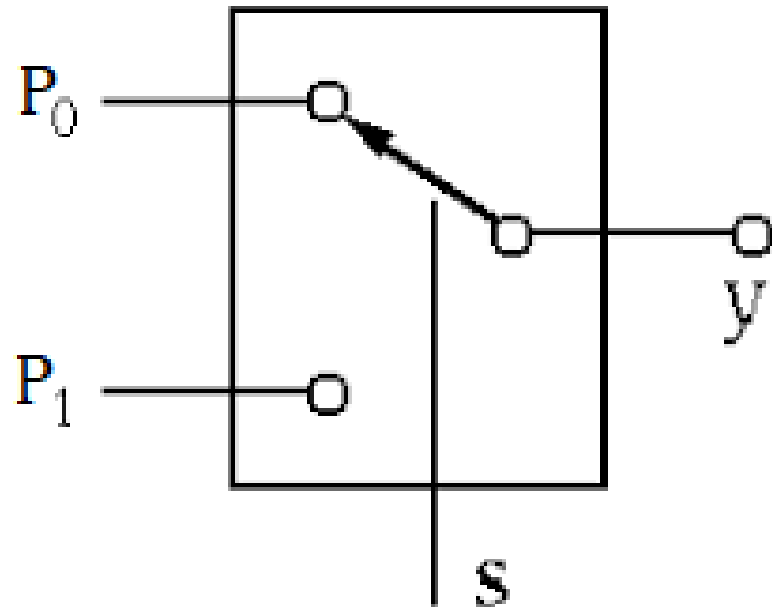

P_0 active, when $S=0$


2x1 MUX

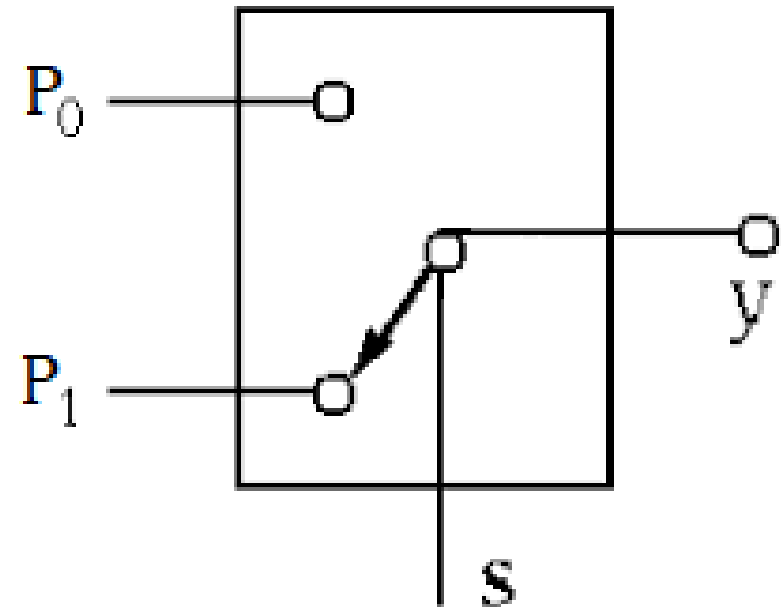


P_1 active, when $S=1$

2 x 1 MUX

$$F = \bar{S}P_0 + SP_1$$

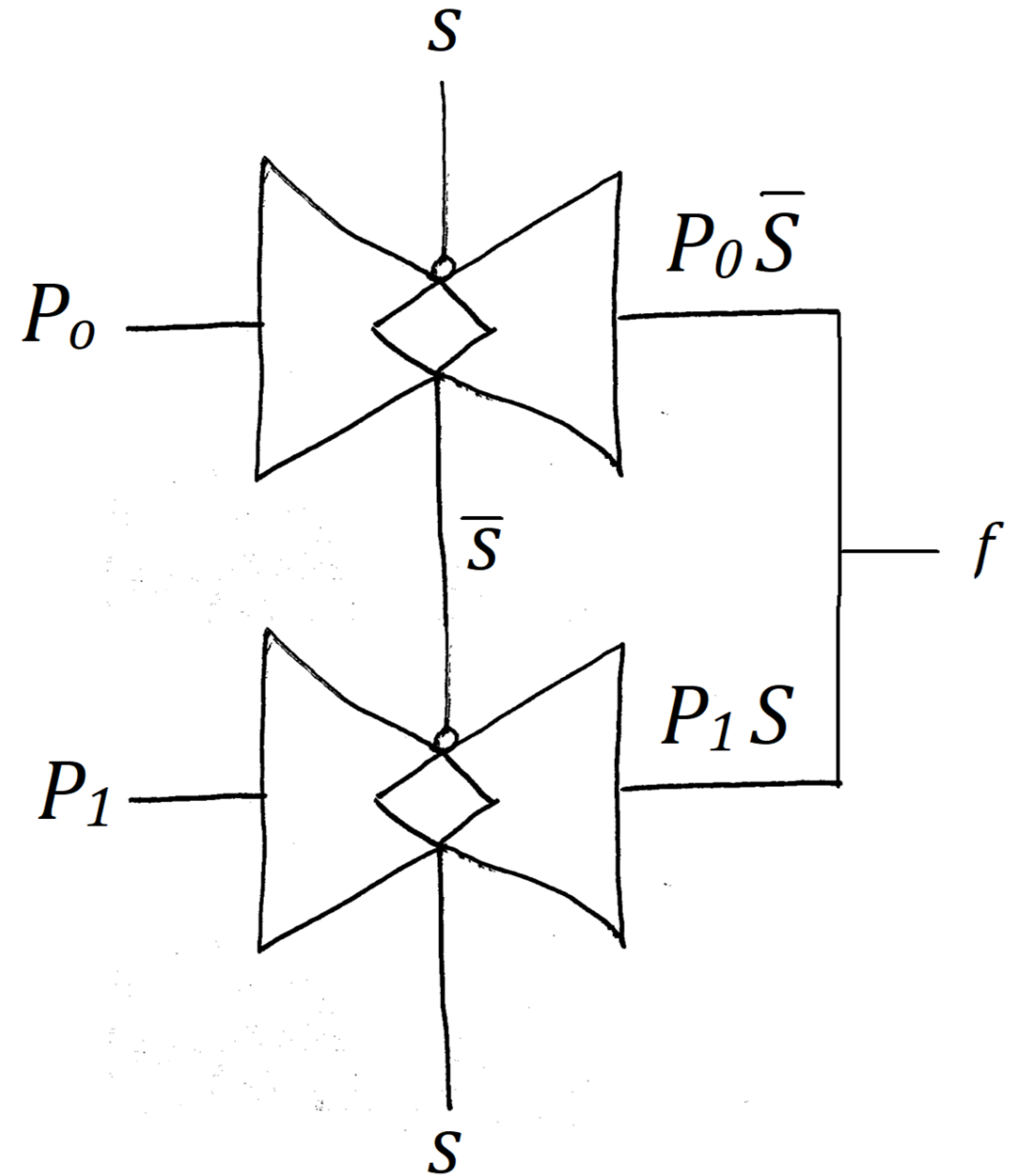


4 x 1 MUX

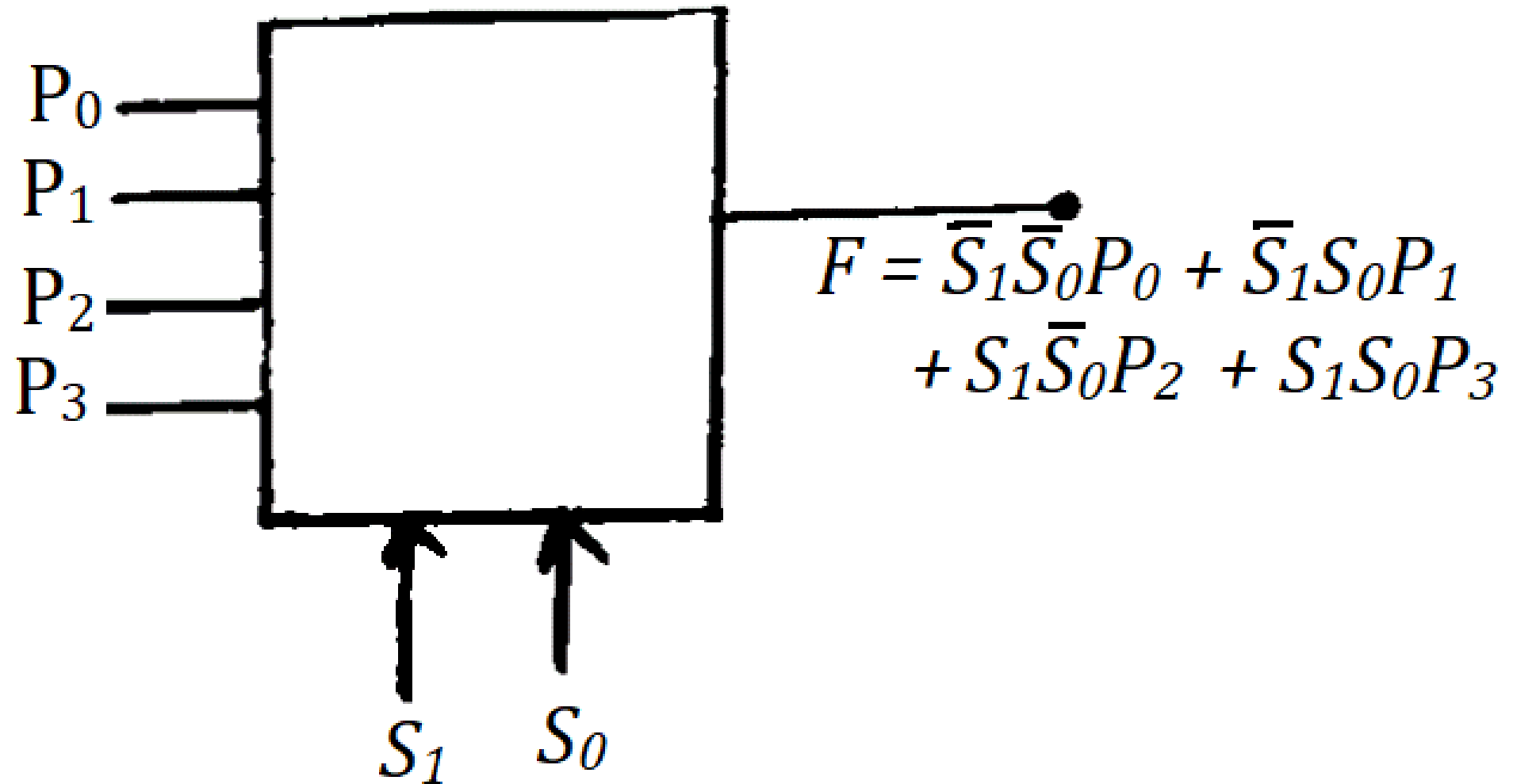

4 x 1 MUX
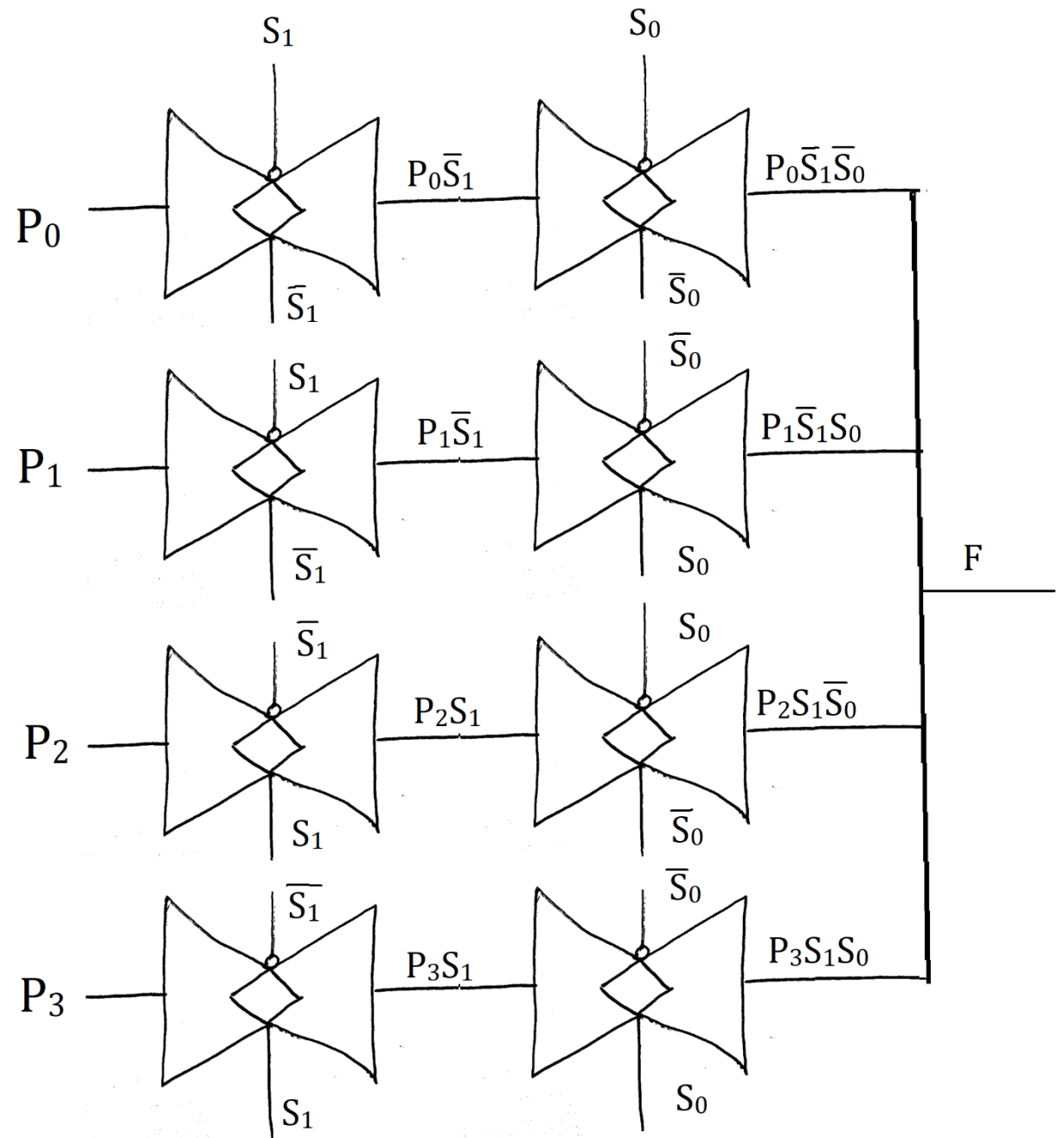
$$F = P_0 \bar{S}_1 \bar{S}_0 + P_1 \bar{S}_1 S_0 + P_2 S_1 \bar{S}_0 + P_3 S_1 S_0$$



Laws of Boolean Algebra

Name	AND form	OR form
Identity law	$1A = A$	$0 + A = A$
Null law	$0A = 0$	$1 + A = 1$
Idempotent law	$AA = A$	$A + A = A$
Inverse law	$A\bar{A} = 0$	$A + \bar{A} = 1$
Commutative law	$AB = BA$	$A + B = B + A$
Associative law	$(AB)C = A(BC)$	$(A + B) + C = A + (B + C)$
Distributive law	$A + BC = (A + B)(A + C)$	$A(B + C) = AB + AC$
Absorption law	$A(A + B) = A$	$A + AB = A$
De Morgan's law	$\overline{AB} = \bar{A} + \bar{B}$	$\overline{\bar{A} + \bar{B}} = \bar{A}\bar{B}$

Expressing Boolean function with Mean terms

$$F = a + b\bar{c}$$

$$= a.1.1 + 1.b\bar{c}$$

$$= a(b + \bar{b})(c + \bar{c}) + (a + \bar{a})b\bar{c}$$

$$= (ab + a\bar{b})(c + \bar{c}) + ab\bar{c} + \bar{a}b\bar{c}$$

$$= abc + \underline{ab\bar{c}} + a\bar{b}c + a\bar{b}\bar{c} + \underline{ab\bar{c}} + \bar{a}b\bar{c}$$

$$= abc + ab\bar{c} + a\bar{b}c + a\bar{b}\bar{c} + \bar{a}b\bar{c} \quad [\text{Idempotent Law } (x+x=x)]$$

$$= \Sigma(2,4,5,6,7)$$

Implement $F(a,b,c) = \Sigma(2,4,5,6,7)$
using Transmission Gate

Truth Table for $F(a,b,c) = \Sigma(2,4,5,6,7)$

a	b	c	f
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

K-Map

Let b and c are the control signals.


a \ bc	00	01	11	10
	0	1	3	2
0	0	1	3	2
1	4	5	7	6
	a	a	a	1

$$F(a,b,c) = \Sigma(2,4,5,6,7)$$

$$a\bar{b}\bar{c} + a\bar{b}c + b\bar{c} + abc$$

Implement using
Transmission Gate:
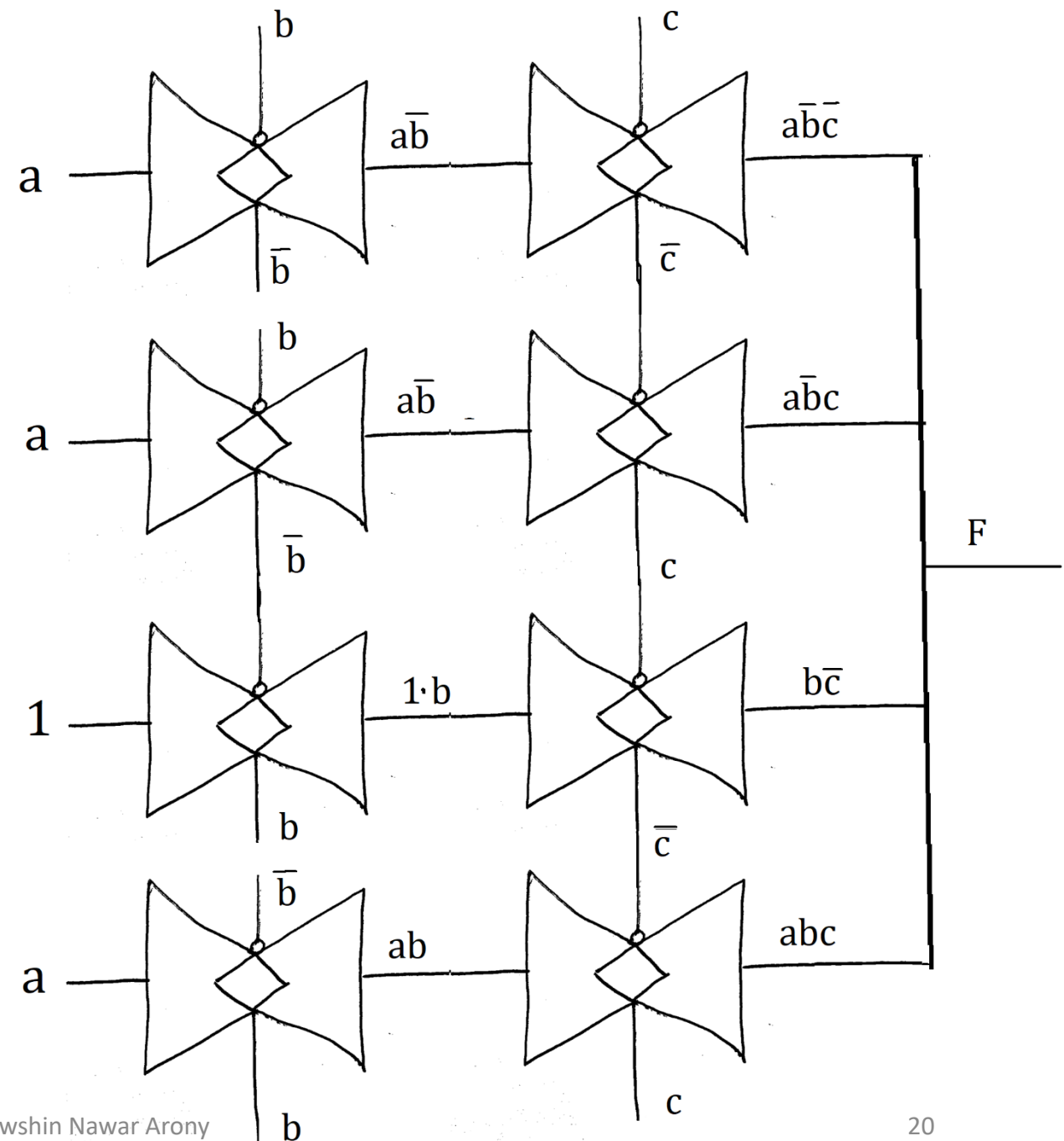
$$f(a,b,c) = a\bar{b}\bar{c} + a\bar{b}c + b\bar{c} + abc$$



2nd Approach

a	b	c	f
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

Let, b and c are the control signal

b	c	output
0	0	a
0	1	a
1	0	1
1	1	a

$$a\bar{b}\bar{c} + a\bar{b}c + b\bar{c} + abc$$

3rd Approach

Given, $f = a + b\bar{c}$

Let, b, c are control signals.

$$\begin{aligned}f(a, b, c) &= b f(a, 1, c) + \bar{b} f(a, 0, c) \\&= b.c. f(a, 1, 1) + b.\bar{c}. f(a, 1, 0) + \bar{b}.c. f(a, 0, 1) + \bar{b}.\bar{c}. f(a, 0, 0) \\&= b.c. a + b.\bar{c}. 1 + \bar{b}.c. a + \bar{b}.\bar{c}. a \\&= abc + b\bar{c} + a\bar{b}c + a\bar{b}\bar{c}\end{aligned}$$

Here,

$$f(a, 1, 1) = a + b\bar{c} = a + 1.\bar{1} = a + 1.0 = a + 0 = a$$

$$f(a, 1, 0) = a + b\bar{c} = a + 1.\bar{0} = a + 1.1 = a + 1 = 1$$

$$f(a, 0, 1) = a + b\bar{c} = a + 0.\bar{1} = a + 0.0 = a + 0 = a$$

$$f(a, 0, 0) = a + b\bar{c} = a + 0.\bar{0} = a + 0.1 = a + 0 = a$$


Implement using CMOS transmission gate,
2x1 or/and 4x1 MUX


- $F(a,b,c) = \Sigma(0,2,4,6)$
- $F(x,y,z) = xy + \bar{z}$
- $F(x,y,z) = xy + yz + zx$
- $F(a,b,c,d) = a\bar{b} + c\bar{d}$

Read Only Memory (ROM)

$2^M \times N$ ROM

M = No. of inputs
 N = No. of outputs

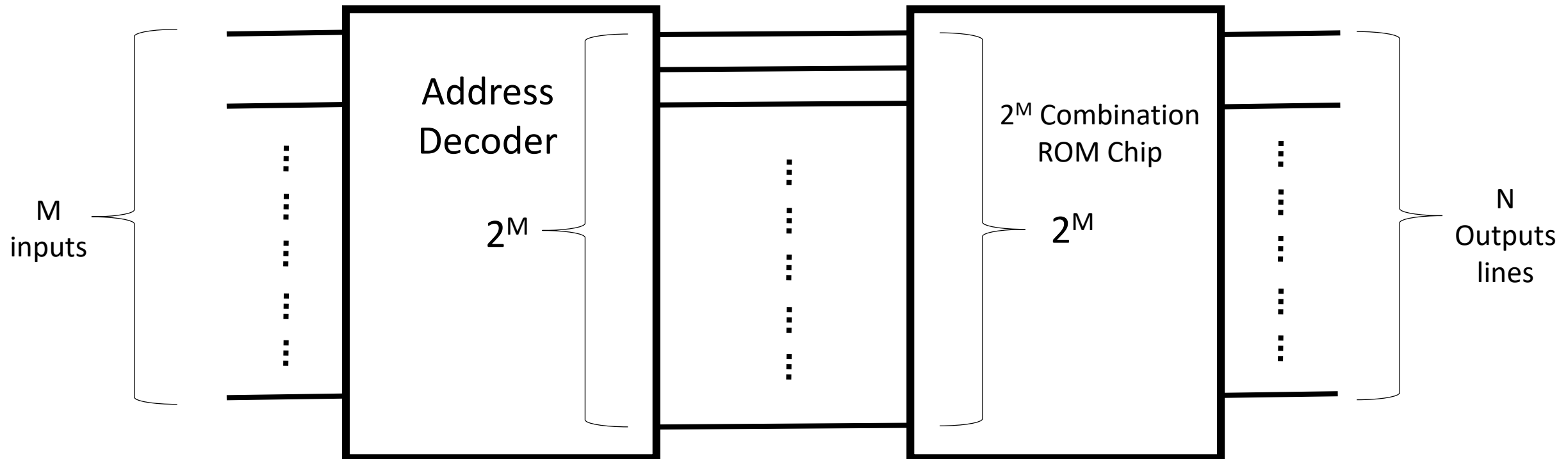


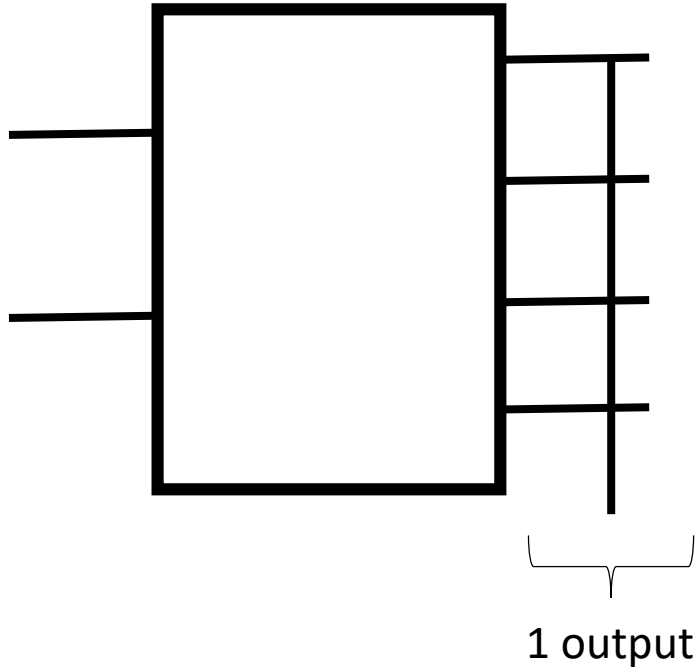

$2^M \times N$ ROM


When $M = 2$ and $N = 1$

$2^2 \times 1 = 4 \times 1$ ROM

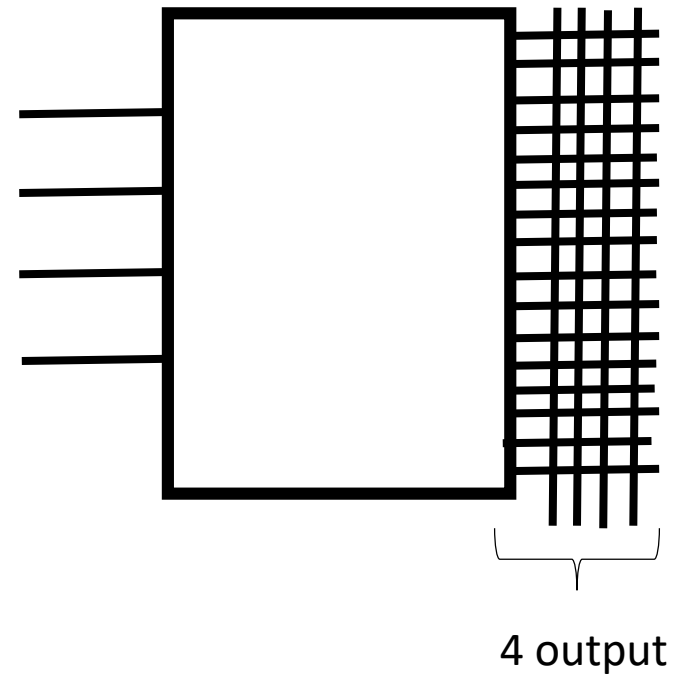

When $M = 4$ and $N = 4$

$2^4 \times 4 = 16 \times 4$ ROM

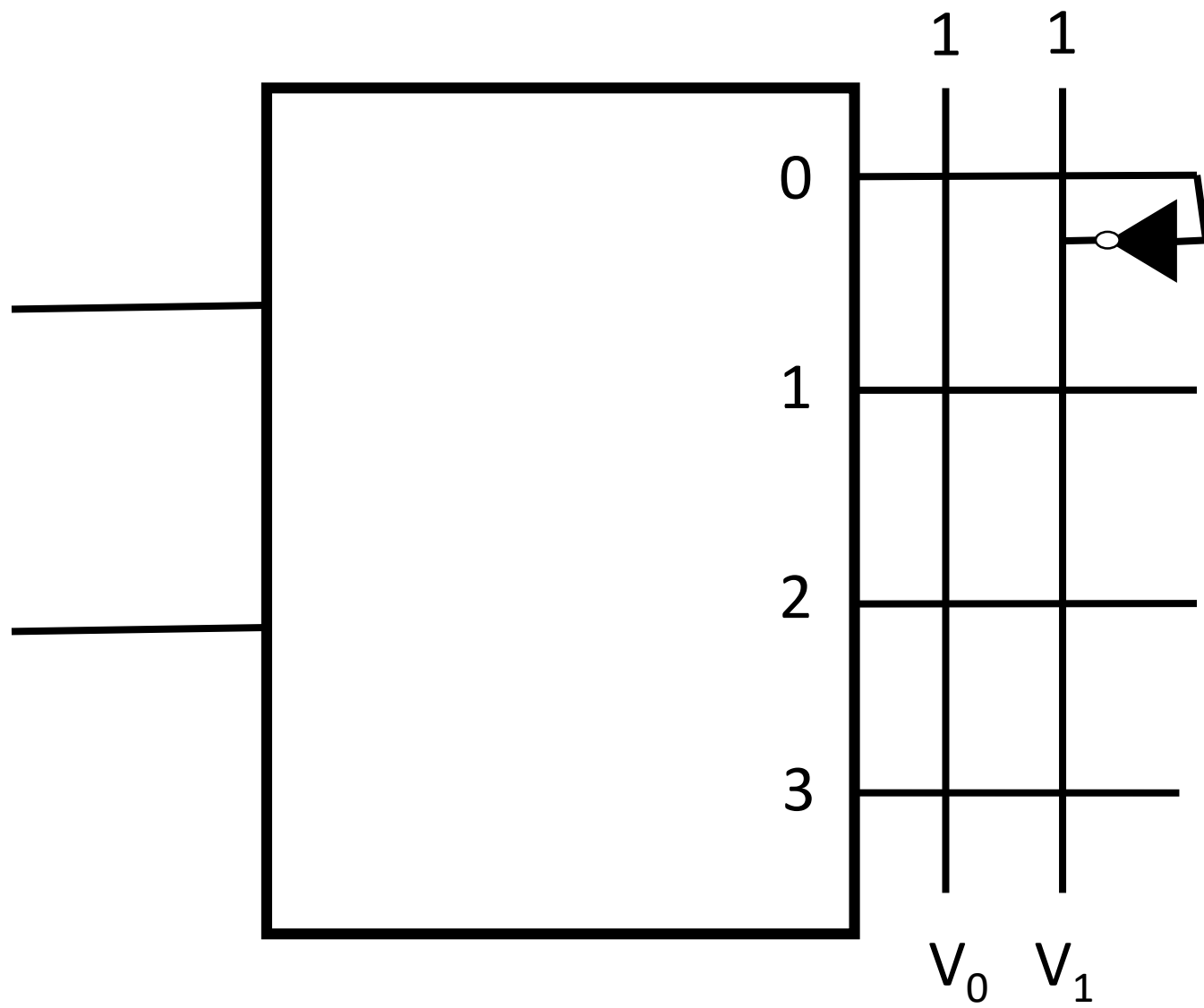

4x2 ROM


Implement the given expression using 4x1 ROM

- $f(A_0, A_1) = \Sigma(1, 2, 3)$

So ROM size:


$$2^2 \times 1 = 4 \times 1 \text{ ROM}$$

A_0	A_1	output
0	0	0
0	1	1
1	0	1
1	1	1

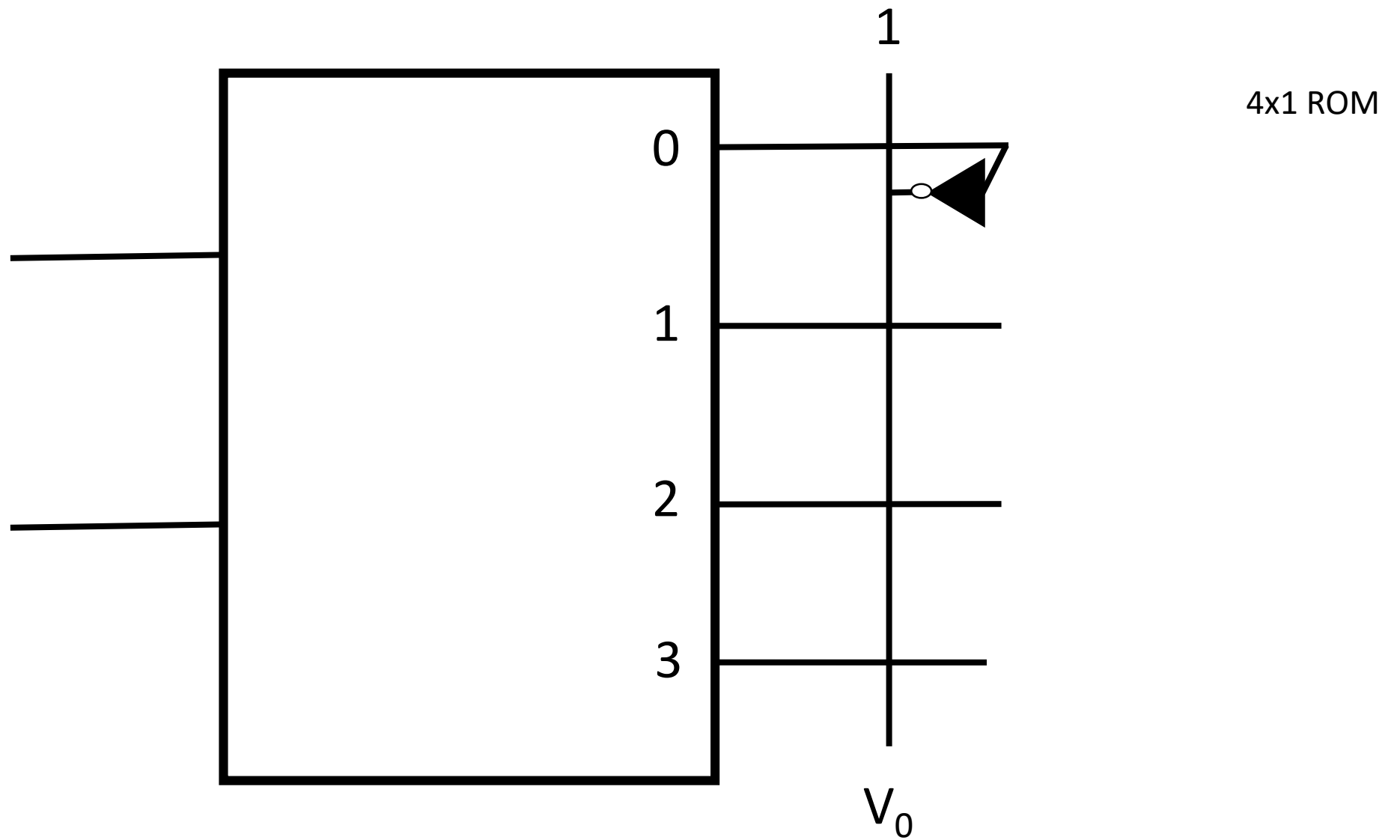

Reviewing NMOS Inverter functionality


V_i	NMOS	V_o
$V(0)$	OFF	V_{DD}
$V(1)$	ON	GND

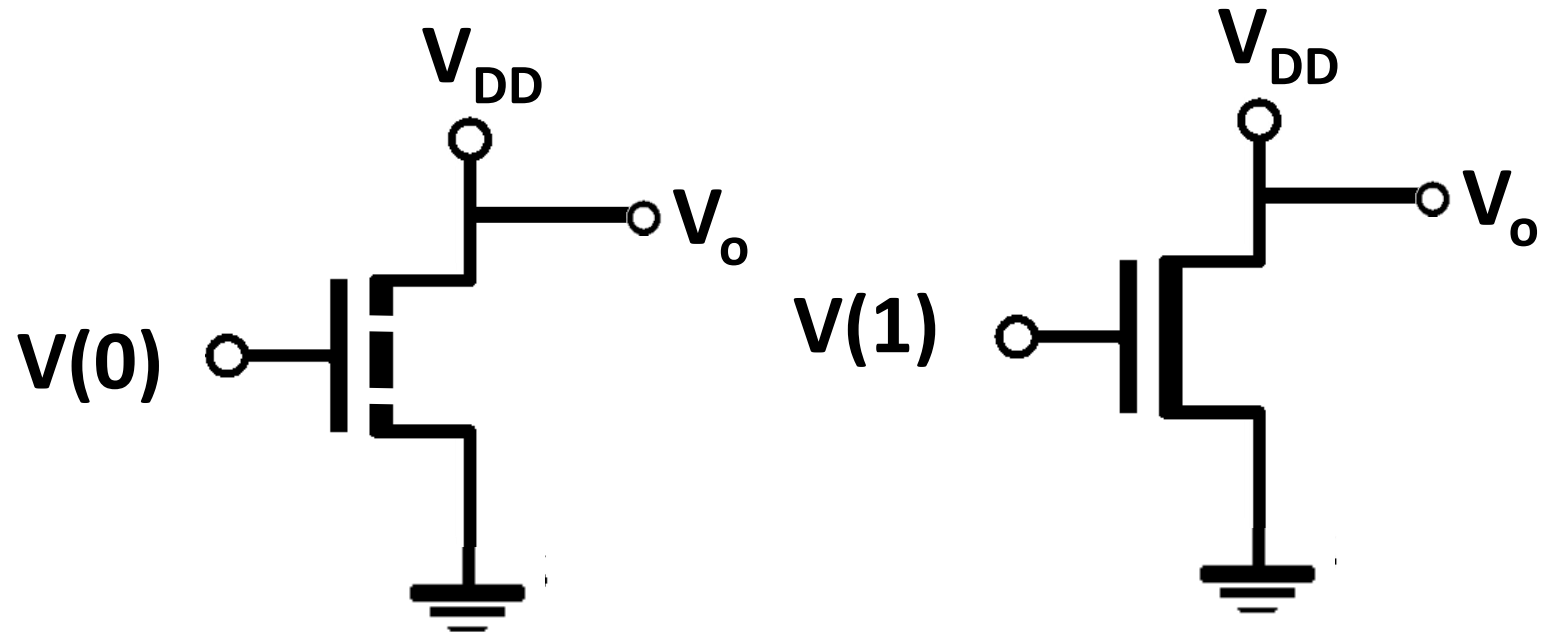

$$f(A_0, A_1) = \Sigma(1, 2, 3) = A_0 + A_1$$


A_0	A_1	output
0	0	0
0	1	1
1	0	1
1	1	1

Use NMOS for 0 outputs.

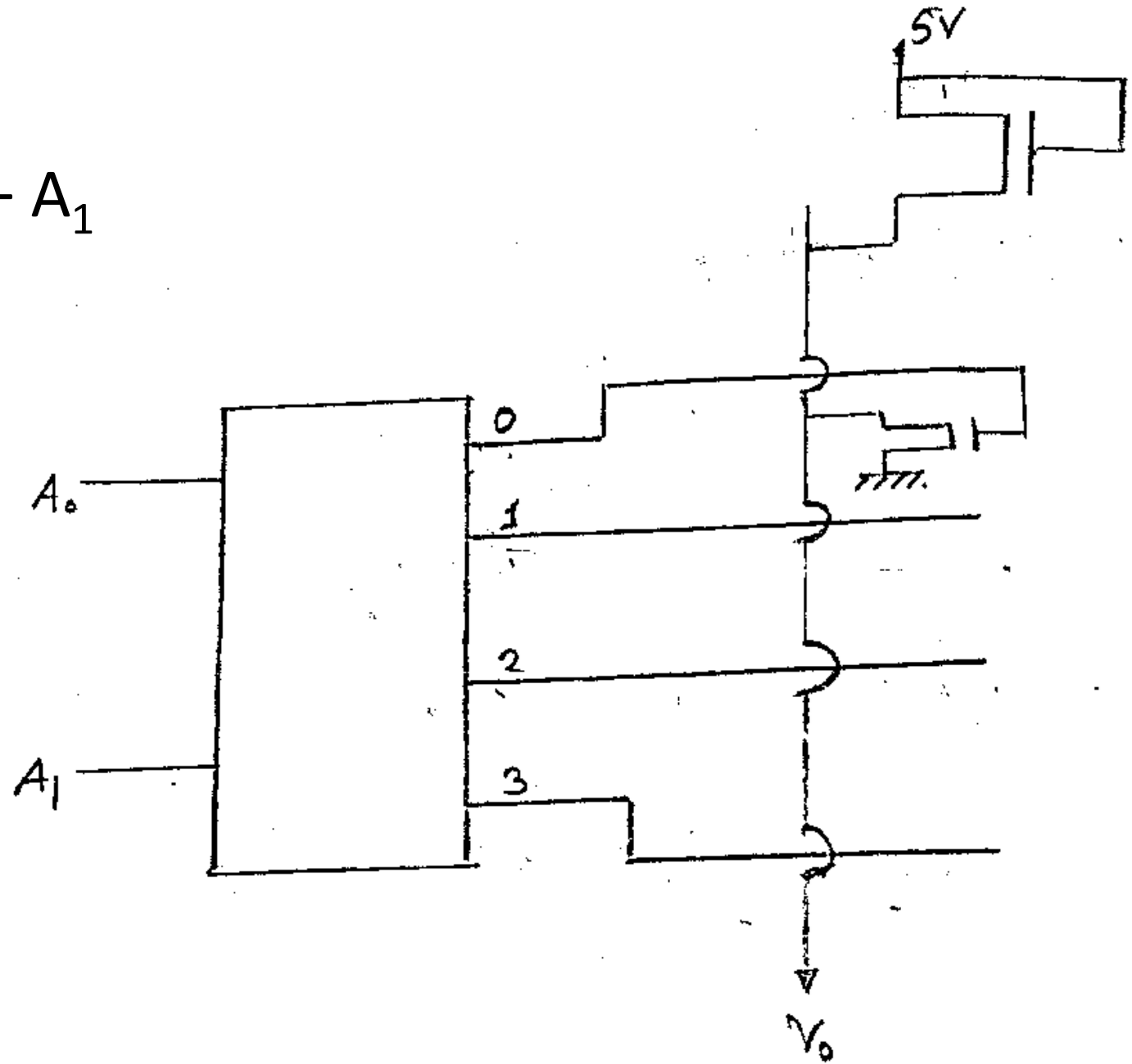

$$f(A_0, A_1) = \Sigma(3) = A_0 A_1$$


A_0	A_1	output
0	0	0
0	1	0
1	0	0
1	1	1

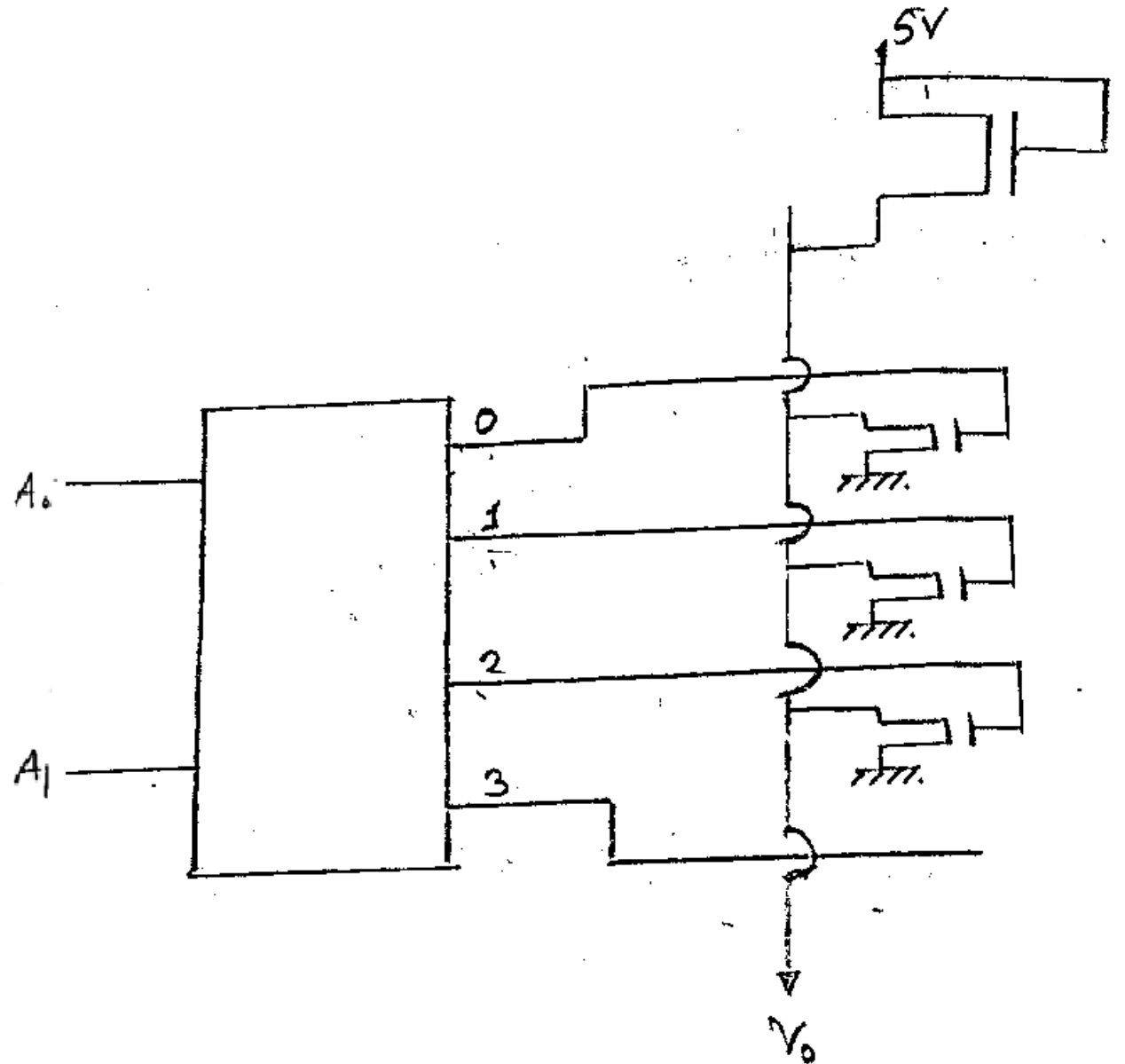

Implement $f(a,b,c) = \Sigma(2,3,5,6)$
using 4 x 1 ROM

Here, $\pi(0,1,4,7)$

Let,
a is selector

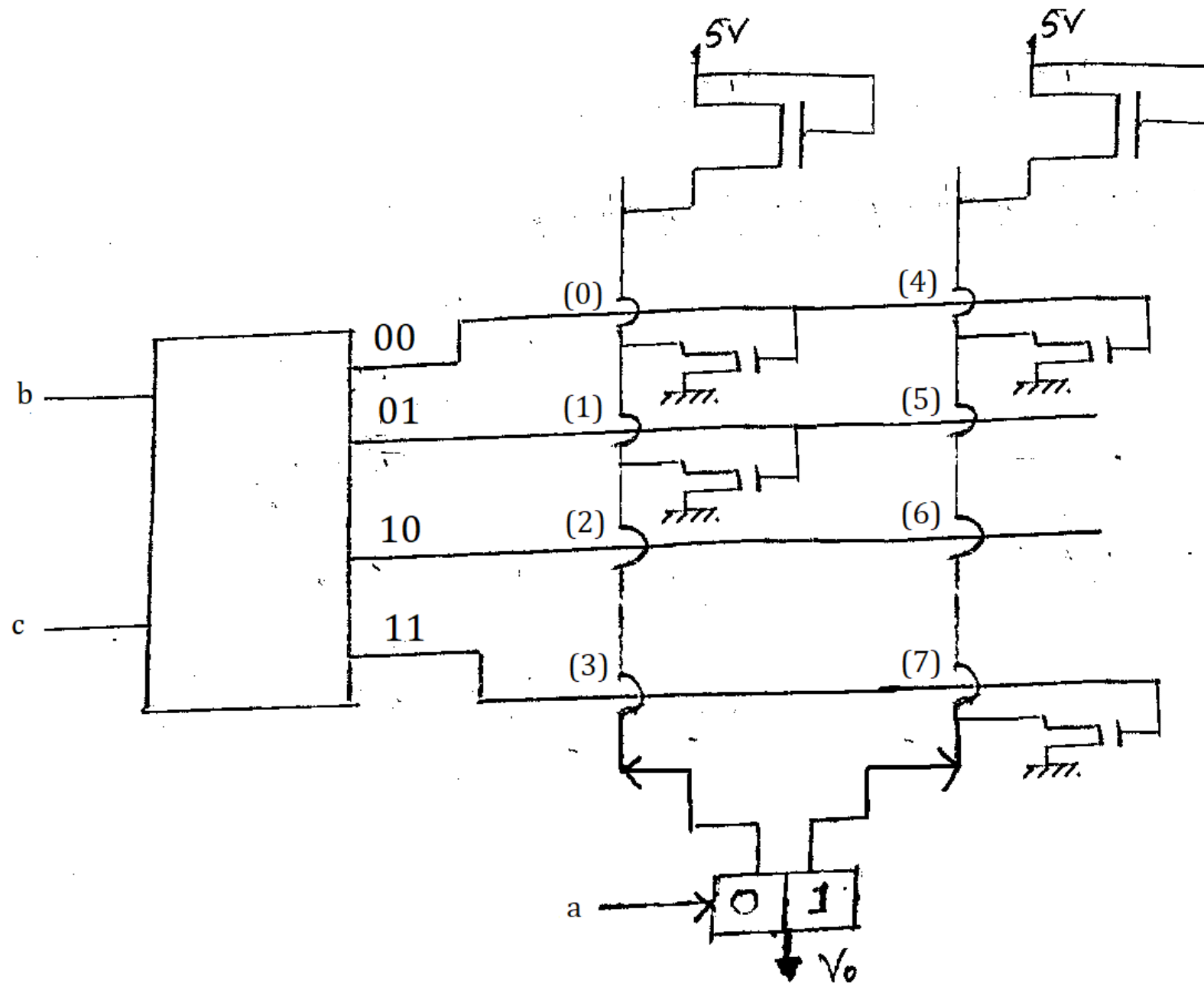

Implement using 2x1 or/and 4x1 ROM

- $F(a,b,c) = \Sigma(0,2,4,6)$
- $F(x,y,z) = xy + \bar{z}$
- $F(x,y,z) = xy + yz + zx$

*Hint: Express the equation into min terms and then implement them.