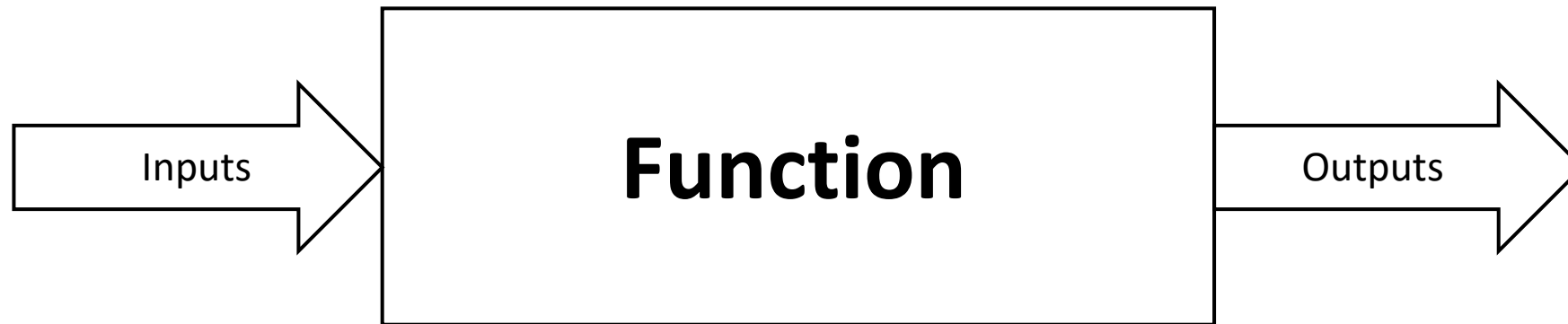


Digital System Design

Lecture - 1

What is a System?

- A set of related components working as a whole to achieve a definite goal
- A system contains:
 - a. Inputs
 - b. A function that converts the inputs to outputs
 - c. Outputs



What is a **Digital** System?

- A system in which signals have a finite number of discrete values
- **Advantages:**
 - a. Easy to design
 - b. Low cost, automated design and fabrication
- **Disadvantages:**
 - a. Physical World is analog
 - b. Less precision
- **Example:**
 - a. Calculator
 - b. Digital Voltmeter

A Combinational Circuit

- Consists of logic gates whose outputs at any time are determined directly from the present combination of inputs without regard to previous inputs.
- Example: Half Adder, Full Adder

A Sequential Circuit

- The outputs of a sequential circuit depend not only on present inputs, but also on past inputs. Moreover, the circuit behavior (function) must be specified by a time sequence of inputs and internal states.
- Example: Flip-flop

Types of Adders:

- **Half Adder:** The half adder accepts **two** binary digits as its input and produce two binary digits as output- a sum bit and a carry bit.
- **Full Adder:** The full adder accepts **three** binary digits as its input and produce two binary digits as output- a sum bit and a carry bit.

Half Adder

Truth Table:

Input		Output	
A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Output Function:

$$S = A'B + AB'$$
$$= A \oplus B$$

$$C = AB$$

Logic Circuit:



Full Adder

Truth Table:


Input			Output	
A	B	C _{in}	S	C _{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Output Function:

$$S = A \oplus B \oplus C_{in} \text{ [Try yourself]}$$

$$C_{out} = AB + (A \oplus B) C_{in} \text{ [Try yourself]}$$

Logic Circuit:

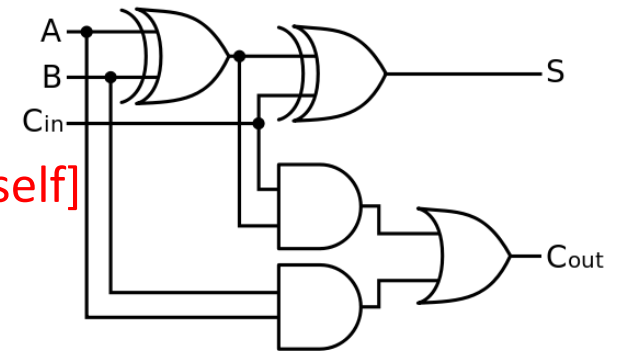

Full Adder (Contd.)

Let,

$$C_{in} = C$$

$$\text{Hence, } S_i = A_i \oplus B_i \oplus C_i$$

And, C_{out} is the C_{in} for the next step.

$$\text{Hence, } C_{i+1} = A_i B_i + (A_i \oplus B_i) C_i$$

Let,

$$A_i \oplus B_i = P_i \text{ and } A_i B_i = G_i$$

So, we get,

$$C_{i+1} = G_i + P_i C_i$$

Substituting $i=1,2,\dots$, we get,


$$C_2 = G_1 + P_1 C_1$$

$$C_3 = G_2 + P_2 C_2$$

$$= G_2 + P_2 (G_1 + P_1 C_1)$$


.....

Binary Adder

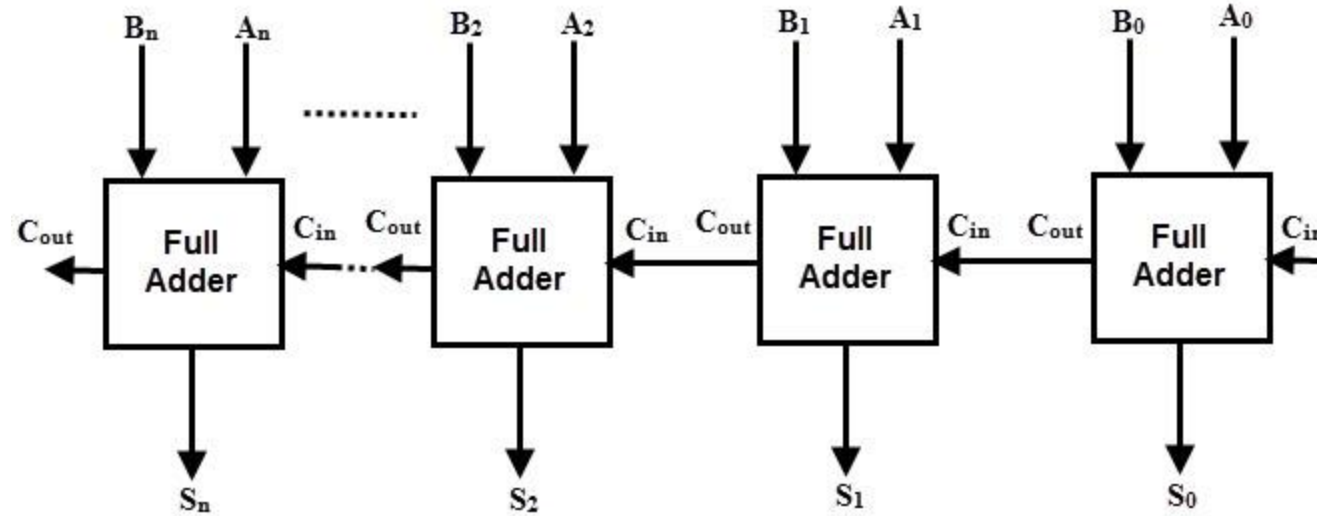

Full Adder using Half Adders

Block Diagram:

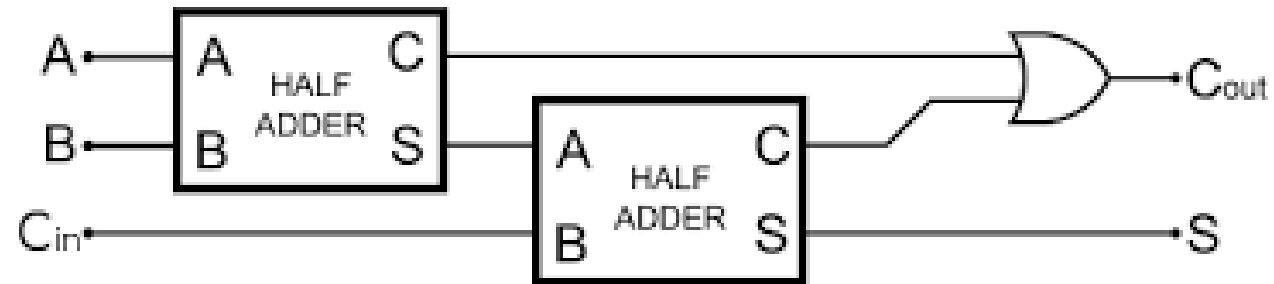

Circuit Diagram:

