
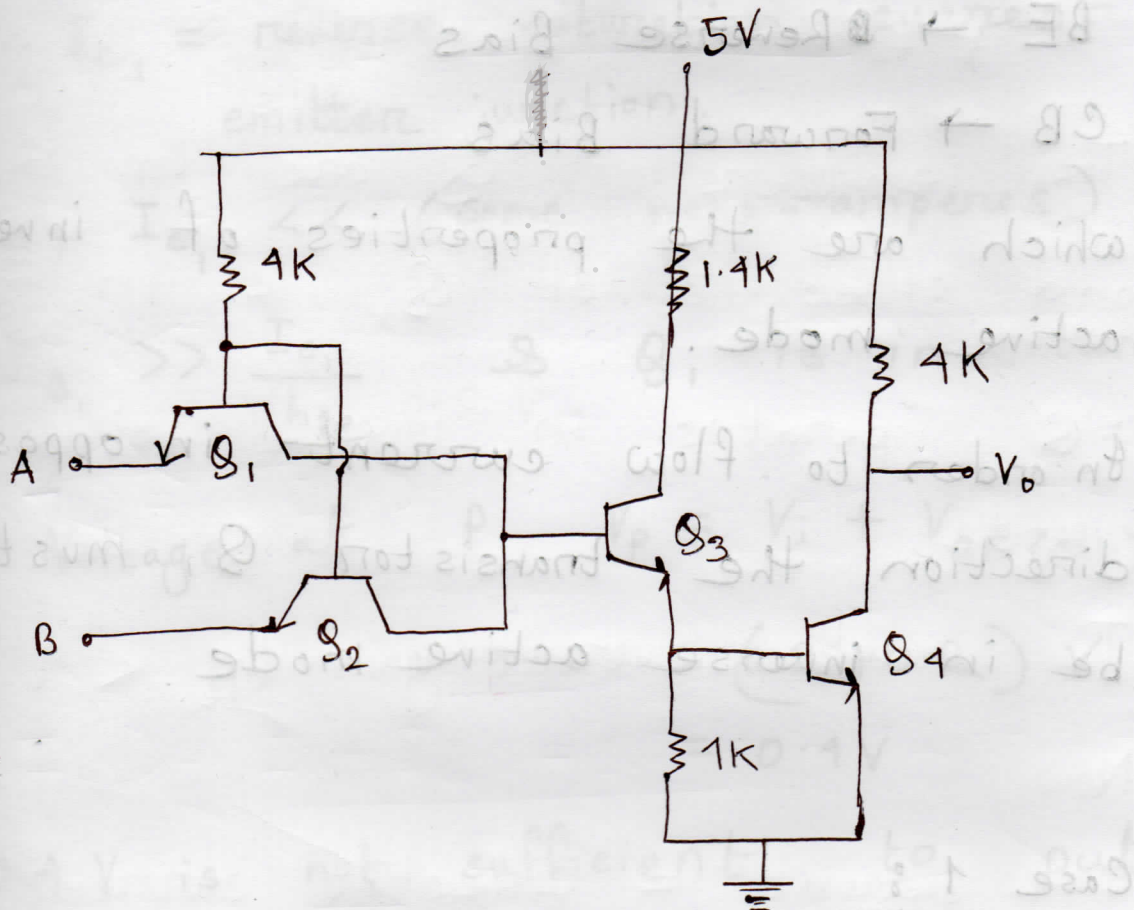


TTL or T²L Gate

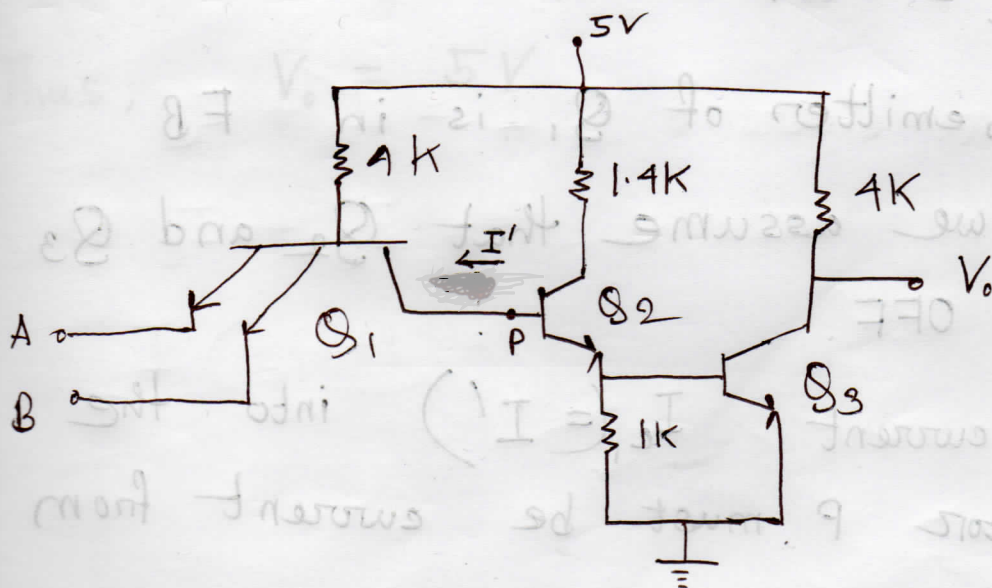

Equivalent ckt



Here, in Q_1 ,

BE \rightarrow Reverse Bias

CB \rightarrow Forward Bias

which are the properties of inverse active mode.

In order to flow current in opposite direction the transistor Q_1 must be in inverse active mode.

Case 1 :

$$\exists V_i = 0.2V$$

Then, emitter of Q_1 is in FB

And, we assume that Q_2 and Q_3 are OFF.

The current $I_{c1} (= I')$ into the collector P must be current from

emitter to base of Q_2

$\therefore I_{c_1}$ = reverse saturation current of emitter junction.

As, $I_{c_1} \ll$ (some nano-amperes)

$I_{B_1} \gg \frac{I_{c_1}}{h_{fe}}$ & Q_1 is in saturation.

\therefore Voltage at P, $V_P = V_i + V_{CE(sat)}$

$$= (0.2 + 0.2) \text{ V} \\ = 0.4 \text{ V}$$

0.4 V is not sufficient to put Q_2 & Q_3 ON.

Thus, $V_o = 5 \text{ V}$.

Case 2 :

$$V_{i} = 5V$$

The emitters of Q_1 are in RB and collector of Q_1 is in FB.

$\therefore Q_1$ operates in inverse active mode.

The inverted current gain, $h_{fe} < 1$

Now,

$$\begin{aligned} \text{I/P current} &= \text{collector current} \\ &= h_{fe} * I_B \end{aligned}$$

$$\begin{aligned} \text{Emitter current, } I' &= I_B + I_C \\ &= I_B + I_B * h_{fe} \\ &= (1 + h_{fe}) I_B \end{aligned}$$

As, the direction is reversed for I' .

$$I' = - (1 + h_{fe}) I_B$$

This I' is large enough to draw Q_2 & Q_3 in saturation.

Thus, $V_o = 0.2 \text{ V}$.