# CSE 3110 Digital System Design Sessional ALU Online

Time: 35 min

## **Instruction:**

Select your set by last 3 digit of your roll mod 4.

For example, if your roll is 180204200, you should answer the set  $(200 \mod 4) = \text{Set } 0$ .

Please note that you won't get any marks if you do not answer the correct set.

Please remember that any sort of plagiarism will result in -20 marks without further explanation.

<u>Set-0</u>

Design the following 4-bit ALU (Arithmetic Logic Unit):

S2	<b>S1</b>	S0	Output	Function
1	1	0	Ai - Bi	Subtract
0	1	0	Ai + 1 + 1	Transfer A with Carry
1	1	1	Ai + Bi	Add
1	0	1	Ai'	Complement A
0	0	0	Ai I Bi	OR

- Report (PDF File)
  - o Function table
  - Output functions for Xi, Yi, Zi
  - o Circuit diagram for Xi, Yi, Zi (Hand drawing)
- Proteus implementation (.pdsprj File)

Set-1

Design the following 4-bit ALU (Arithmetic Logic Unit):

S2	S1	S0	Output	Function
0	0	0	Ai - 1	Decrement A
1	0	1	Ai + 1 + 1	Transfer A with Carry
0	0	1	Ai - Bi - 1	Subtract with Borrow
0	1	0	Ai xor Bi	XOR
1	1	1	Ai'	Complement A

- Report (PDF File)
  - o Function table
  - Output functions for Xi, Yi, Zi
  - o Circuit diagram for Xi, Yi, Zi (Hand drawing)
- Proteus implementation (.pdsprj File)

Set-2

Design the following 4-bit ALU (Arithmetic Logic Unit):

S2	<b>S1</b>	S0	Output	Function
0	1	1	Ai	Transfer A
0	0	1	Ai + Bi + 1	Add with Carry
0	1	0	Ai - 1	Decrement A
1	1	0	Ai xor Bi	XOR
1	0	0	Ai   Bi	OR

- Report (PDF File)
  - o Function table
  - Output functions for Xi, Yi, Zi
  - o Circuit diagram for Xi, Yi, Zi (Hand drawing)
- Proteus implementation (.pdsprj File)

Set-3

Design the following 4-bit ALU (Arithmetic Logic Unit):

S2	<b>S1</b>	S0	Output	Function
0	0	0	Ai + Bi	Add
0	0	1	Ai – Bi -1	Subtraction with Borrow
1	0	1	Ai	Transfer A
1	1	0	Ai . Bi	AND
0	1	1	Ai   Bi	OR

- Report (PDF File)
  - o Function table
  - Output functions for Xi, Yi, Zi
  - o Circuit diagram for Xi, Yi, Zi (Hand drawing)
- Proteus implementation (.pdsprj File)