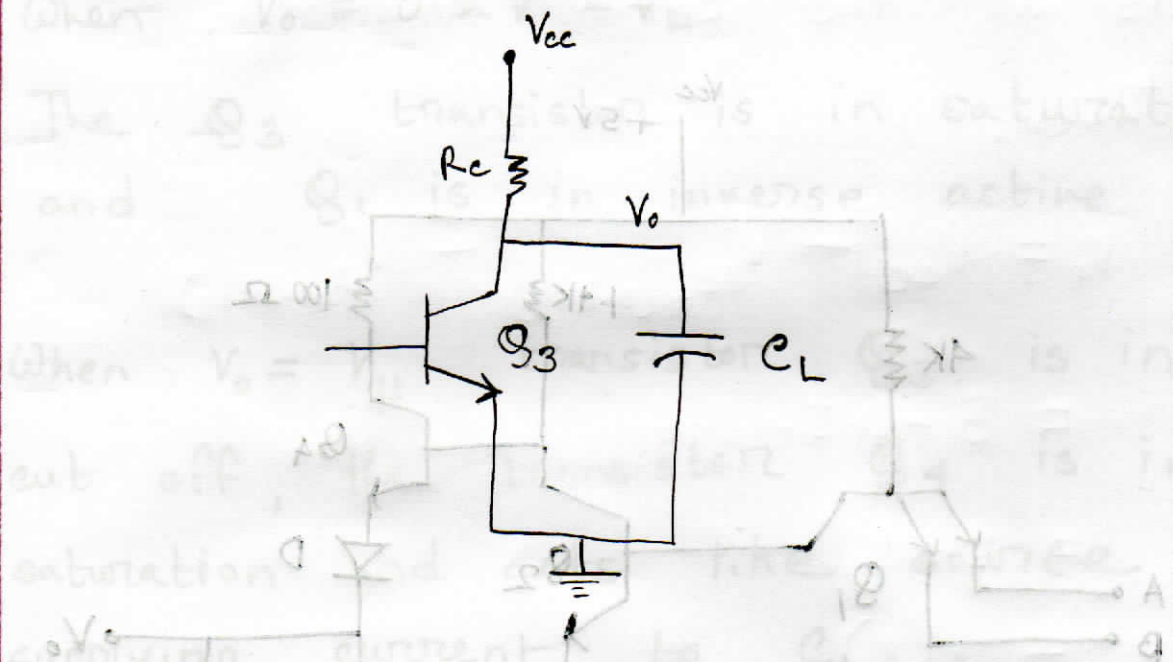


## Passive pull-up ckt




When  $V_o$  changes from  $0.2\text{ V}$  to  $V_{cc}$  then  $Q_3$  is in cut-off and the capacitor charges exponentially from  $V_{CE(sat)}$  to  $V_{cc}$ .

$$I = \frac{V_{cc} - V_{CE(sat)}}{R_c}$$

$$\text{Time constant} = R_c C_L \quad [C_L = \text{fixed}]$$

Wired End :

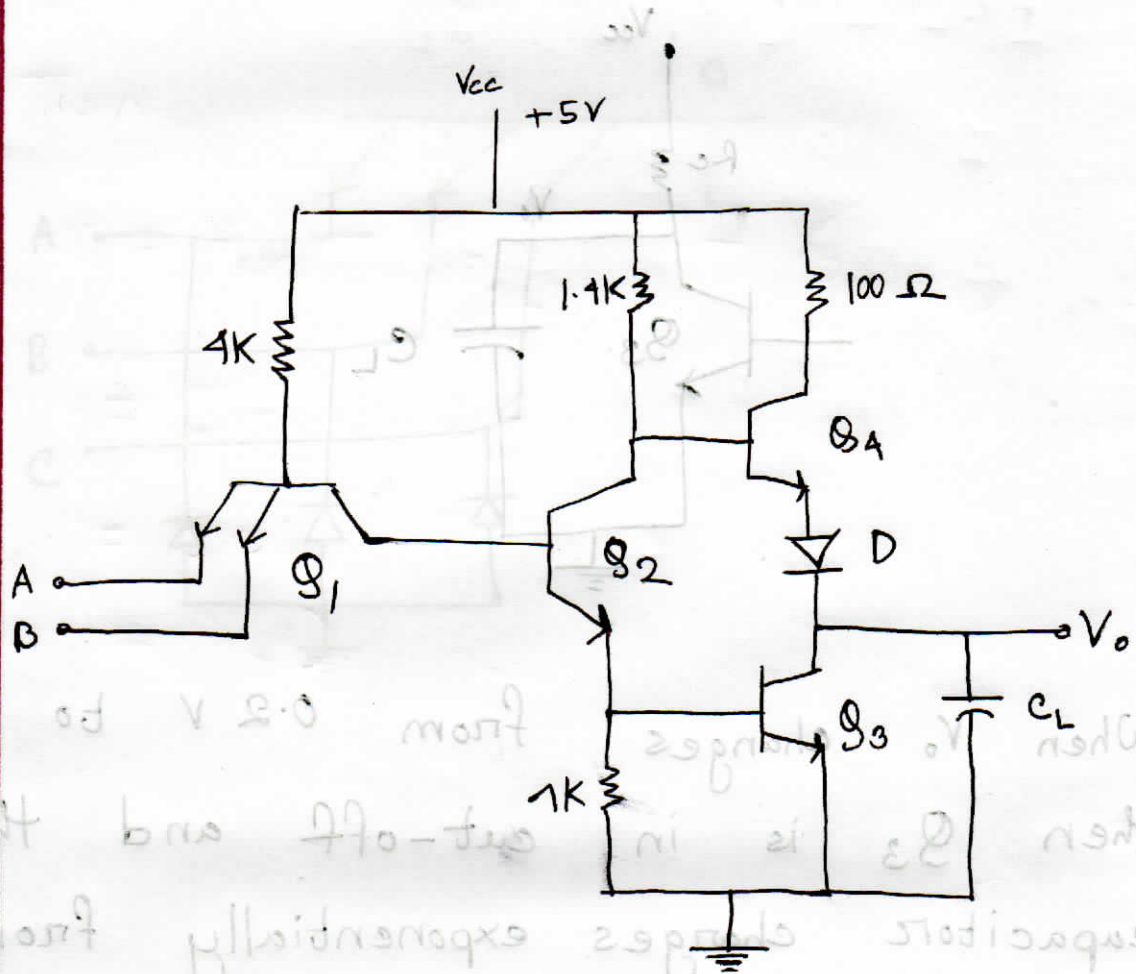

In this ckt, transistor  $Q_4$  acts like an active pull-up  $V_{OH} =$  ckt replacing the passive pull up resistor  $R_c$ . This output configuration is called "totem-pole"

amplifier because  $Q_4$  sits up on  $Q_3$

When  $V_o = 0.2 V = V_L$

The  $Q_3$  transistor is in saturation and  $Q_4$  is in inverse active mode

When  $V_o = V_H$  transistor  $Q_3$  is in cut off, the transistor  $Q_4$  is in saturation and acts like  $V_{source}$  supplying current to  $C_L$ .

The diode is used because the value of  $i$  will decrease and dissipation will decrease.

Here,  $Q_4$  and diode combinedly form the active pull up  $ckt$ .

When,  $V_o$  increases the current in  $Q_4$  decreases, and  $Q_4$  comes out of saturation and finally  $V_o$

reaches a steady state when  $Q_4$  is at the cutin condition.

Then,

$$V_o = V_{cc} - V_{BE_4(\text{cutin})} - V_{D(\text{cutin})}$$

$$= 5 - 0.5 - 0.6$$

$$= 3.9 \text{ V}$$

$$= V(1)$$