

*Ahsanullah University of Science and Technology
Department of Computer Science and Engineering
Course No: CSE2106 Course Title: Digital Logic Design Lab
Experiment 08 & 09*

Experiment -08

- a. Design a 4-Bit CLA (Carry Look Ahead) Adder Circuit.
- b. Design a Magnitude Comparator for 4-Bit Using Logic Gates.

Experiment -09 (GOOGLE THE ICs TO HAVE PIN NUMBERS)

- a. Design a 4 to 2-Line Priority Encoder Where the Priority is-

$$I_0 < I_1 < I_2 < I_3$$

- b. Implement the Following Boolean Function Using
 - I. An 8 to 1-Line Multiplexer (IC-74151)
 - II. A 4 to 1-Line Multiplexer (IC-74153)

And Other Basic Gates.

$$F(A, B, C, D) = \sum (1, 3, 5, 8, 11, 14)$$

- c. Implement the Following Boolean Function Using
 - I. 1 to 8-Line De-Multiplexer / 3 to 8-Line Decoder (IC-74138)
 - II. 1 to 16-Line De-Multiplexer / 4 to 16-Line Decoder (IC-74154)

$$F(A, B, C, D) = \sum (2, 3, 5, 7, 11, 13)$$