Ahsanullah University of Science and Technology (AUST)
Department of Computer Science and Engineering

LAB REPORT

Course No. : CSE2210

Course Title: Digital Electronics and Pulse Techniques Lab

Experiment Number: 05

Name of the Experiment: Implementation of clocked SP Flip Flop using RTL NOR gates.

Submitted By:

180204142   S. M Tasnimul Hasan